
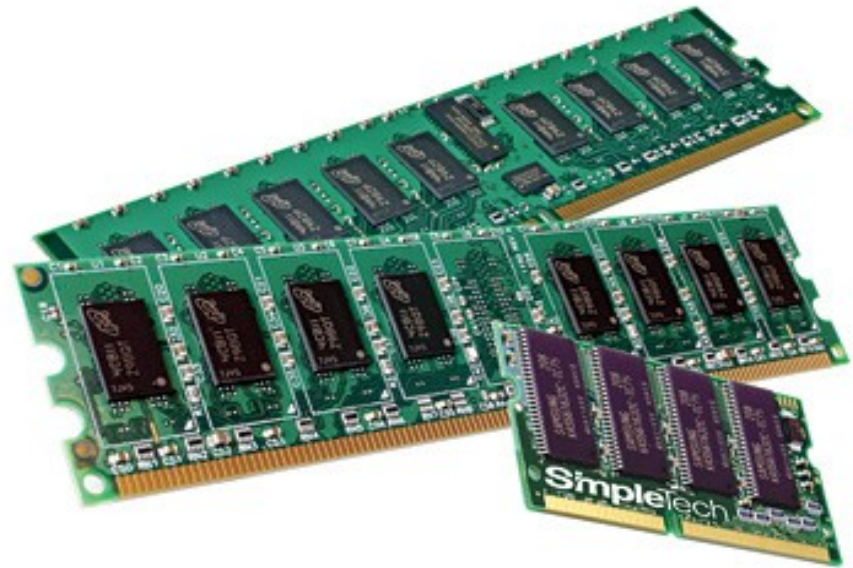


Logic Design: Implementing Memory

 Memory: an organism's ability to **store, retain and recall** information




Delay Line memory




gebruikt van fysica van eigenschappen van stoffen om iets op te slaan

 
werd erg vertraagd vanbinnen om 'op te slaan' voor paar minuten



Magnetic Core memory

 

 ferromagnetische ringetjes matrix, gemagnetiseerd of nt gemagnetiseerd, elk is 1 bit




Modern memory bank



Clock Signal

(memory retains data over time)

 


Clocking methodology:

determines when data is valid and stable relative to the clock

Edge-triggered clocking:

all state changes occur on a clock edge

Digital Signals (analog reality)

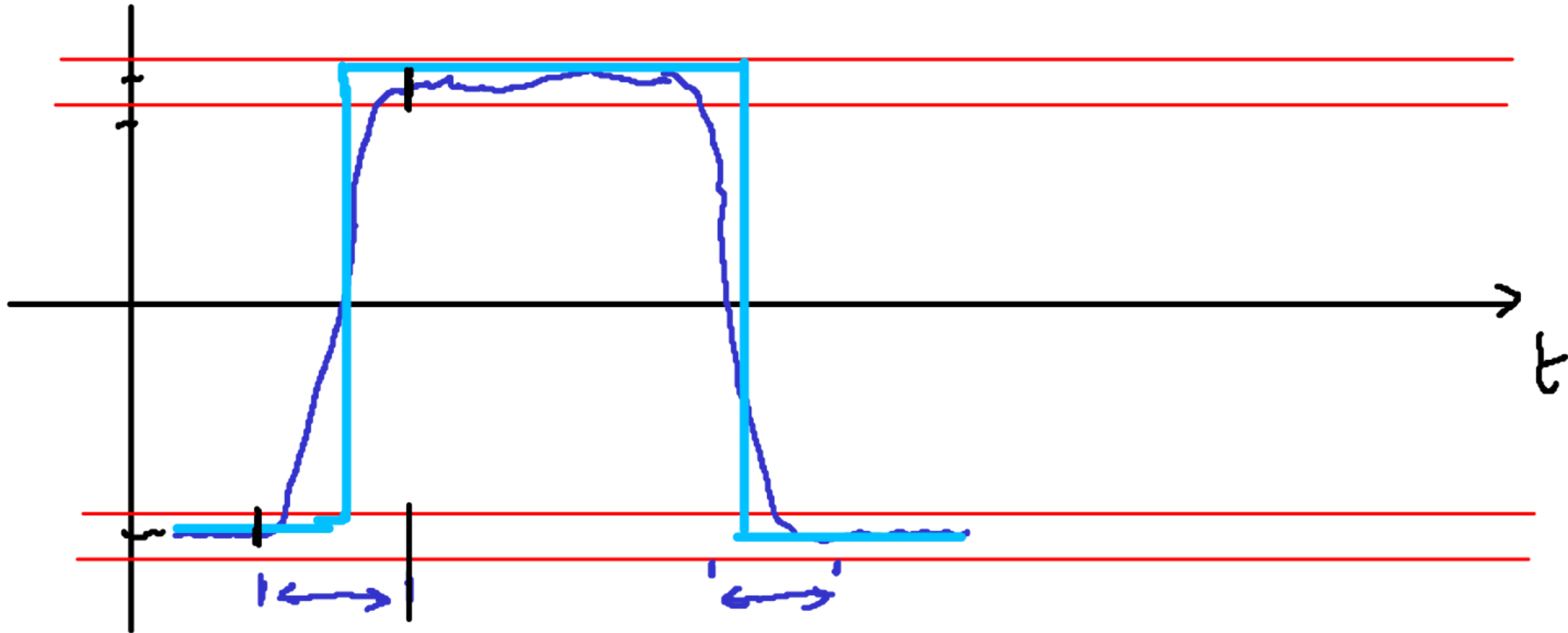


State Elements: “memory”

State Element → Combinational Logic → State Element
(function/computation)




Latch: store value

 S-R Latch (unclocked): store and remember value



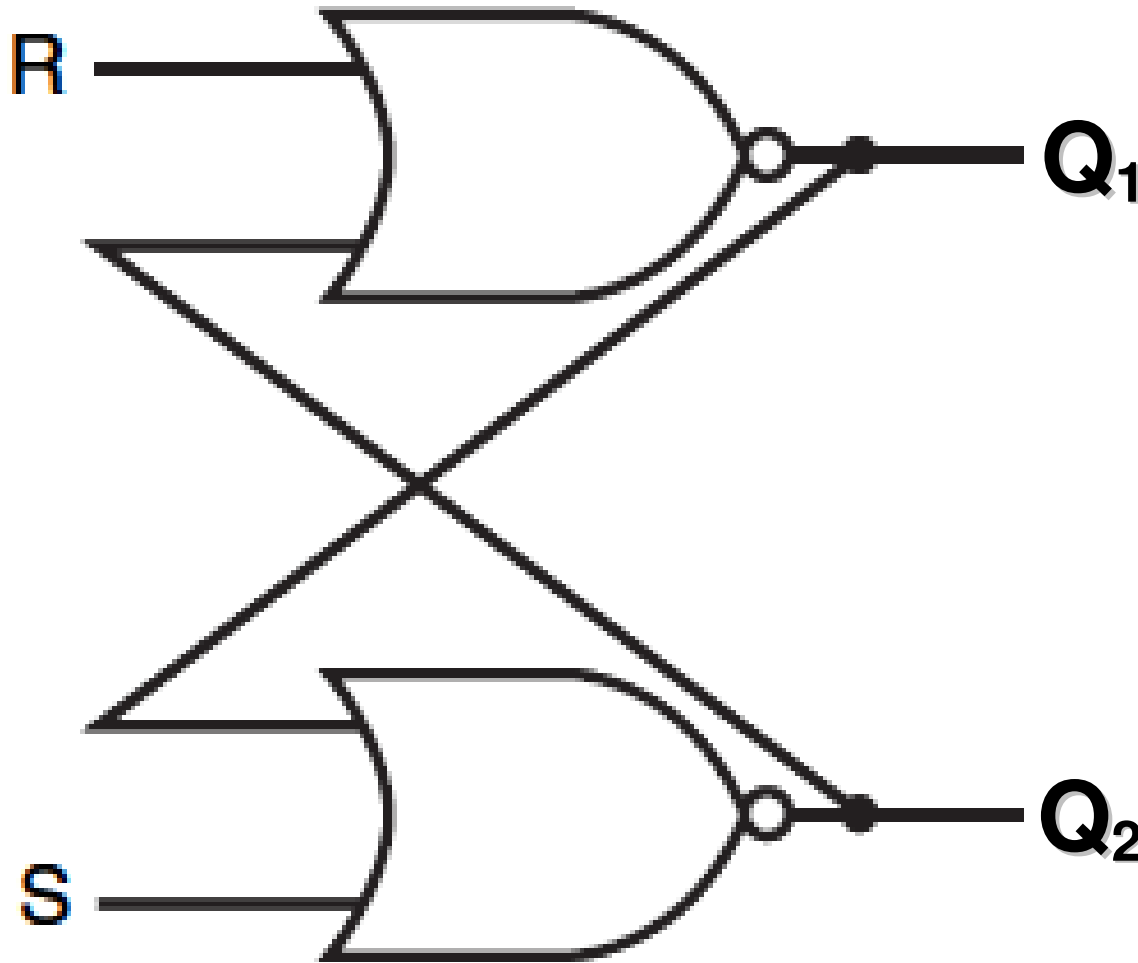S-R Latch (unclocked): store and remember value



$$Q_1 = \text{not } (R \text{ or } Q_2)$$

$$Q_2 = \text{not } (S \text{ or } Q_1)$$

→

$$Q_1 = \text{not } (R \text{ or } \text{not } (S \text{ or } Q_1))$$


$$Q_2 = \text{not } (S \text{ or } Q_1)$$

→

$$Q_1 = \text{not } R \text{ and } (S \text{ or } Q_1)$$

$$Q_2 = \text{not } (S \text{ or } Q_1)$$

S-R Latch set

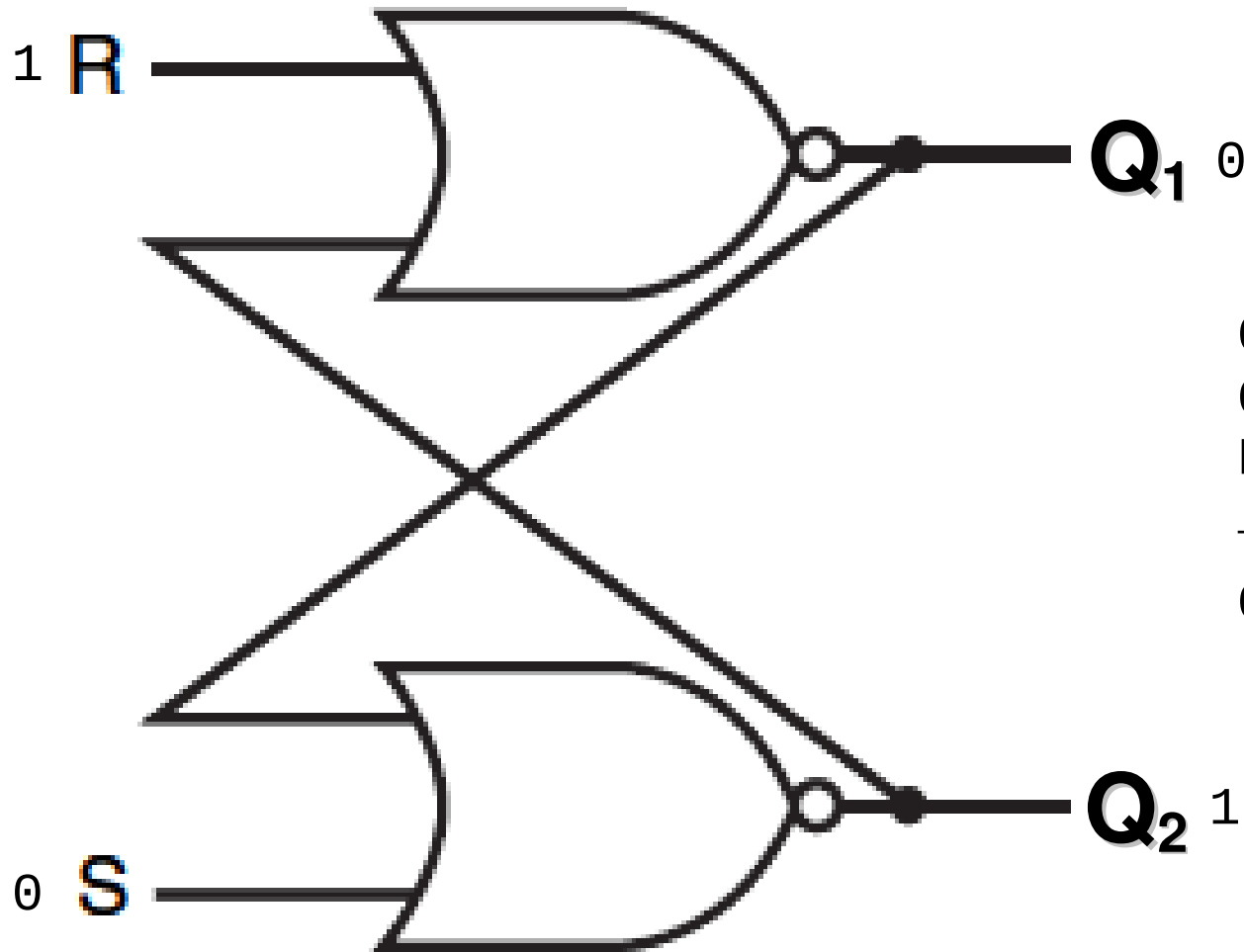

$$Q_1 = \text{not } R \text{ and } (S \text{ or } Q_1)$$


$$Q_2 = \text{not } (S \text{ or } Q_1)$$

$$R = 1, S = 0$$

→

$$Q_1 = 0, Q_2 = \text{not } Q_1 = 1$$

S-R Latch remember output value

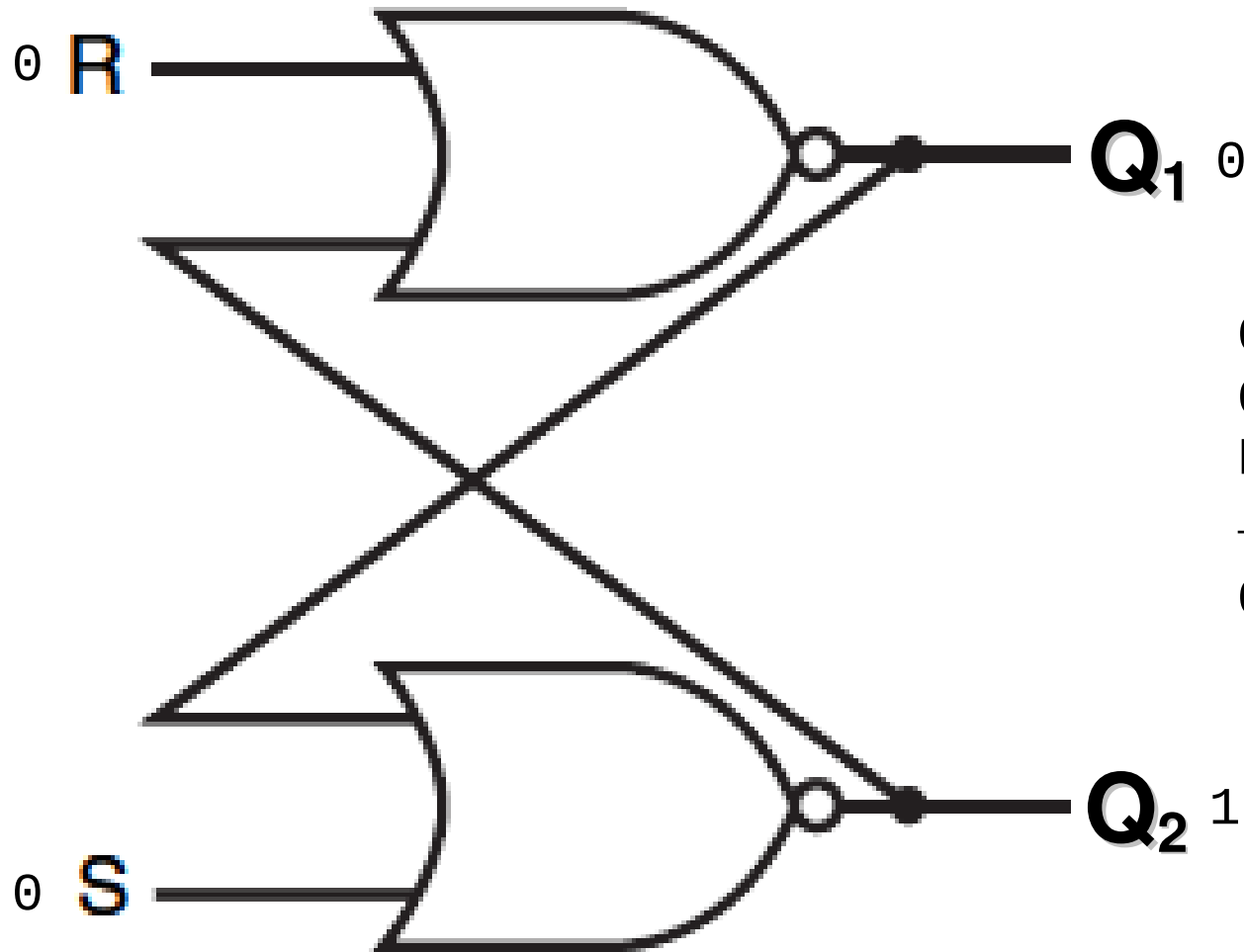

$$Q_1 = \text{not } R \text{ and } (S \text{ or } Q_1)$$


$$Q_2 = \text{not } (S \text{ or } Q_1)$$

$$R = 0, S = 0$$

→

$$Q_1 = Q_1, Q_2 = \text{not } Q_1$$

S-R Latch set

 

$$Q_1 = \text{not } R \text{ and } (S \text{ or } Q_1)$$


$$Q_2 = \text{not } (S \text{ or } Q_1)$$

$$R = 0, S = 1$$

→

$$Q_1 = 1, Q_2 = 0 = \text{not } Q_1$$

S-R Latch remember output value

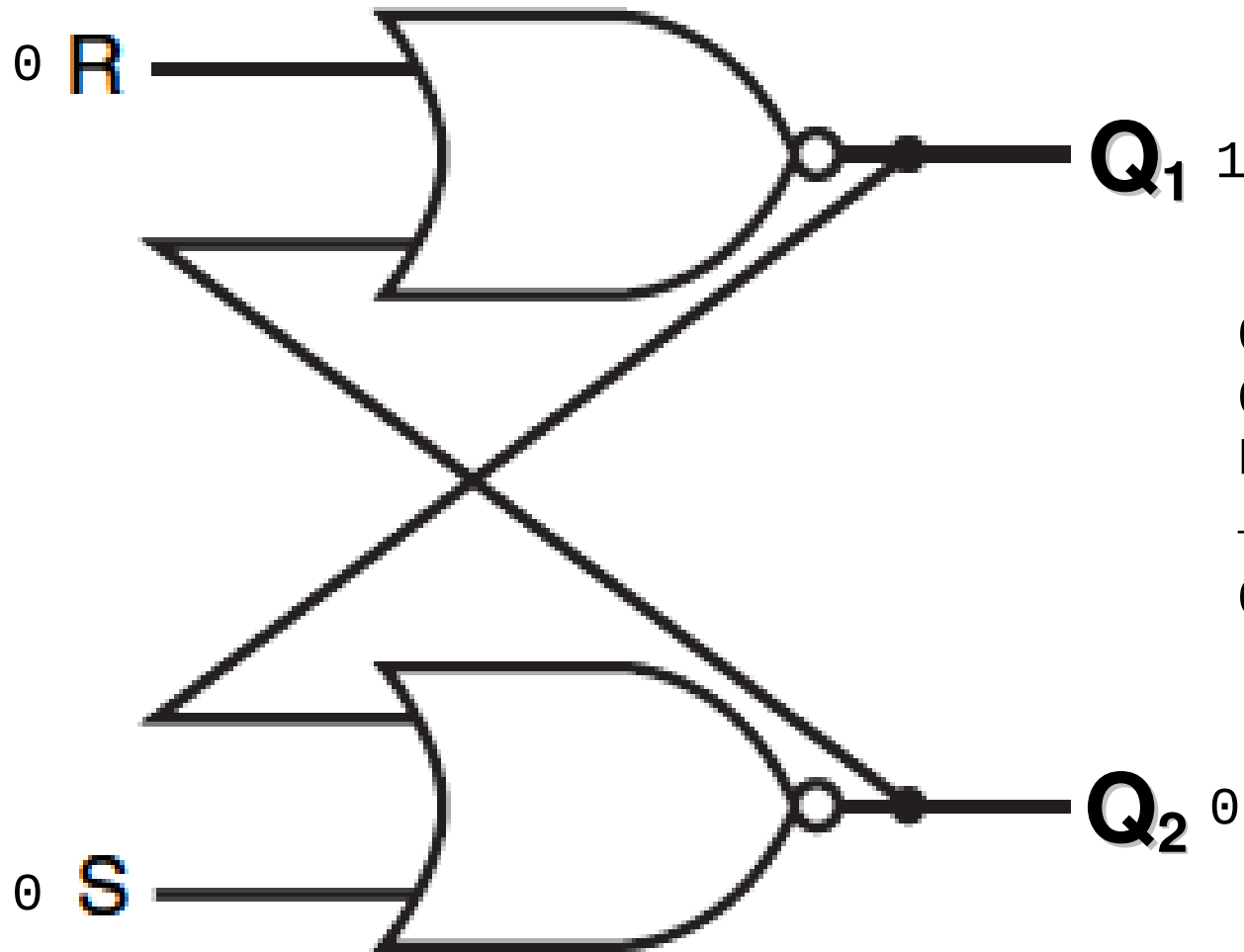

$$Q_1 = \text{not } R \text{ and } (S \text{ or } Q_1)$$


$$Q_2 = \text{not } (S \text{ or } Q_1)$$

$$R = 0, S = 0$$

→

$$Q_1 = Q_1, Q_2 = \text{not } Q_1$$

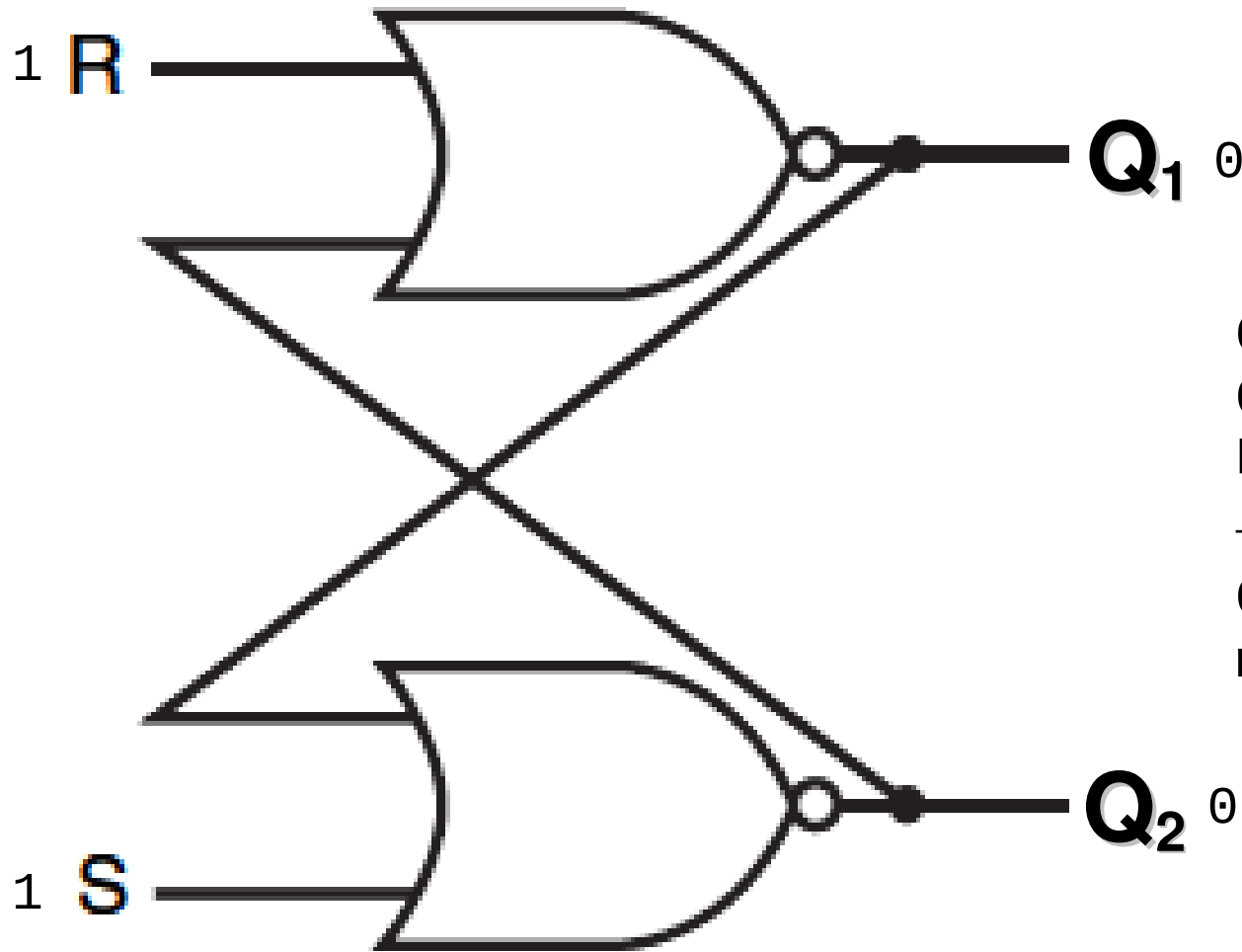S-R Latch — no longer $Q_2 = \text{not } Q_1$



$$Q_1 = \text{not } R \text{ and } (S \text{ or } Q_1)$$

$$Q_2 = \text{not } (S \text{ or } Q_1)$$

$$R = 1, S = 1$$

→

$$Q_1 = 0, Q_2 = 0$$

may become meta-stable
(**analog** reality: delays)

Latch:

change **while** clock **asserted**
(clock connected to R or S)

Flip-Flop:


change **on** clock **edge**

D latch ("transparent")

data

C: "Clock"

D: "Data"

 

$R = C \text{ and not } D$

$S = C \text{ and } D$

→

when C = 1: "open"

$R = \text{not } D$

$S = D$

→ $Q = S = D$

when C = 0: "closed"

$R = 0$

$S = 0$


→ Q is not changed

$R = S = 1$


not possible

R = 1 en S = 1 not possible
will destabilise and ruin the latch

D latch operation

 


D latch operation

 

What if *D* changes during *C* asserted?


When ***C*** is asserted (high), the output ***Q*** follows the input ***D***.
If ***D*** changes while ***C*** is high, ***Q*** will update to match ***D***.

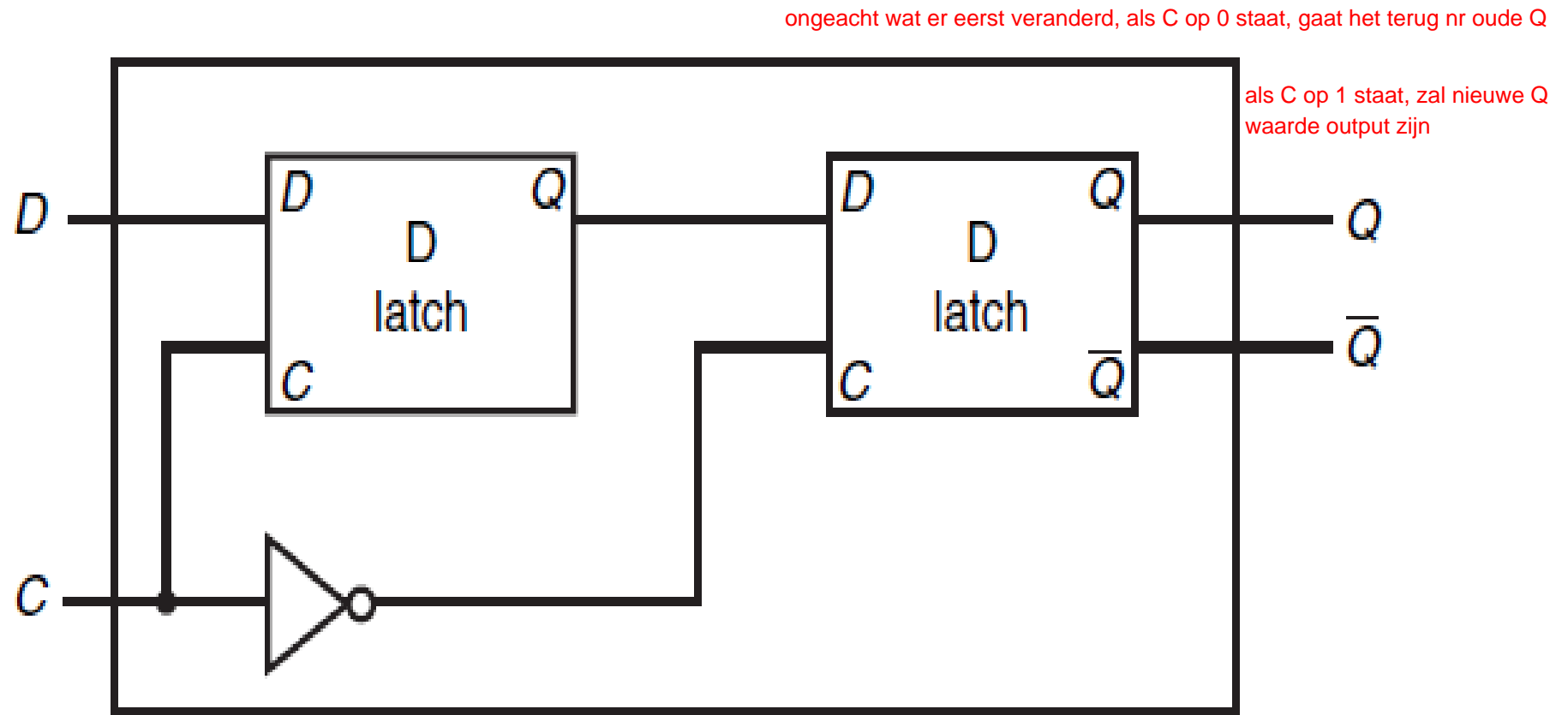D flip-flop (not “transparent”) with falling-edge trigger




data komt binnen, C staat op 1, data wijzigt, maar op moment van falling edge van clock, wordt laatste waarde bewaard

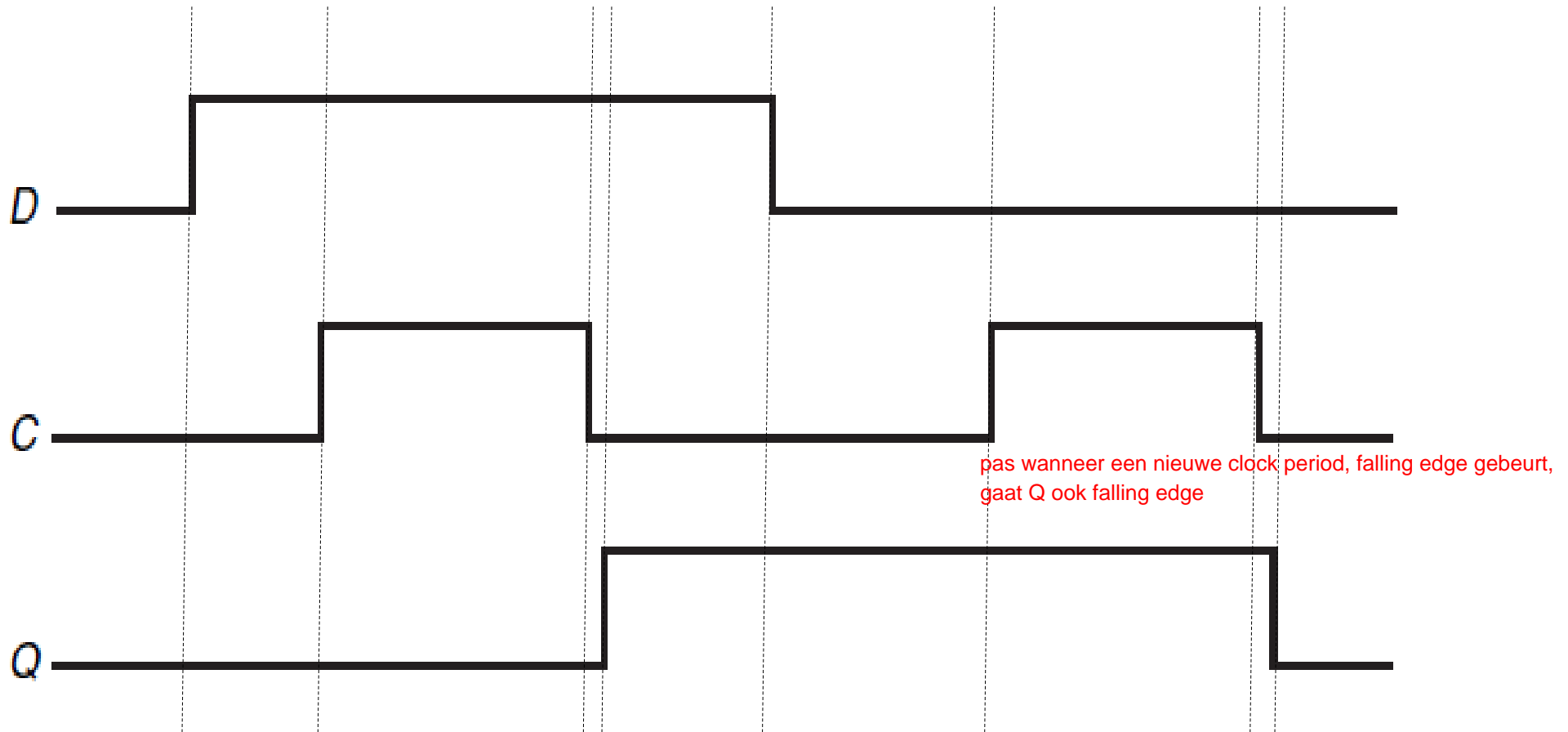
D flip-flop with falling-edge trigger operation



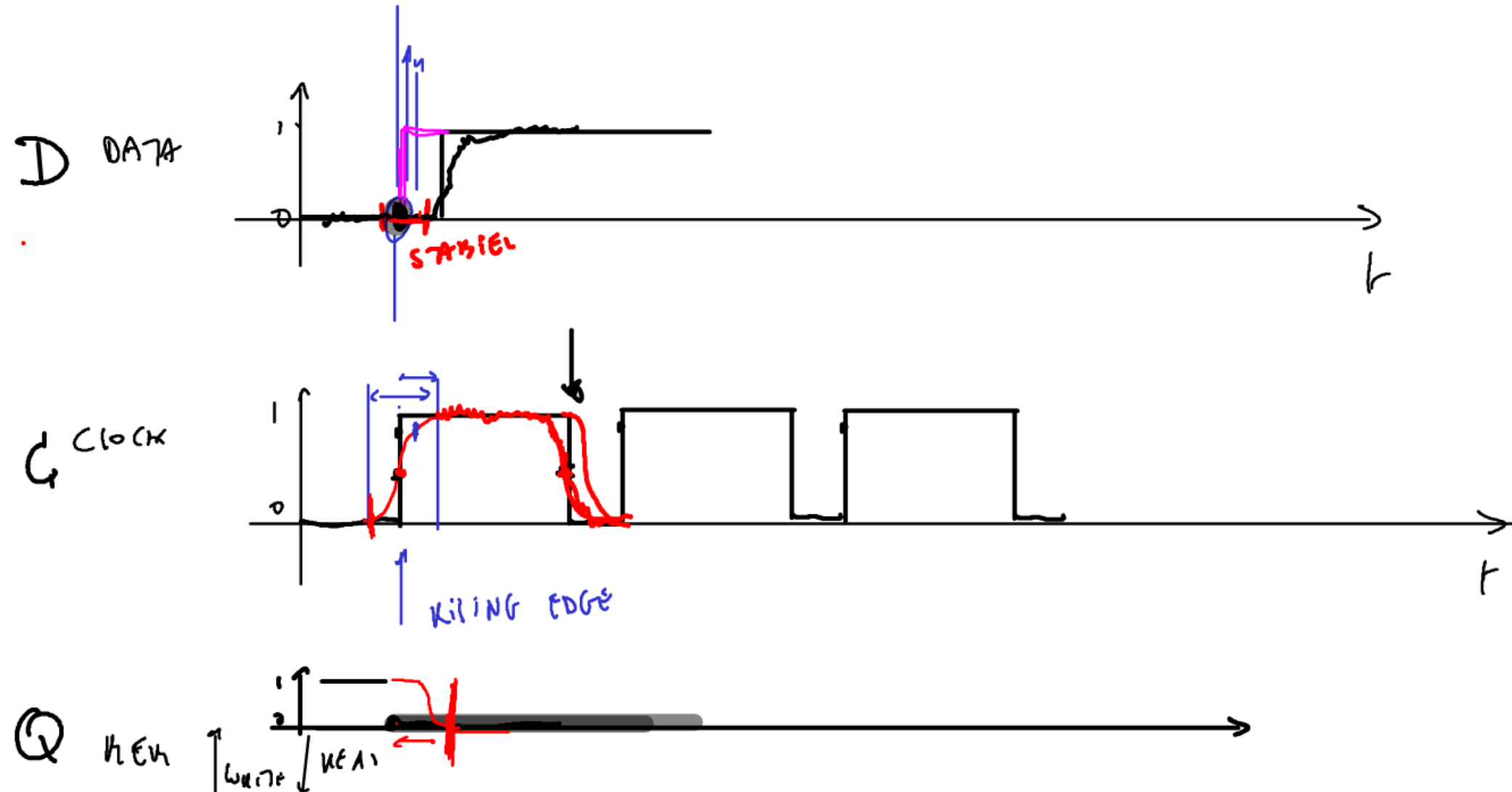timing constraints: “leaky” abstraction (rising edge)



 D flip-flop (falling edge) timing constraints




Register File

k-bit registers
(using k D flip-flops, see later: 4x2 SRAM)


number of registers n
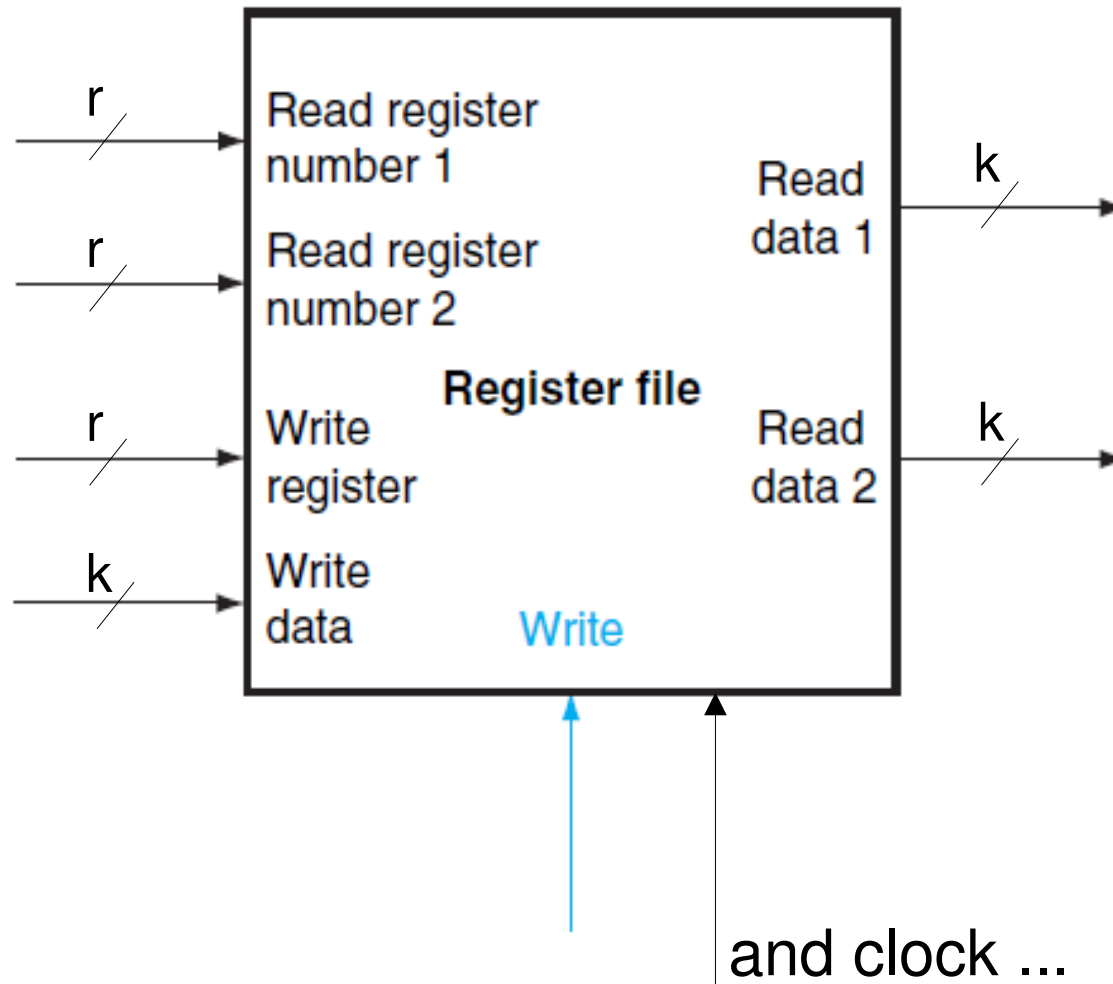
$$\rightarrow r = \lceil \log_2 n \rceil$$




Register File: read

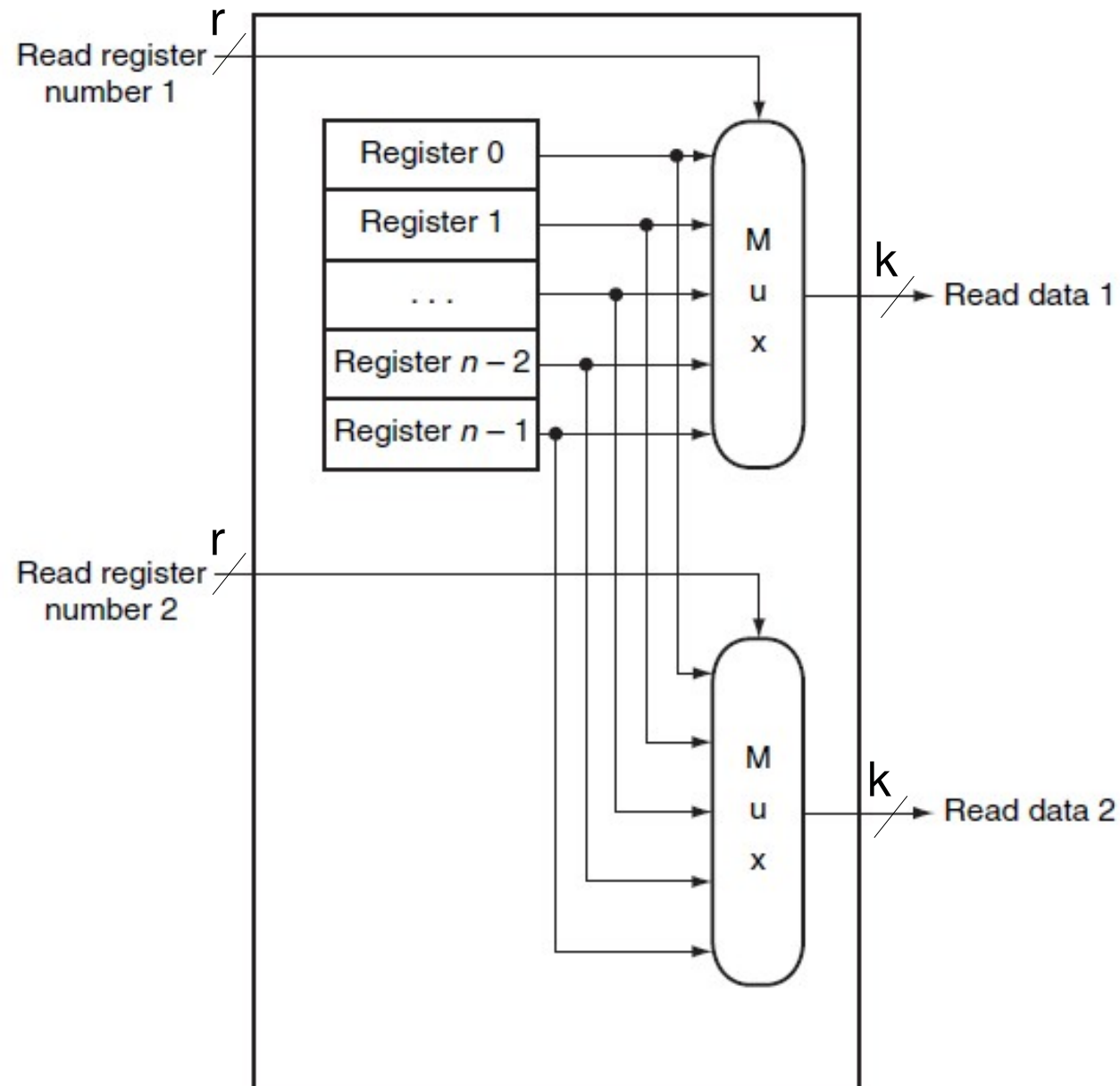selecteren van een bep. adres
=> vb 2 milj, multiplexor met 2 milj wordt moeilijk




Register File: write

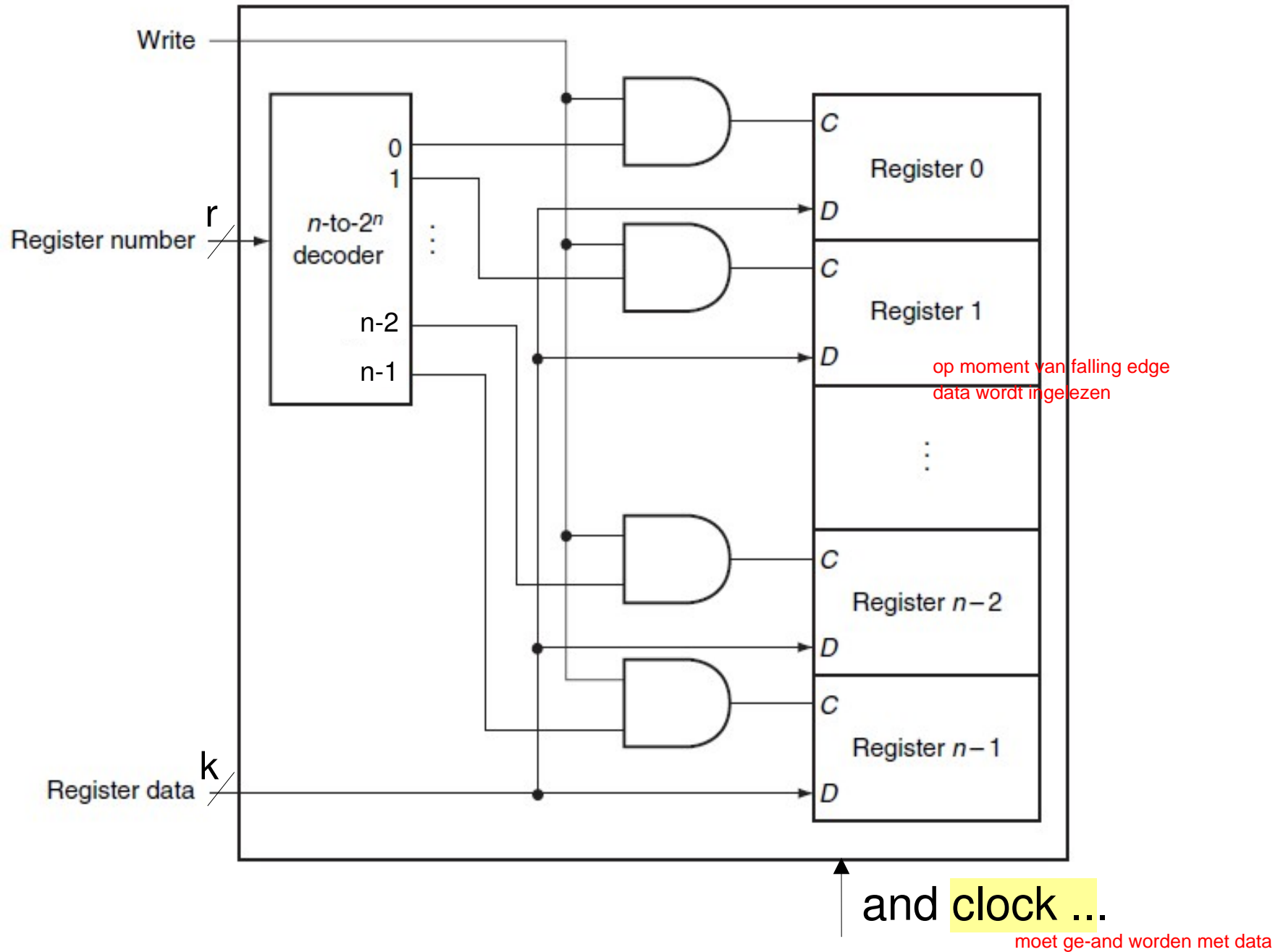


Large Memory:

 Static Random Access Memory (SRAM) vs. Dynamic Random Access Memory (DRAM)



Random Access vs. Sequential Access: access time
RAM vs. ROM (Read Only Memory)

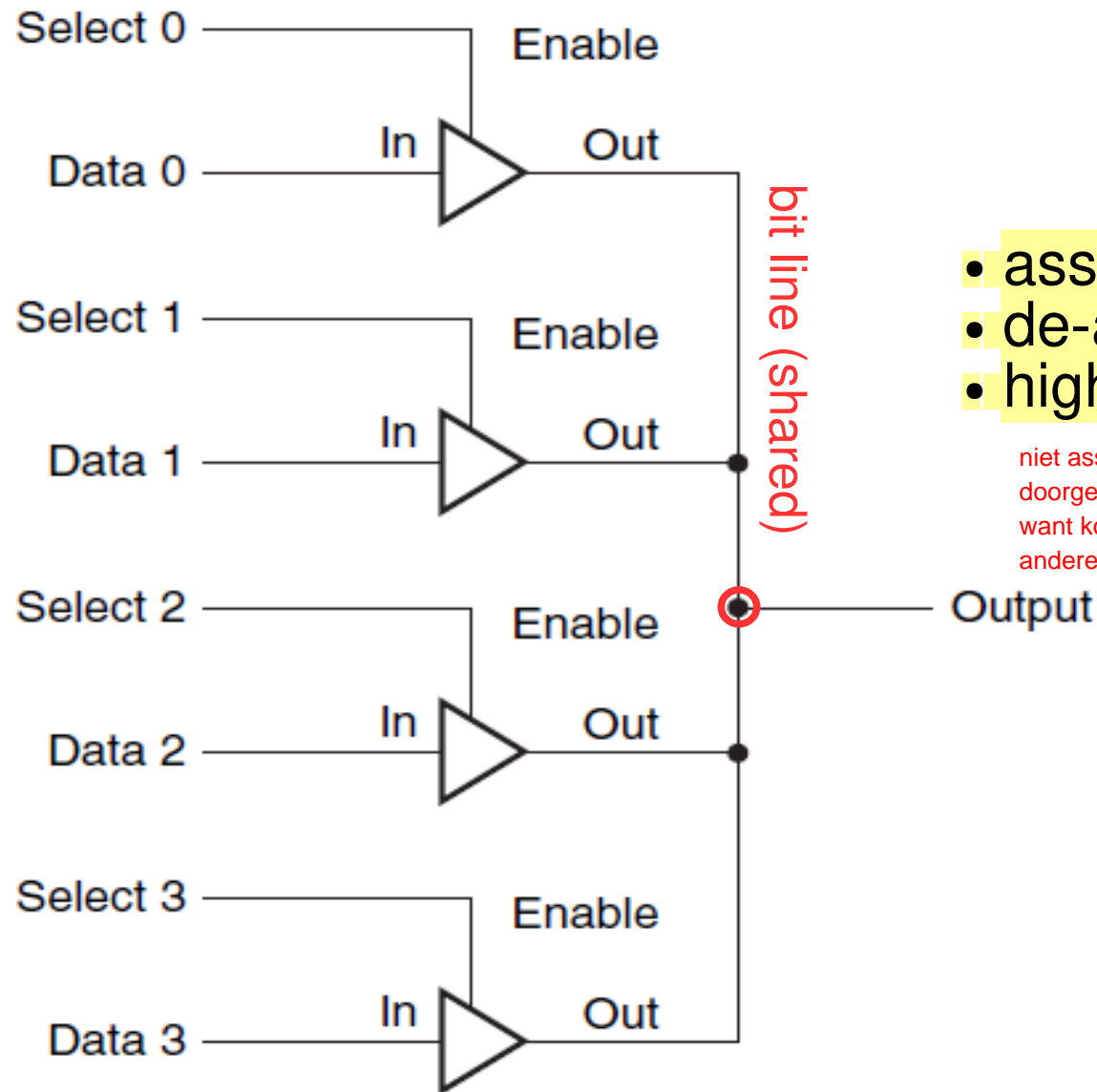Three-state buffers (replace multiplexer)



- asserted
- de-asserted
- high-impedance


niet asserted niet de-asserted, gewoon
doorgelaten
want kortsluiting als het ene 0V is en de
andere 5V

4x2 SRAM

(output enable, chip select omitted)

4 locaties met 2 bits

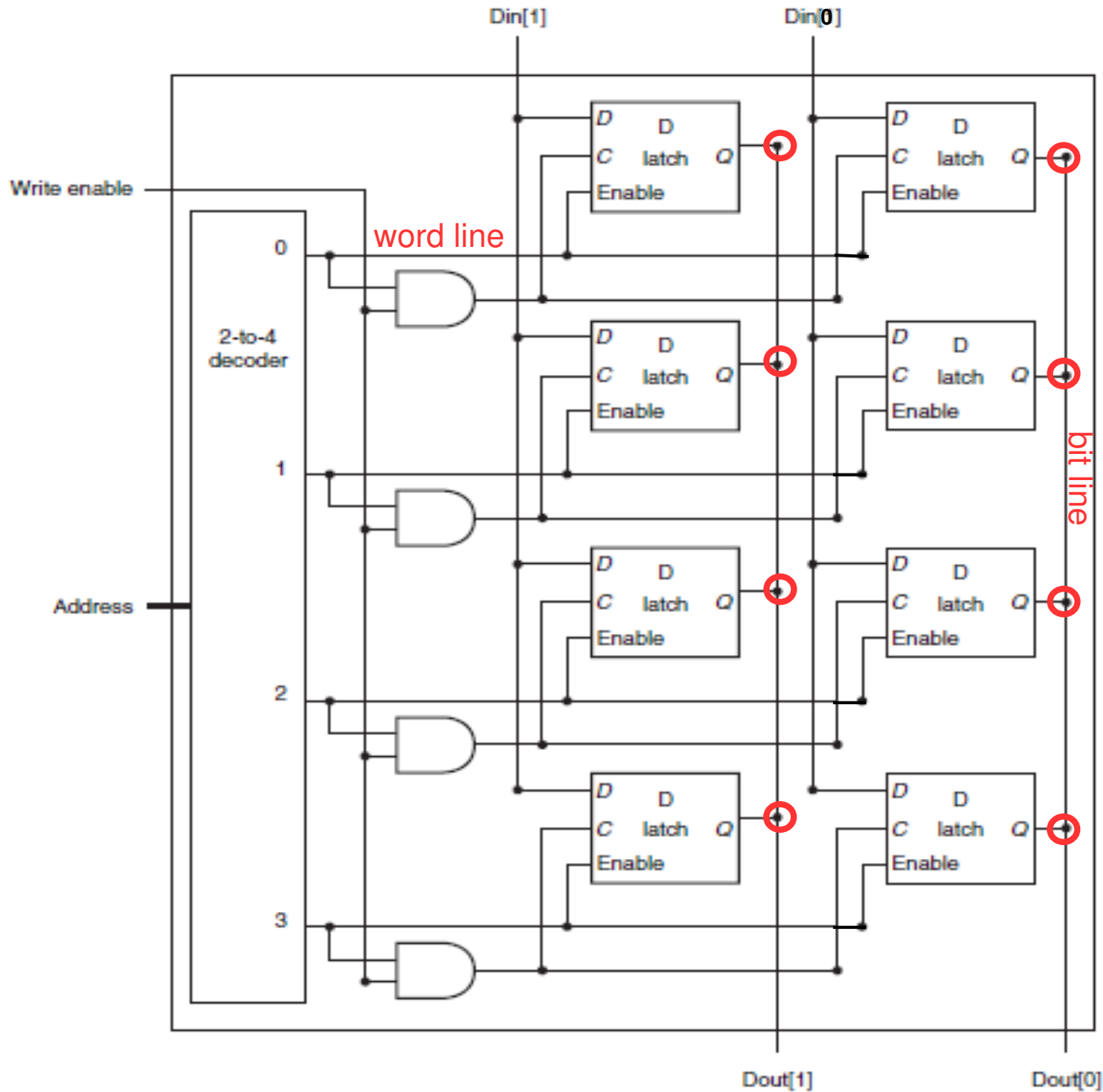multiplexor al weg,
maar wel grote decoder




No large
multiplexer
at output!

SRAM array (read)

4Mx8


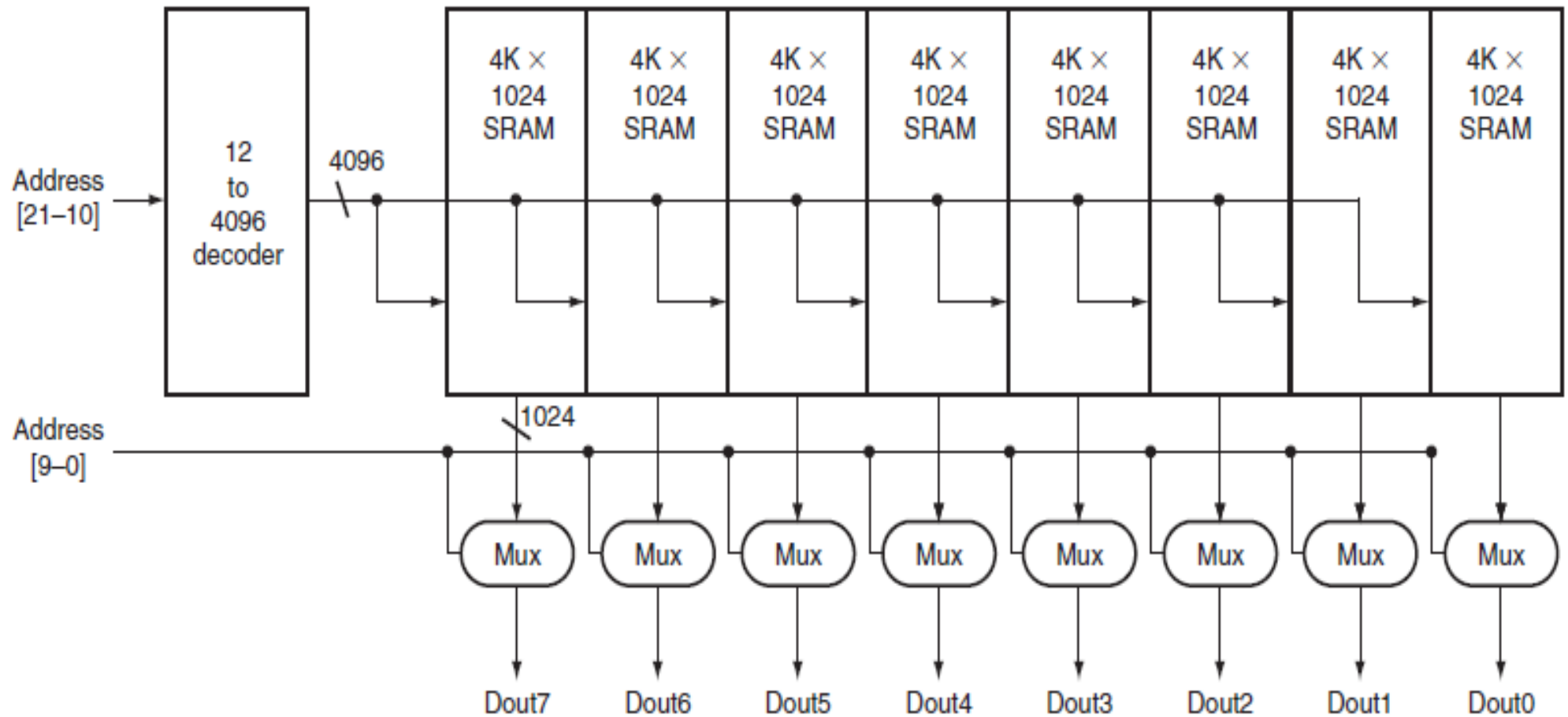
2-level decoding process
to remove need for huge decoder



DRAM: Dynamic, use capacitor instead of flip-flop

store information in capacitor → **volatile**, needs **refresh**

  only 1 transistor per bit (to access data) → denser and cheaper




read/write/refresh

refresh by read and write-back

(rate = **ms**, 64ms row refresh)

DRAM array

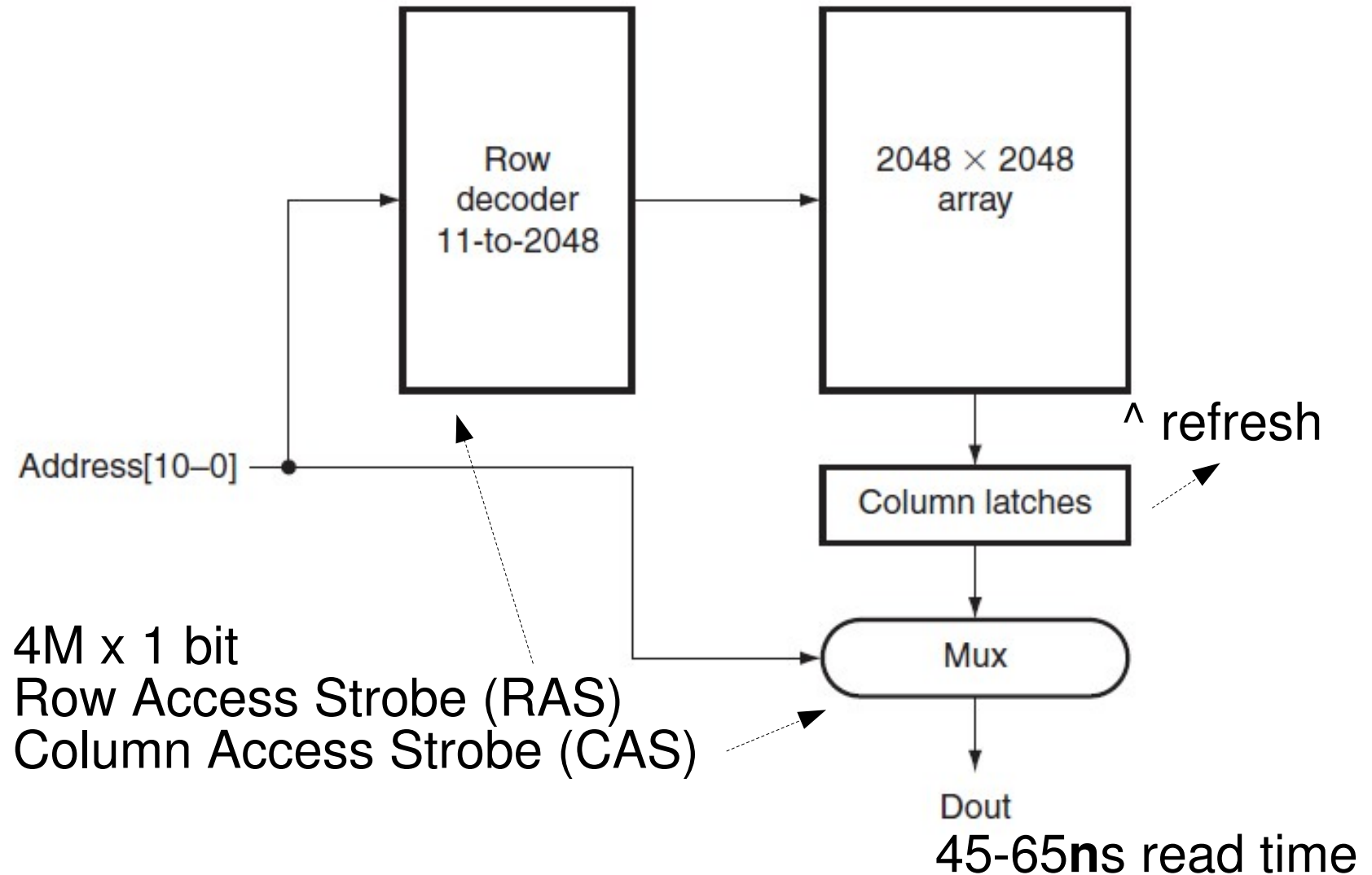


Synchronous RAM (**SSRAM** and **SDRAM**):

“burst” of data from a series of sequential addresses (use **clock**, not address)
Synchronized (on rising clock edge) with datapath

Errors (in information transmission/storage)

 → **encoding/decoding** (hence the name “codec”, e.g., H.264)



Error Detection Code

(in information transmission/storage)

1 bit **parity**: detect 1 bit error
= distance-2 code

even/odd parity

Error Correction Code (ECC)

Data Word	Code bits	Data	Code bits
0000	000	1000	111
0001	011	1001	100
0010	101	1010	010
0011	110	1011	001
0100	110	1100	001
0101	101	1101	010
0110	011	1110	100
0111	000	1111	111

0110 011 with 1 bit data error gives one of :

1110 011, 0010 011, 0100 011, 0111 011


ECCode 011 appears in table for

0110 (**edit distance** 1) ← most likely

0001 (edit distance 3, 2, 2, 2 respectively)

ECC RAM

aka “server class” memory

 


Non-ECC RAM

Finite State Machines (DFA, FSA, FSM)

DETERMINISTIC
DFA
 
$$FSA = \langle S, s_i \in S, T \subseteq S' \times S' \times L, Acc \rangle$$



$$S = \{ s_1, s_2, s_3 \}$$

$$s_1 = s_1$$


$$T = \{ ((s_1, s_2), "a"), ((s_2, s_2), "b"), ((s_2, s_3), "c") \}$$

$$L = \{ "a", "b", "c" \}$$

$$Acc = \{ s_3 \}$$

for "language" recognition

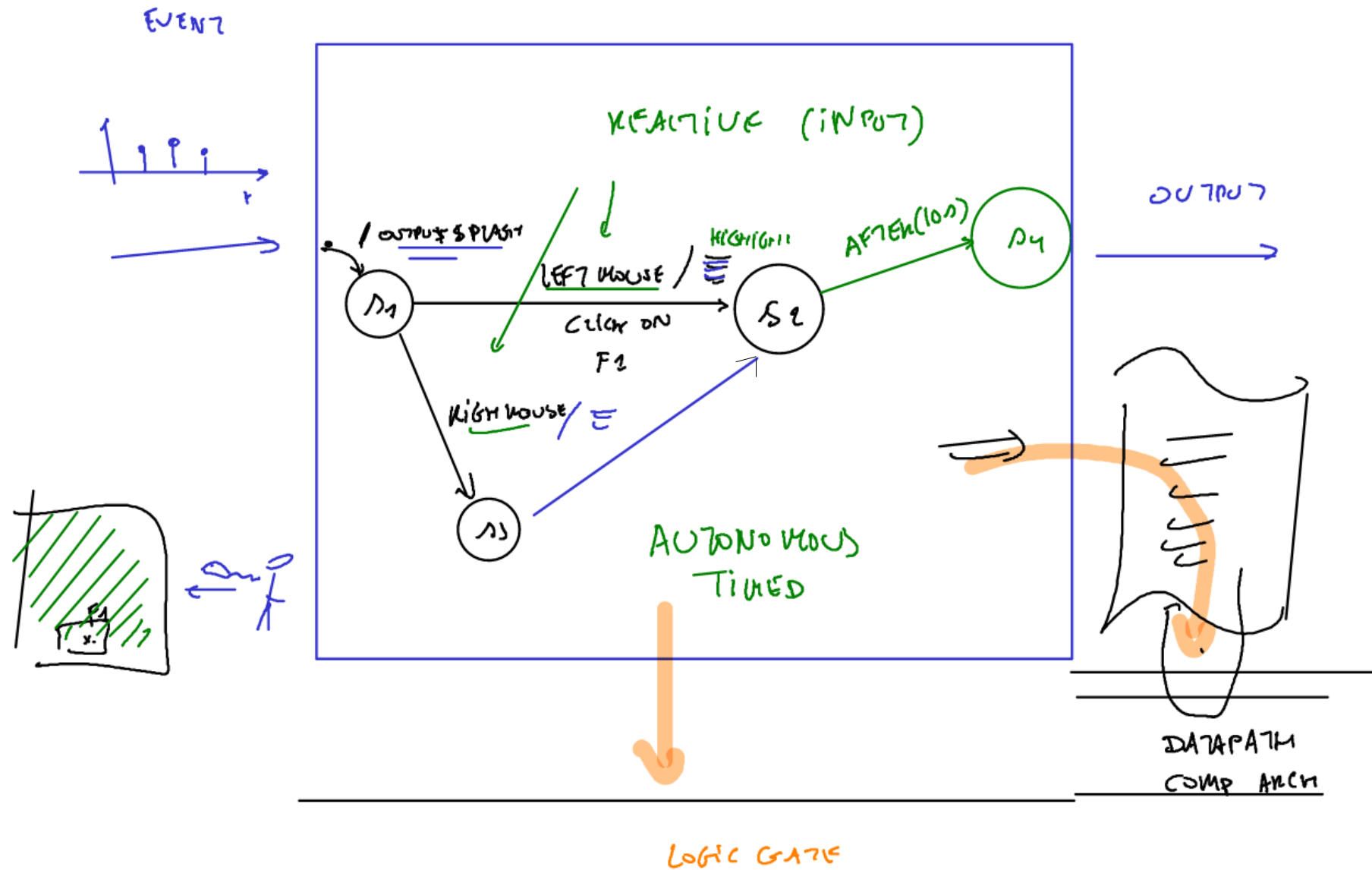Finite State Machines (Discrete Event – DE)



for system (behaviour) specification (and synthesis)


Traffic Light (Discrete-Time – DT)

fairness (in case of conflict)


	Inputs		Next state
	NScar	EWcar	
NSgreen	0	0	NSgreen
NSgreen	0	1	EWgreen
NSgreen	1	0	NSgreen
NSgreen	1	1	EWgreen
EWgreen	0	0	EWgreen
EWgreen	0	1	EWgreen
EWgreen	1	0	NSgreen
EWgreen	1	1	NSgreen

	Outputs	
	NSlite	EWlite
NSgreen	1	0
EWgreen	0	1

Traffic Light

 

Traffic Light

 


encode CurrentState (NSgreen or Ewgreen) in 1 bit

```
NextState = (~CurrentState . EWcar) + (CurrentState . ~NScar)
NSlite     = ~CurrentState
EWlite     = CurrentState
```


... evaluated every clock cycle ... add after(delay) ... ?

Finite State Machines

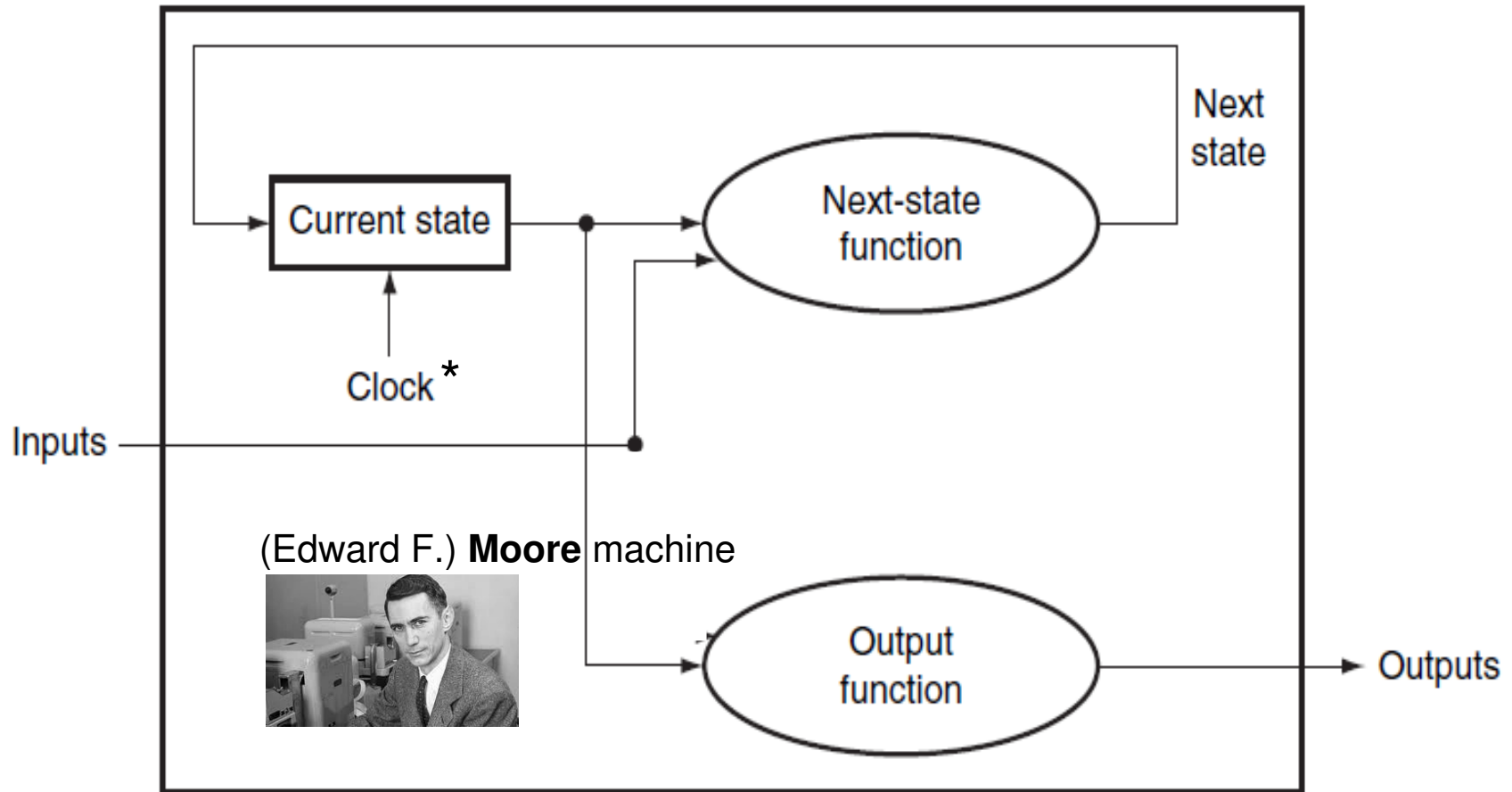

* Discrete-Time (DT) realization (vs. Discrete-Event (DE))

Finite State Machines

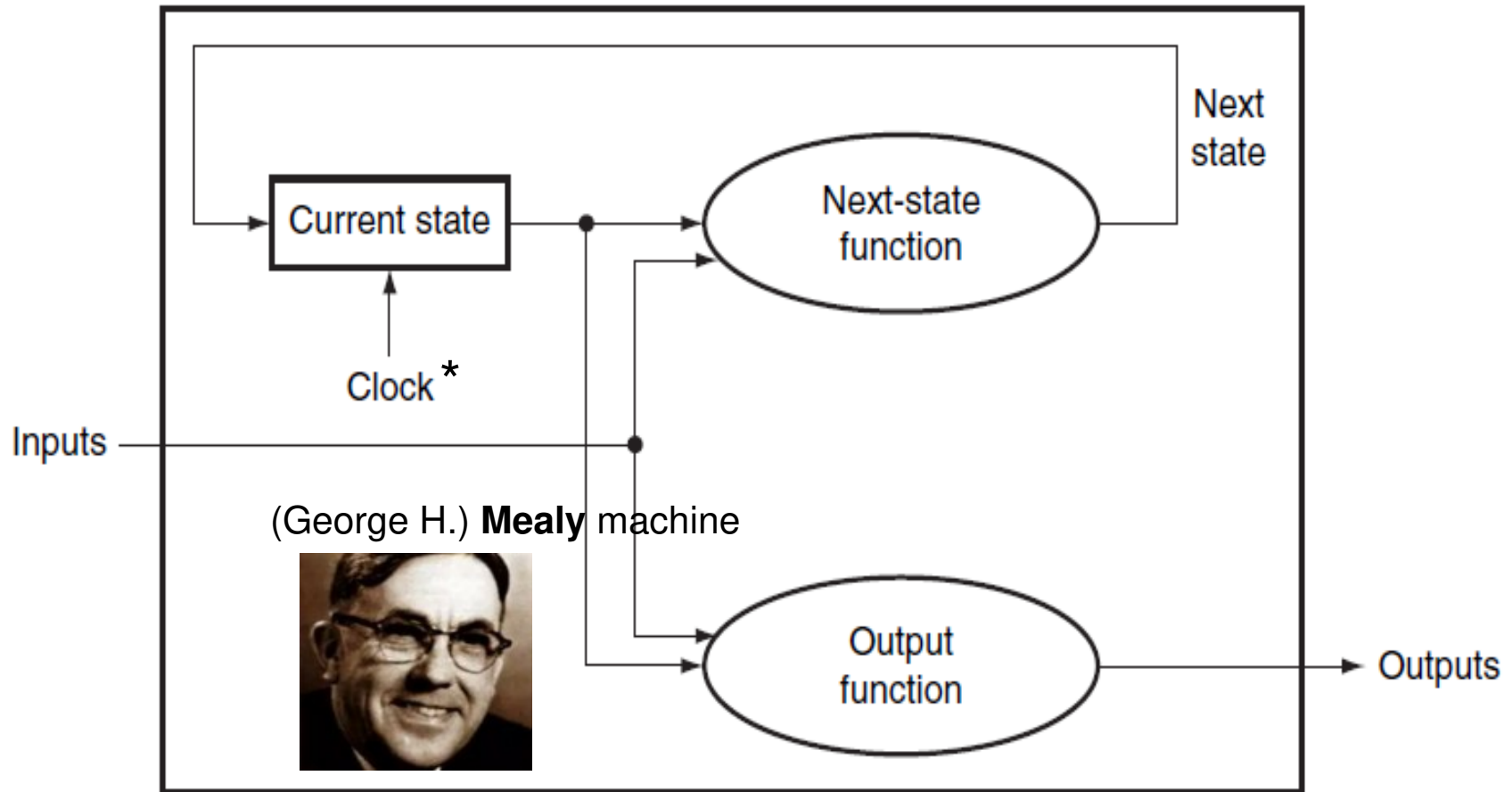

* Discrete-Time (DT) realization (vs. Discrete-Event (DE))

Traffic Light

