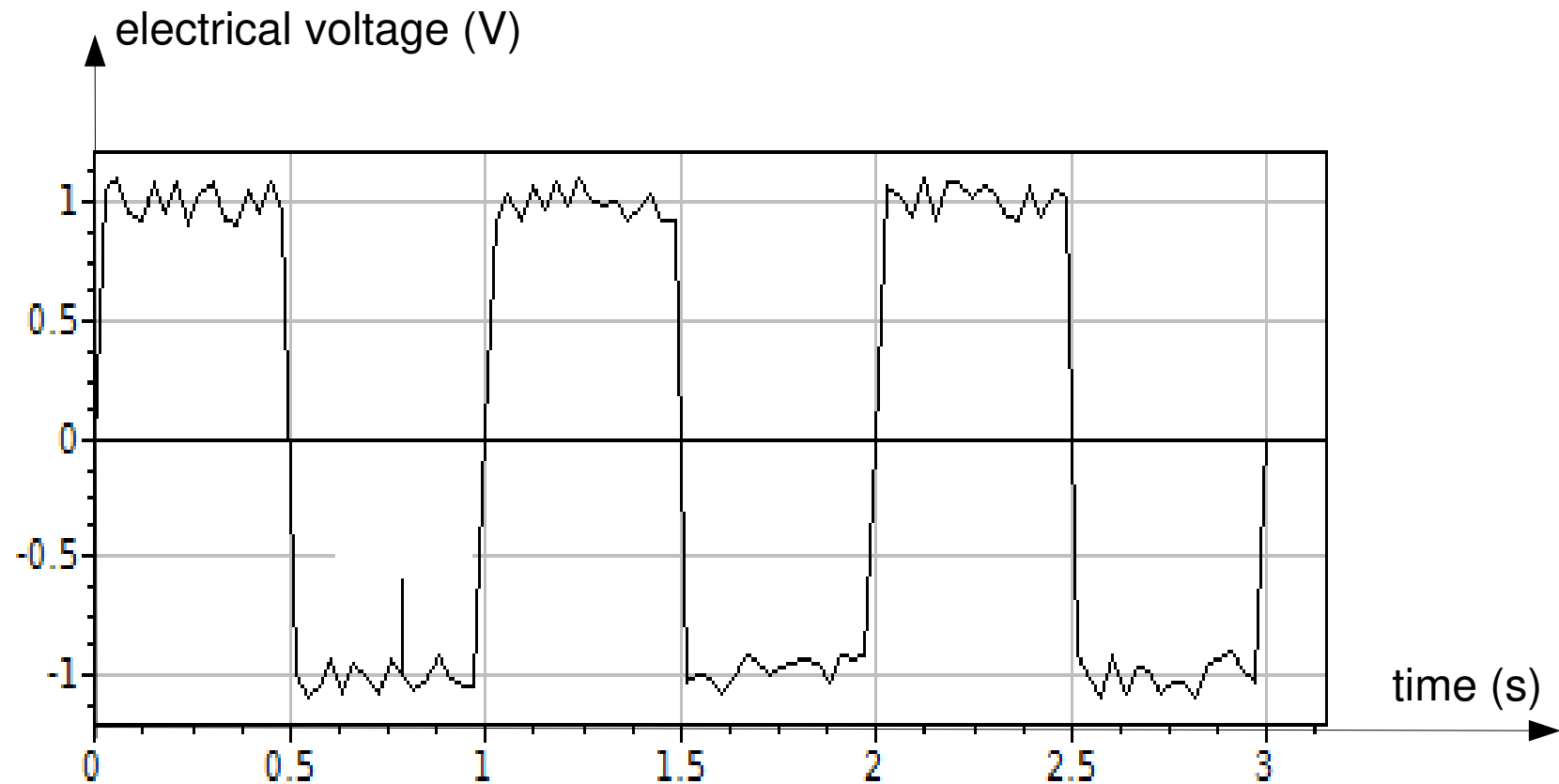



Logic Design: Implementation of functionality by means of “Logic Gates”

(Appendix B of P&H textbook)


from Analog ...



... to Digital

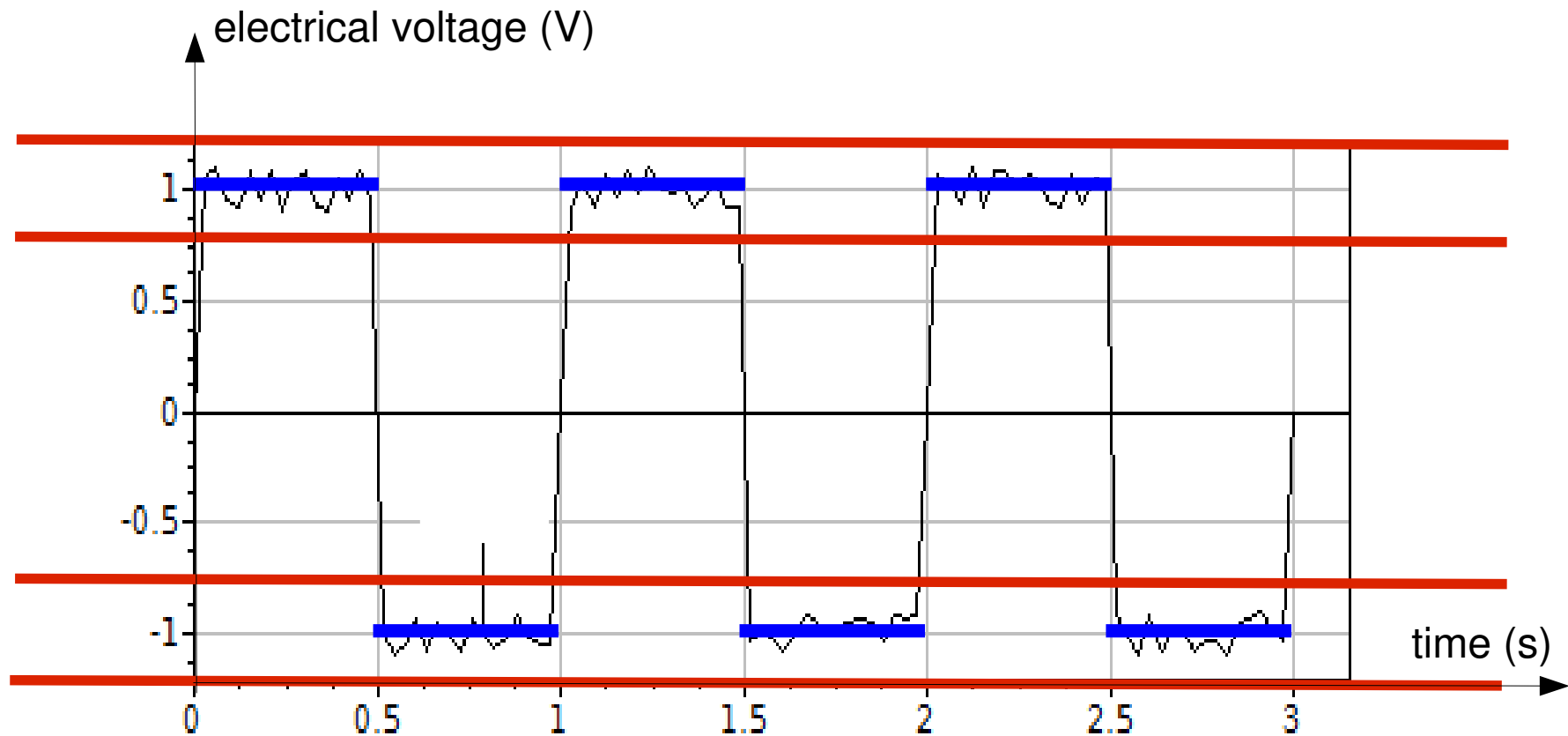


... to Digital

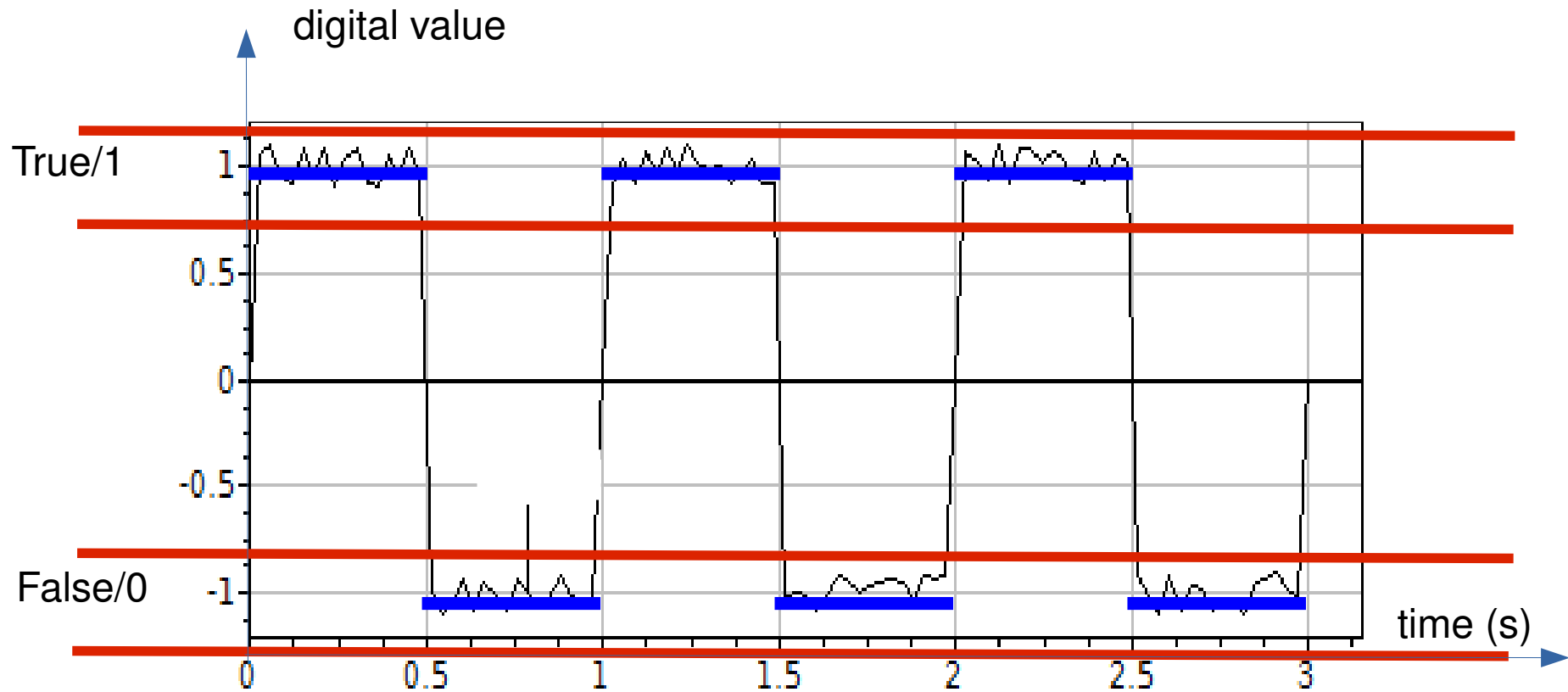

logical 0/1 – Boolean True/False – asserted/de-asserted – high/low

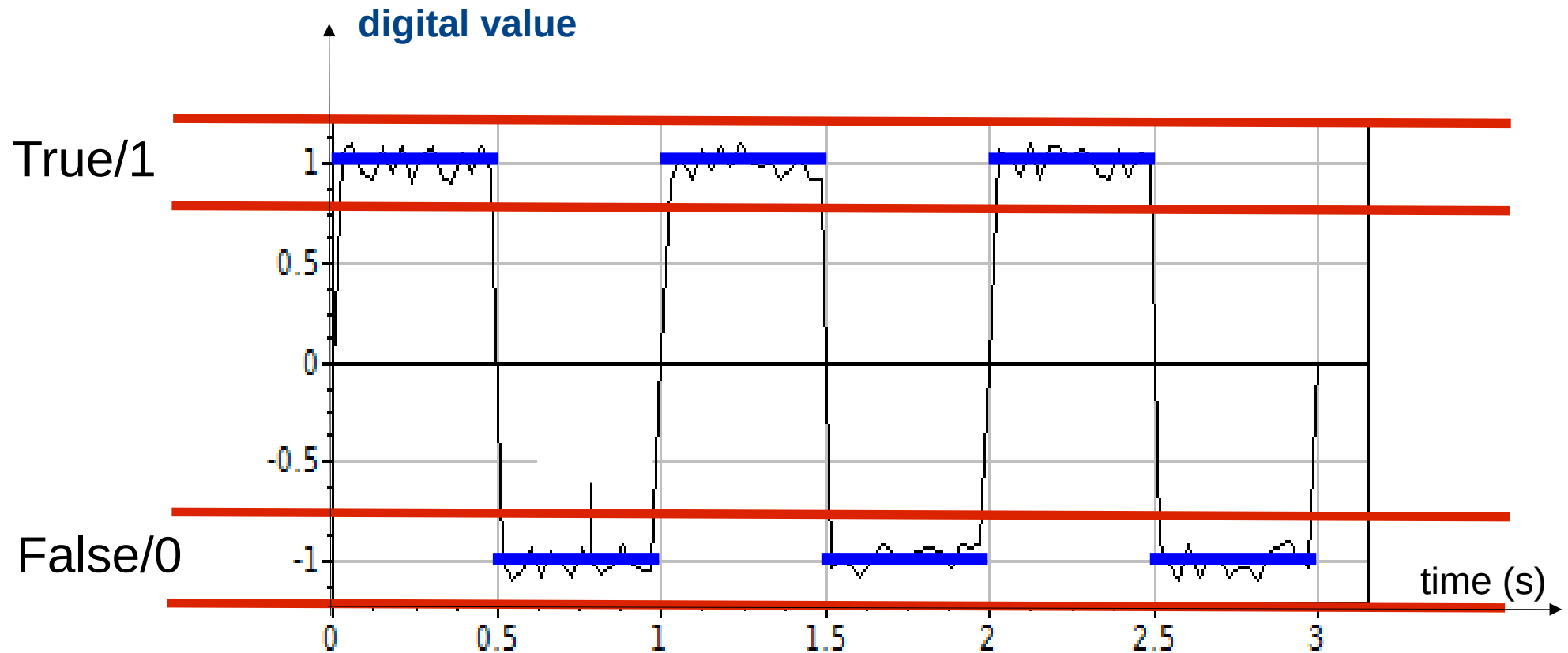
Digital Signals are based on Analog Signals
→ Digital (logic) operations process Analog Signals



logical 0/1 – Boolean True/False – asserted/de-asserted – high/low

Attenuation, Noise, ... : Analog vs. Digital

Analog

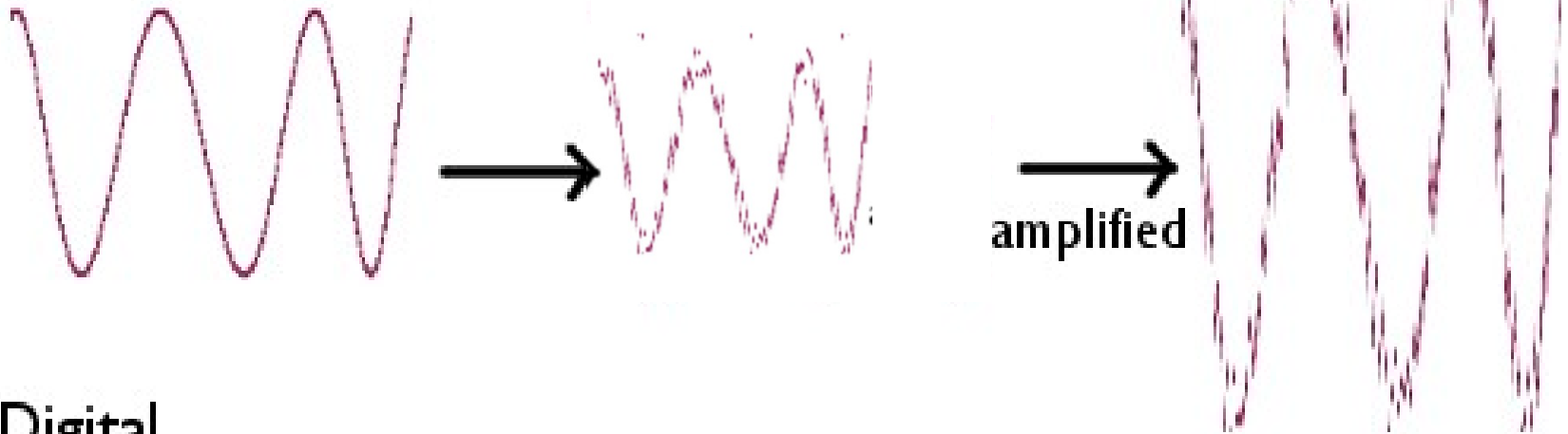

Digital



RS232 (serial communication data transmission)

The **RS-232 standard** defines the **voltage levels** that correspond to **logical one** and **logical zero** levels for the **data transmission** and the **control signal lines**.

Valid signals are either in the range of **+3 to +15 volts** or the range **-3 to -15 volts** with respect to the "Common Ground" (**GND**) pin; consequently, the range between **-3 and +3 volts** is not a valid RS-232 level.

For **data transmission lines** (TxD, RxD, and their secondary channel equivalents), **logic one** is represented as a **negative voltage** and the signal condition is called "mark". **Logic zero** is signaled with a **positive voltage** and the signal condition is termed "space".

Control signals have the opposite polarity: the asserted or active state is positive voltage and the de-asserted or inactive state is negative voltage. Examples of control lines include request to send (RTS), clear to send (CTS), data terminal ready (DTR), and data set ready (DSR).





<https://en.wikipedia.org/wiki/RS-232>

RS232 (serial communication data transmission)


ASCII Char	Hex	Bin	ASCII Char	Hex	Bin		
65	A	41	0100 0001	97	a	61	0110 0001
66	B	42	0100 0010	98	b	62	0110 0010
67	C	43	0100 0011	99	c	63	0110 0011
68	D	44	0100 0100	100	d	64	0110 0100
69	E	45	0100 0101	101	e	65	0110 0101
70	F	46	0100 0110	102	f	66	0110 0110
71	G	47	0100 0111	103	g	67	0110 0111
72	H	48	0100 1000	104	h	68	0110 1000
73	I	49	0100 1001	105	i	69	0110 1001
74	J	4A	0100 1010	106	j	6A	0110 1010
75	K	4B	0100 1011	107	k	6B	0110 1011
76	L	4C	0100 1100	108	l	6C	0110 1100
77	M	4D	0100 1101	109	m	6D	0110 1101
78	N	4E	0100 1110	110	n	6E	0110 1110
79	O	4F	0100 1111	111	o	6F	0110 1111
80	P	50	0101 0000	112	p	70	0111 0000
81	Q	51	0101 0001	113	q	71	0111 0001
82	R	52	0101 0010	114	r	72	0111 0010
83	S	53	0101 0011	115	s	73	0111 0011
84	T	54	0101 0100	116	t	74	0111 0100
85	U	55	0101 0101	117	u	75	0111 0101
86	V	56	0101 0110	118	v	76	0111 0110
87	W	57	0101 0111	119	w	77	0111 0111
88	X	58	0101 1000	120	x	78	0111 1000
89	Y	59	0101 1001	121	y	79	0111 1001
90	Z	5A	0101 1010	122	z	7A	0111 1010

<linuxhint/>

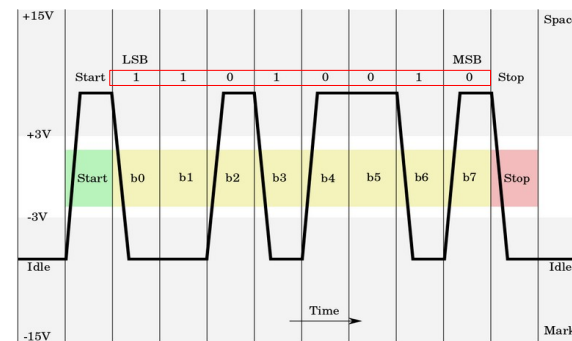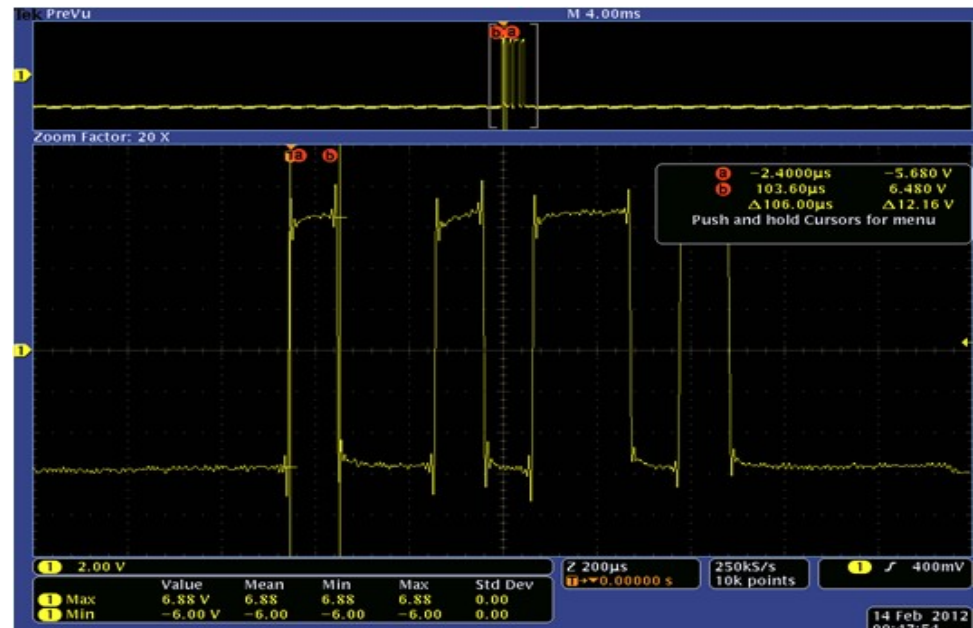


<https://en.wikipedia.org/wiki/RS-232>

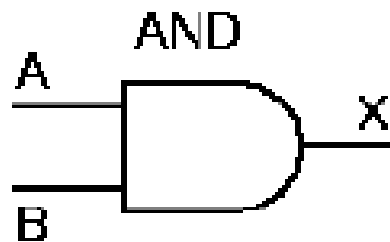
Universal Basis of **all** Digital Hardware: Logic Gates



A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

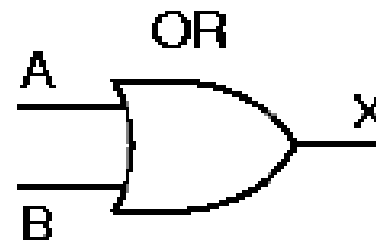

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

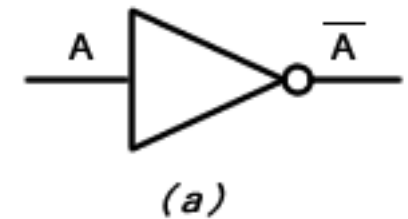

A	\overline{A}
0	1
1	0

Different commonly used notations

A AND B

$A \cdot B$

$A \wedge B$

$\&\&$

$\&\&$

$\&\&$

and

A OR B

$A + B$

$A \vee B$

$\|\|$

$\|\|$

$\|\|$

or

NOT A

\overline{A}

$\neg A$

!

!

!

not

C/C++

JAVA

JAVASCRIPT



PYTHON

MATH.


LOGIC

PROG. LANG.

Logic Gates

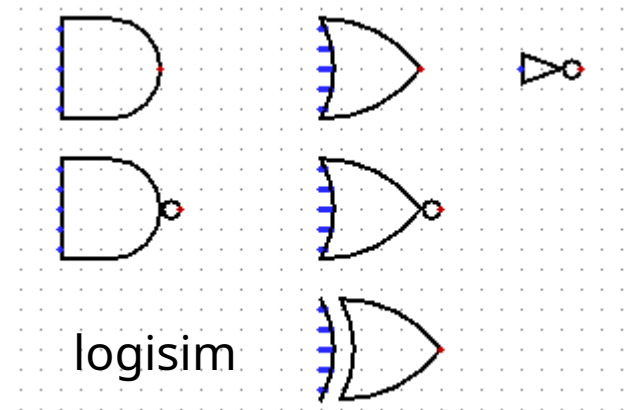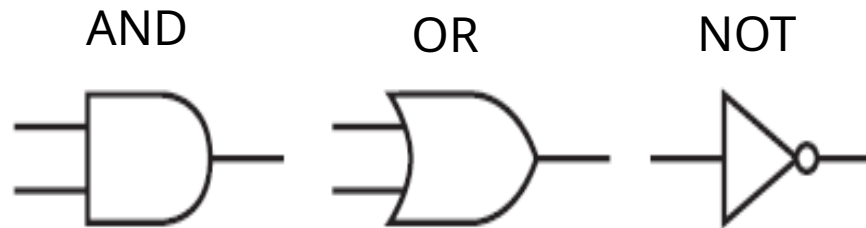


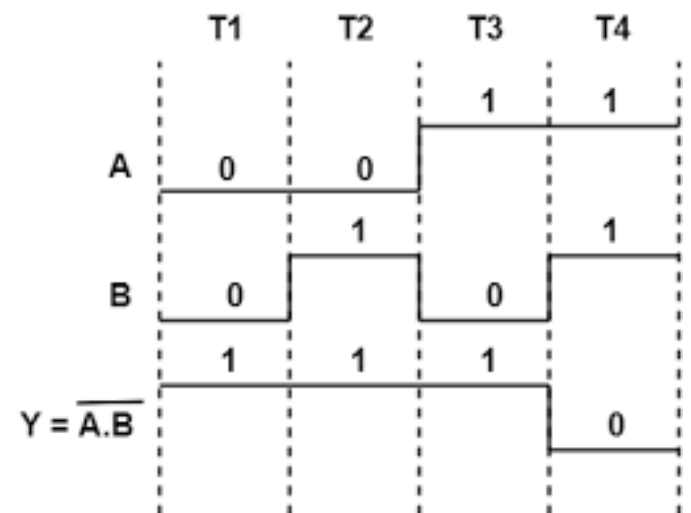Shorthand notation for combinations including NOT




Note: operate on digital time-varying **signals**!

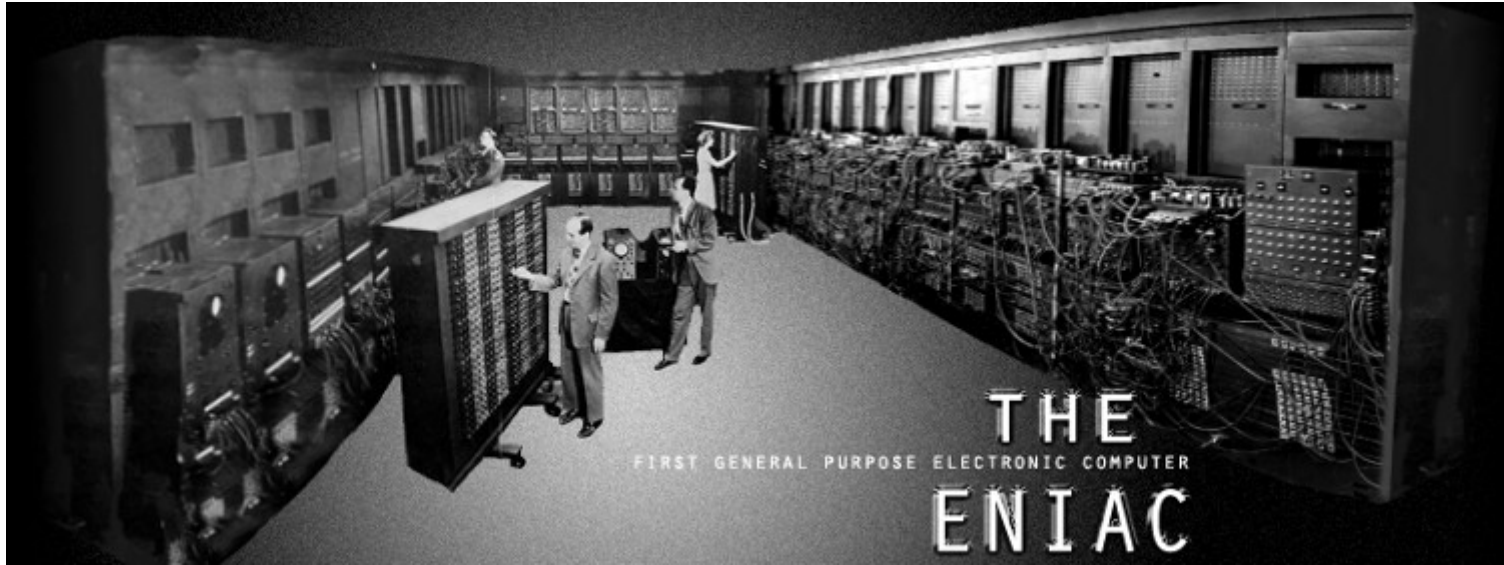Implementing **Digital** (Logic) Components using **Analog** Electrical Components




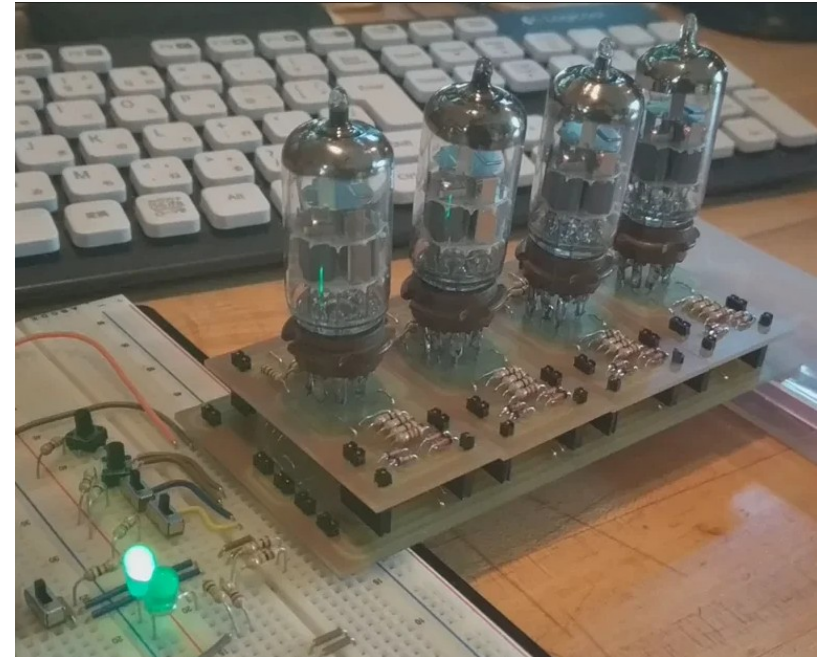“Electronic Numerical Integrator And Computer”




Implementing **Digital** (Logic) Components using **Analog** Electrical Components

AND

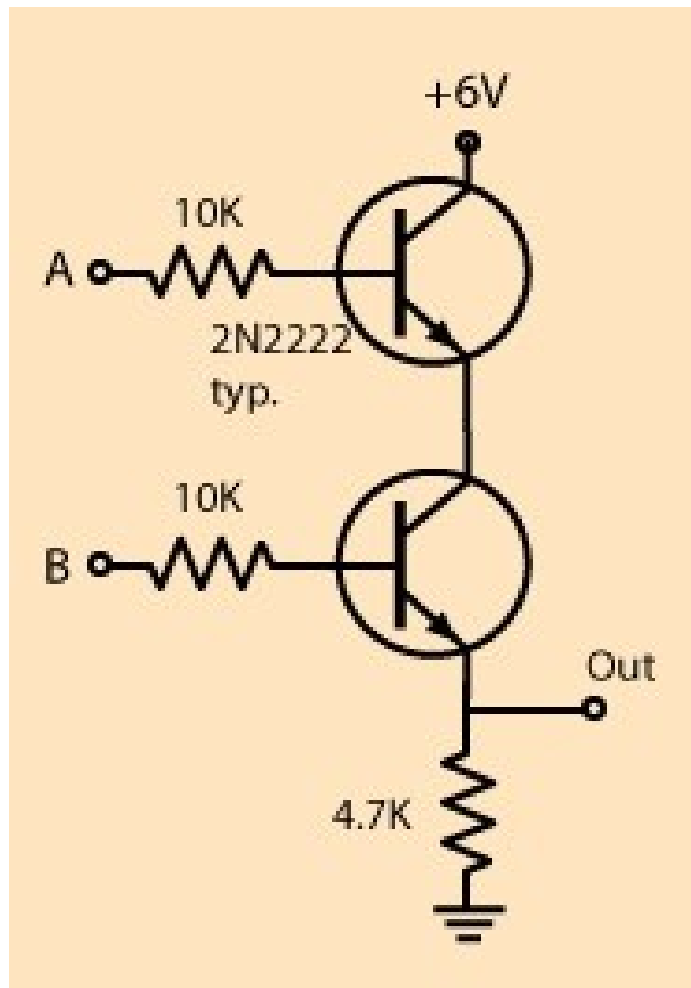


resistor

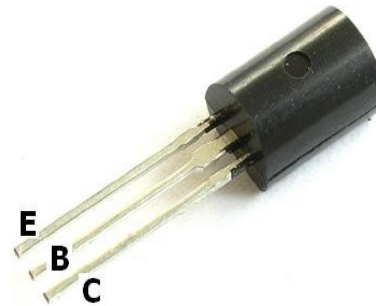

transistor

Used to amplify electrical signals.
When used "in saturation"
acts as a switch.





OR

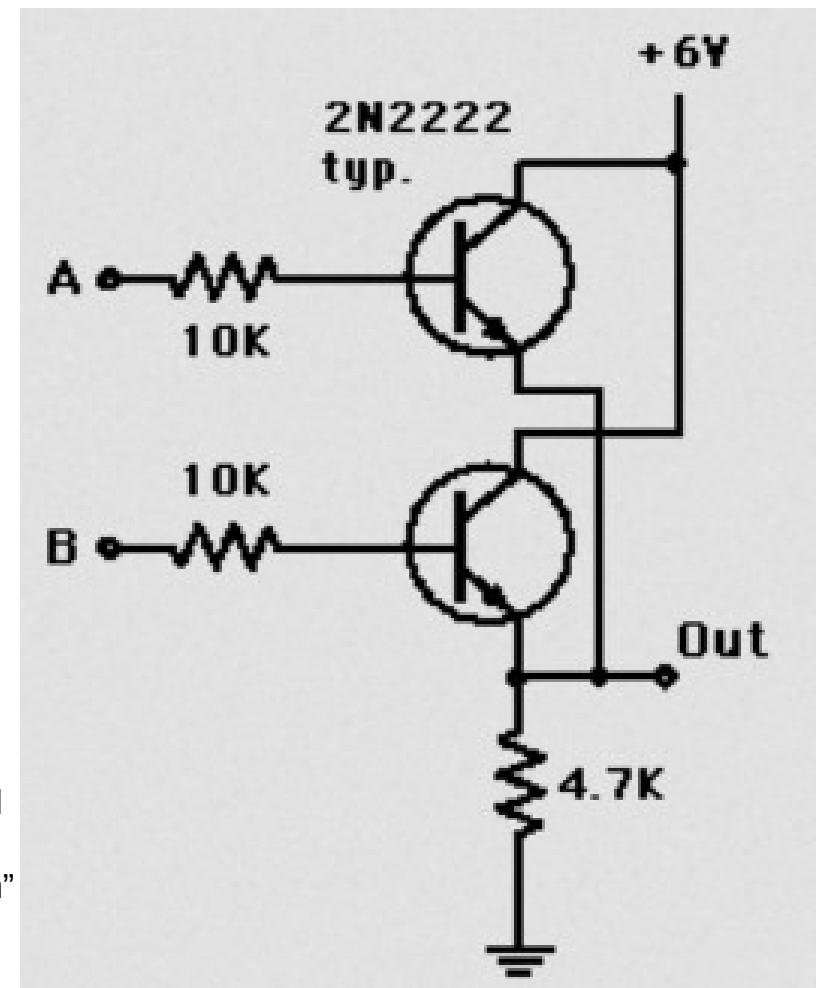

physical (analog) view

= zeer klein getal => voor

SMALL PROPAGATION DELAY
⇒

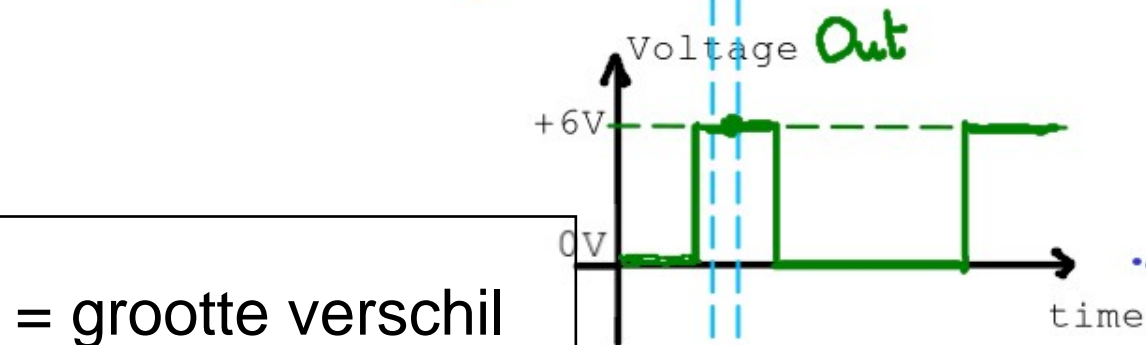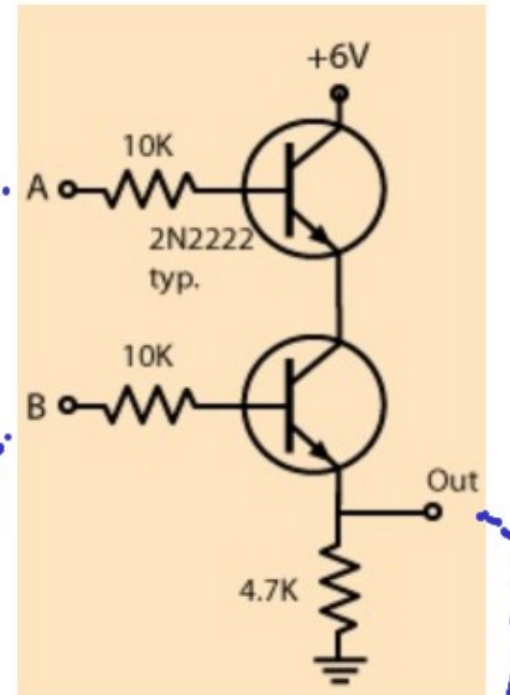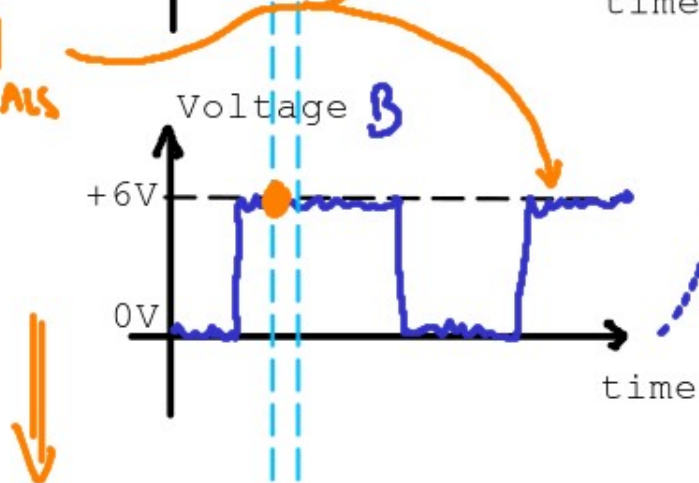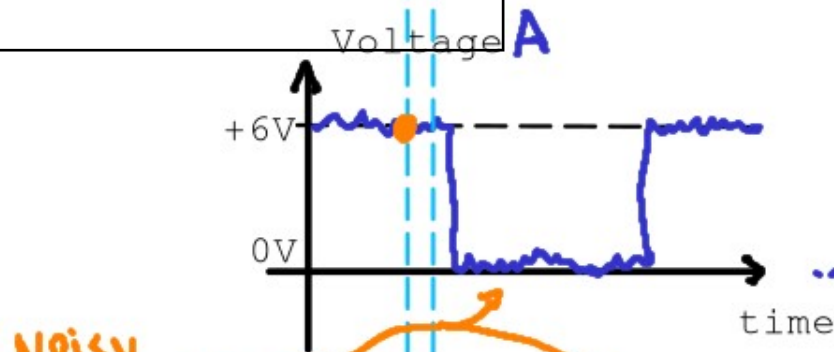

= grootte verschil

SMALL PROPAGATION DELAY


logical (digital) view (idealized)

INSTANTANEOUS
TRANSITIONS


ϕ PROPAGATION DELAY
 \Rightarrow



time

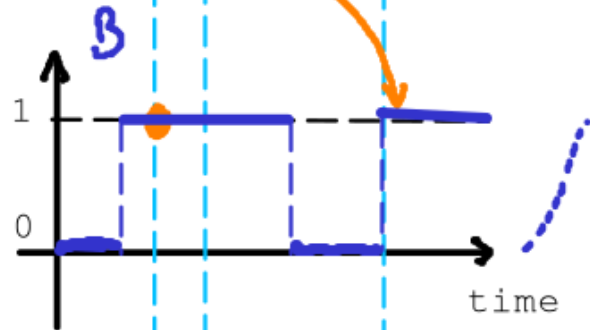

time

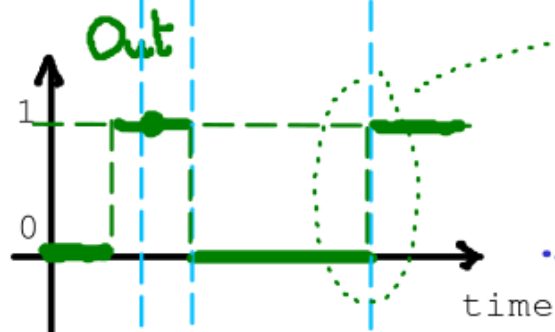

time

ϕ PROPAGATION DELAY



abstraction:
should still be
a function
(unique value)

gesloten bolletje: echte waarde
open bolletje: niet



NOISELESS
SIGNALS



Implementing Logic Components:

SN 7400N with 4 NAND gates (~ 8 transistors)

jaren '70

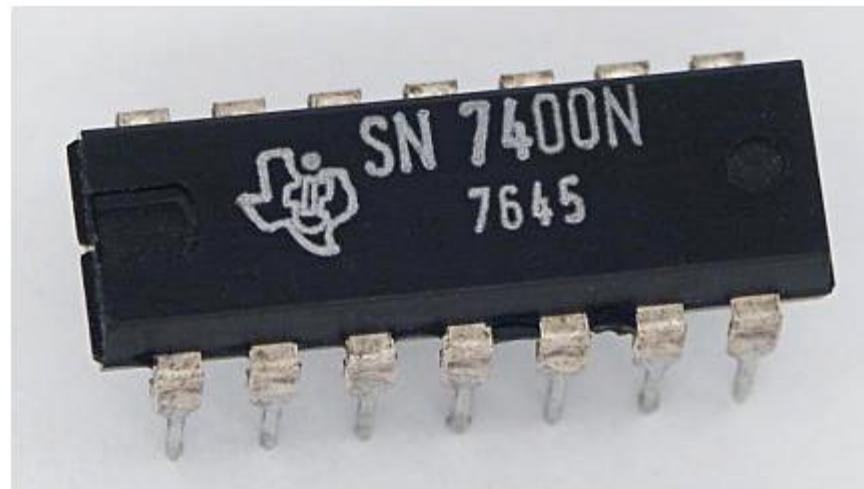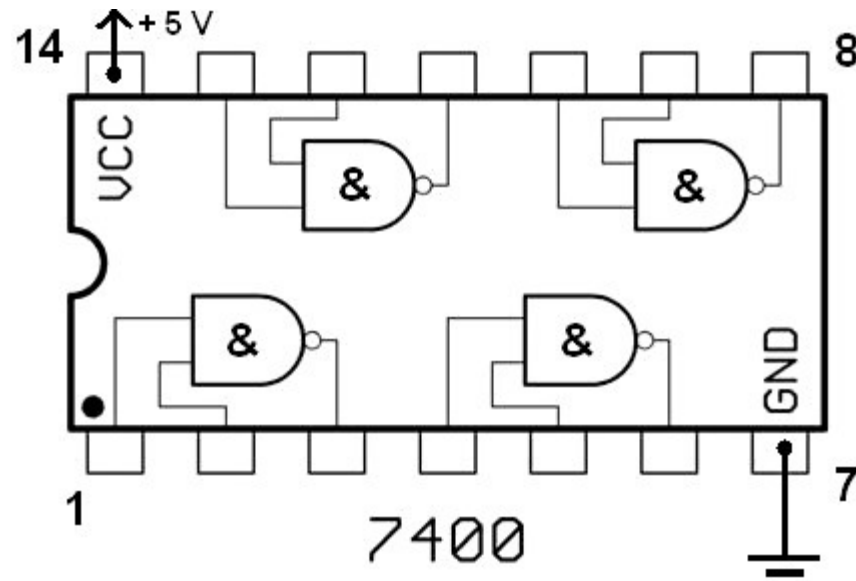


manufactured in the 45th week of 1976

Implementing Logic Components:

jaren '90

32 bit MIPS R3000 processor (115000 transistors)

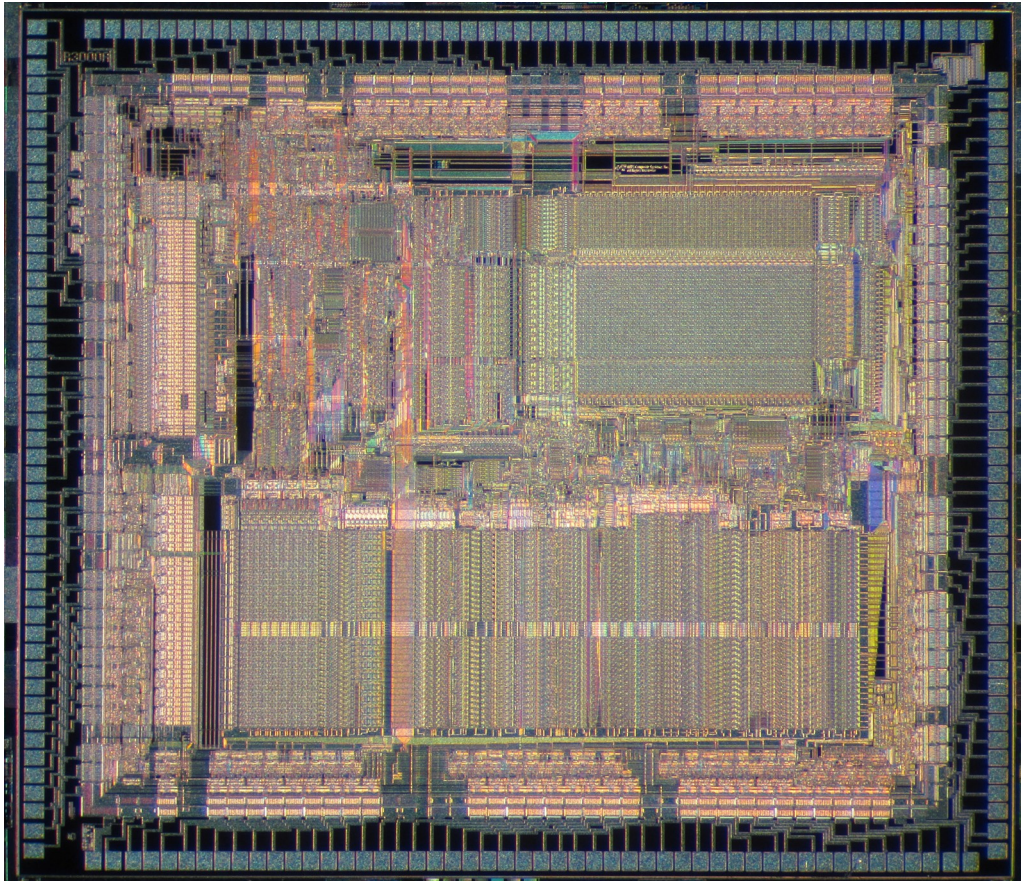

early 1990s



www.cpu-world.com

ééns te veel transistors ==> meerdere cores ==> parallel werken

<https://www.mips.com/blog/five-most-iconic-devices-to-use-mips-cpus/>



transistor count ~ computing/memory power
→ **exponential growth** in computing/memory power


CPU Transistor Counts 1971-2008 & Moore's Law

anders veel te steile grafiek

Logarithmic scale!

Transistor count ~ ...

vanaf hier multiple cores

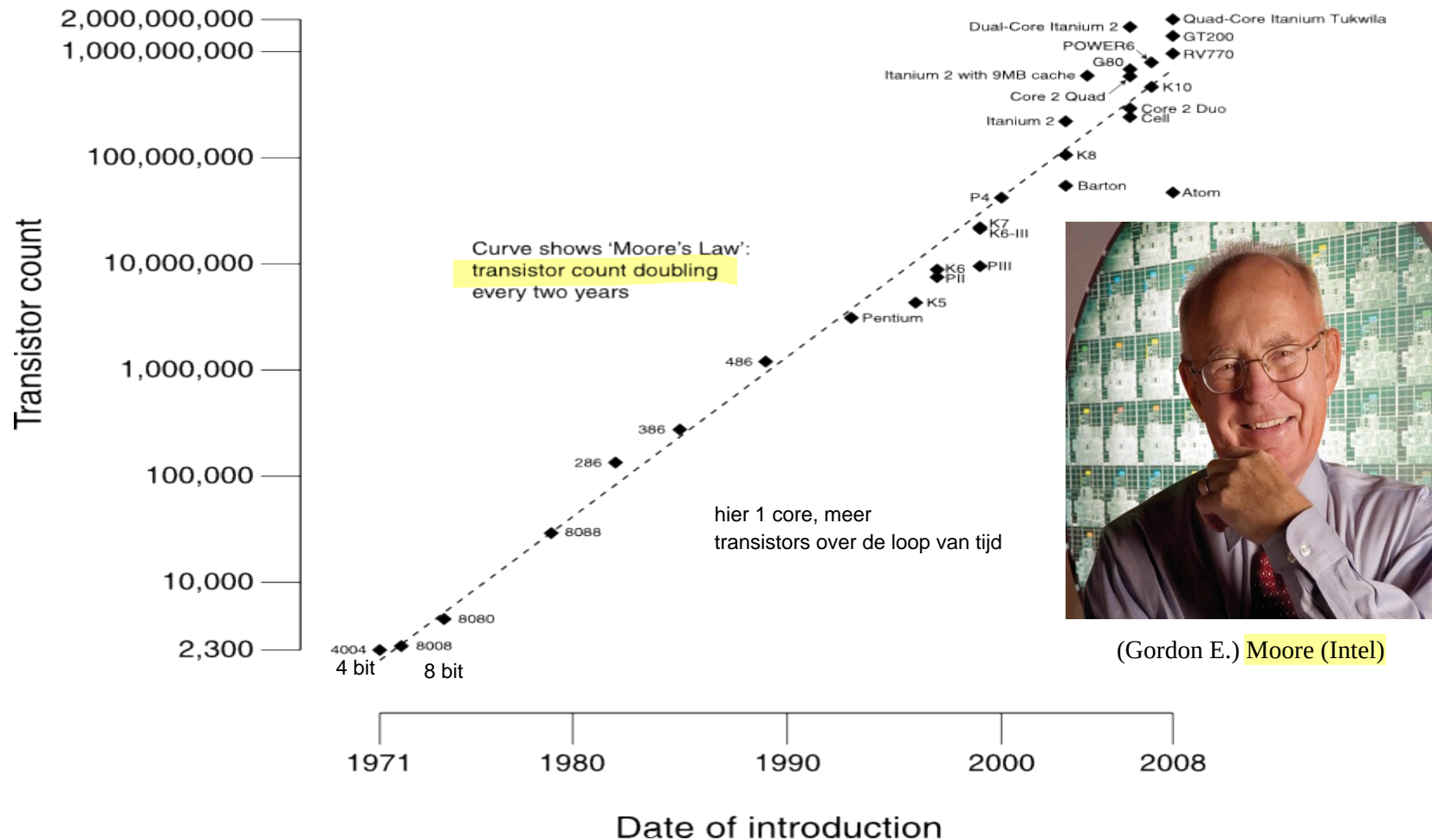

hij zei: voor dez prijs & zelfde grootte ==> 2x zoveel transistors

Types of circuits:

- “**combinational**” logic/circuit:
implements a **function** (input \rightarrow output)
- “**sequential**” logic/circuit: implements **memory**

A)

$f(a1, a2)$
 $= a1 \text{ AND } a2 \quad \text{=== voor alle } a1, a2 \text{ als element van } \{\text{TRUE}, \text{FALSE}\}$

$f(\text{TRUE}, \text{TRUE}) = \text{TRUE}$

B)

a1	a2	f(a1, a2)
FALSE	FALSE	FFFT
FALSE	TRUE	
TRUE	FALSE	
TRUE	TRUE	

Specifying (modelling) combinational logic:


“truth table”

Inputs			Outputs		
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

Implements a “total” function →
how many table rows for N inputs?

N inputs --> #COMBINATIES = 2^N

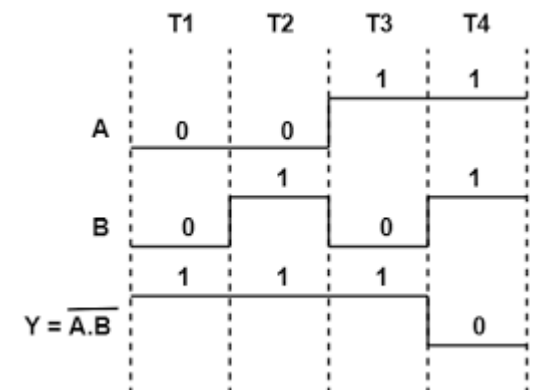Note: these are (digital) “**signals**” !



Specifying (modelling) combinational logic:

Logic (Boolean) formula:

$(out1, out2) = f(in1, in2, in3)$ where


- $out1 = (in1 \text{ AND } in2) \text{ OR } in3$
- $out2 = \text{NOT } (in2 \text{ OR } in3)$

Derived truth table representation of f:

in1	in2	in3	out1	out2
0	0	0	0	1
0	0	1	1	0
0	1	0	0	0
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Boolean algebra: AND (.), OR (+), NOT (-)


- Identity law: $A + 0 = A$ and $A \cdot 1 = A$.
- Zero and One laws: $A + 1 = 1$ and $A \cdot 0 = 0$.
- Inverse laws: $A + \bar{A} = 1$ and $A \cdot \bar{A} = 0$
- Commutative laws: $A + B = B + A$ and $A \cdot B = B \cdot A$.
- Associative laws: $A + (B + C) = (A + B) + C$ and $A \cdot (B \cdot C) = (A \cdot B) \cdot C$.
- Distributive laws: $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$ and $A + (B \cdot C) = (A + B) \cdot (A + C)$.

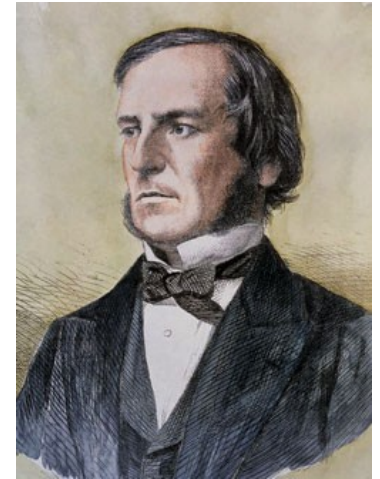

George Boole
(1815 - 1864)

De Morgan's laws:

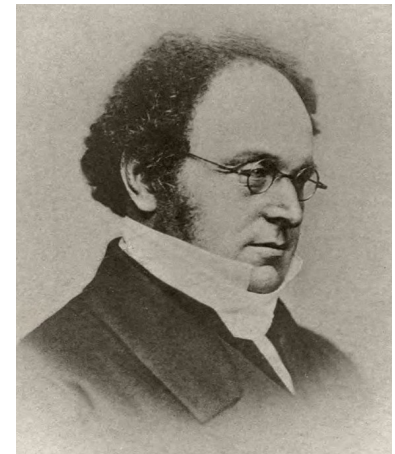- $\overline{A + B} = \bar{A} \cdot \bar{B}$
- $\overline{A \cdot B} = \bar{A} + \bar{B}$



Augustus De Morgan
(1806-1871)



Associativity



aanneemen maar 2 transistors in OR gate
want 1 gate = *2 transistors

VRAAG EX:
#GATES & DELAY
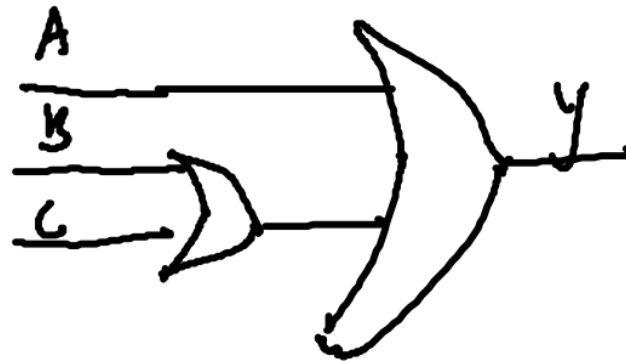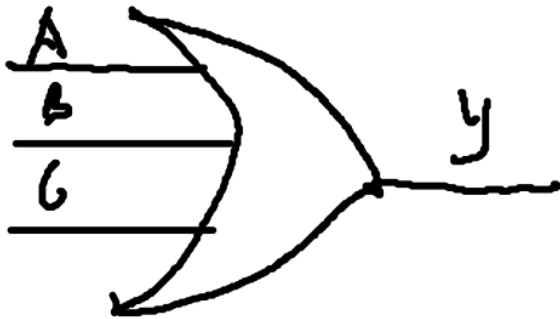
$$y = A + B + C = A + (B + C) = (A + B) + C$$



“truth table”

Inputs			Outputs		
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

Compact representation as Logic Formulae?

“Sum of Products” (1 outputs) or

“Product of Sums” (0 outputs)


(see lab sessions)

Sum of Products


Inputs			Output
A	B	C	D
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$D = (\bar{A} \cdot \bar{B} \cdot C) + (\bar{A} \cdot B \cdot \bar{C}) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot B \cdot C)$$

Programmable Logic Array (PLA)

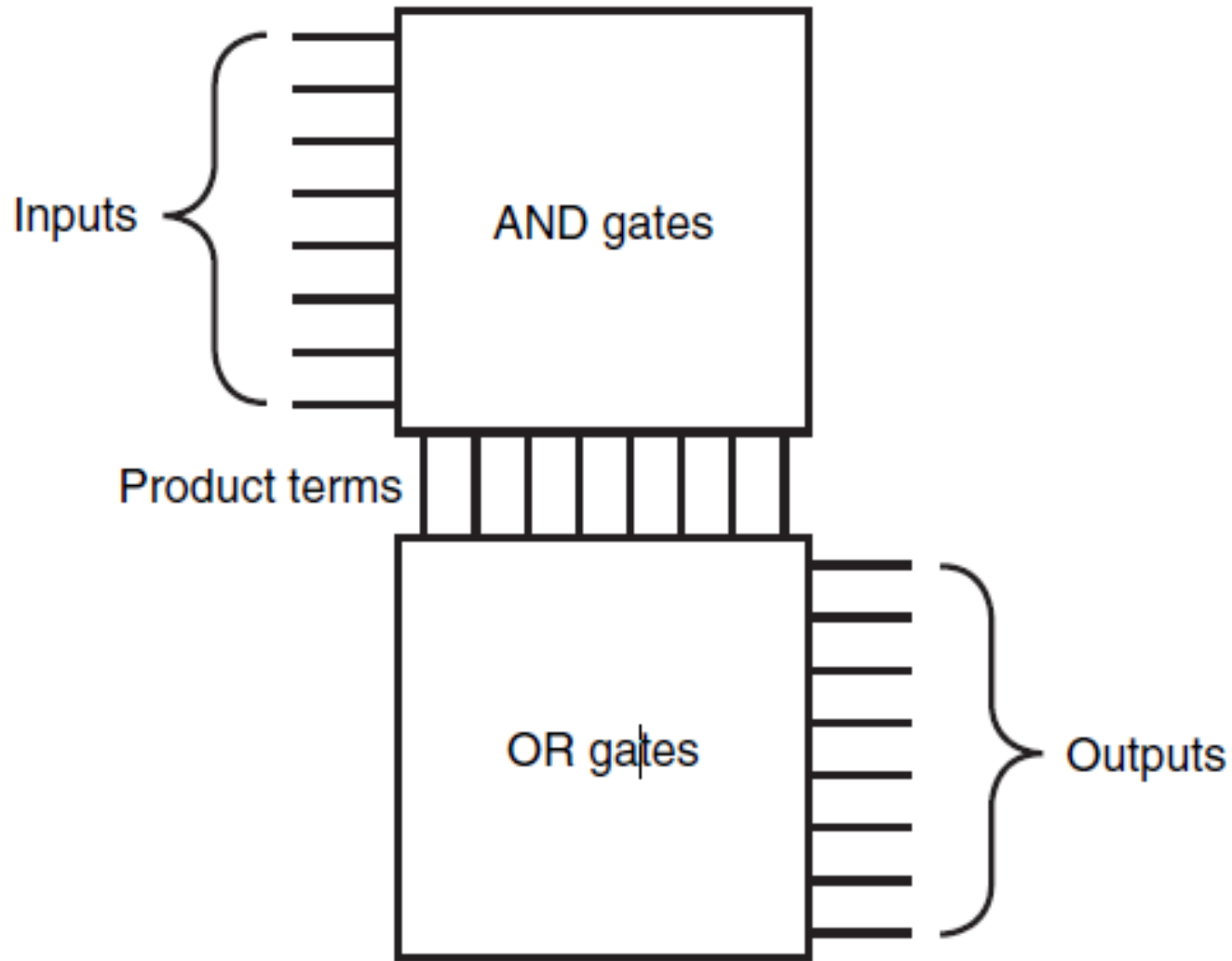

Programmable Logic Array (PLA)

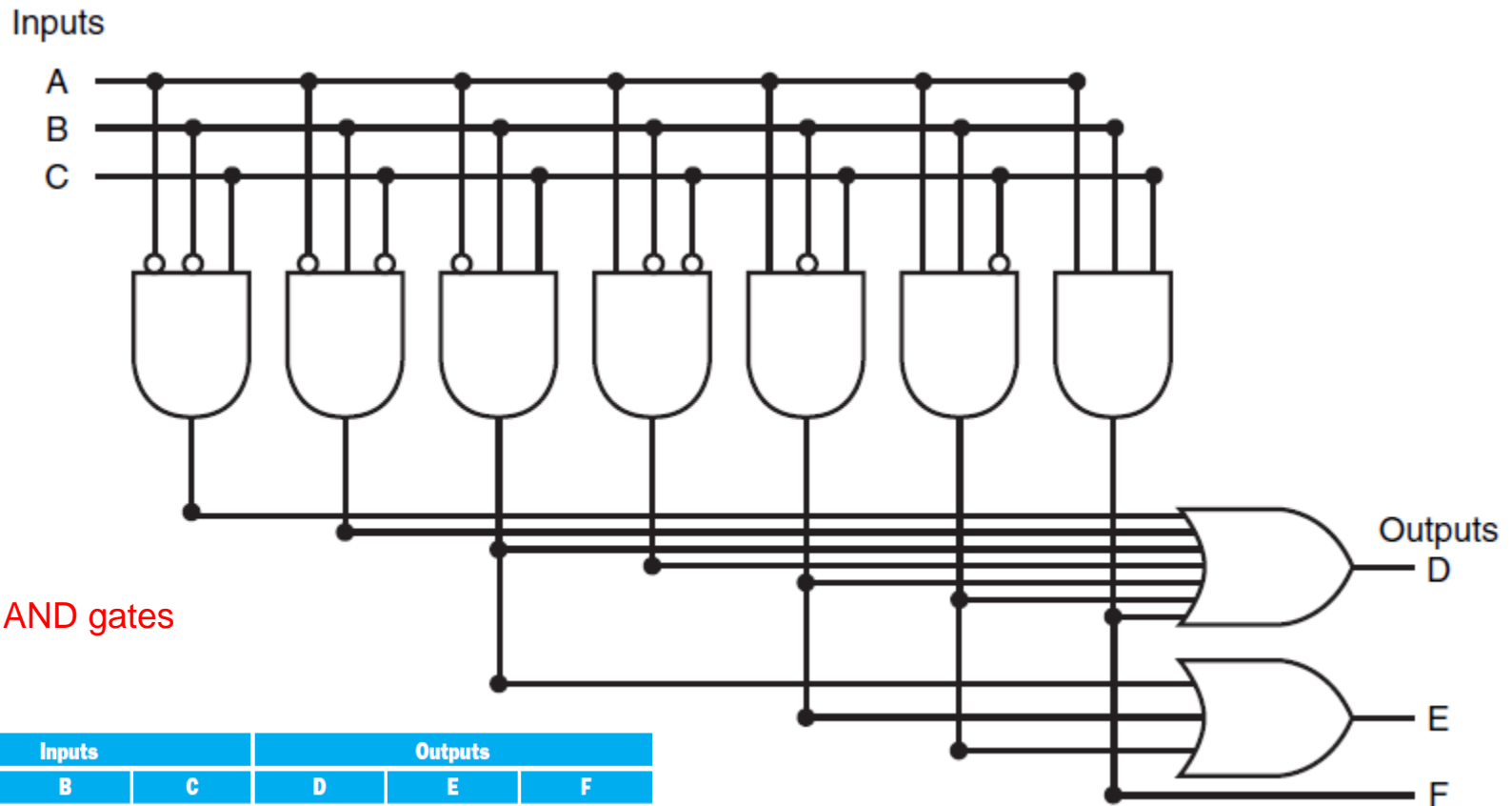


ergste geval: 2^3 AND gates

Inputs			Outputs		
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

how many logic gates?
how long does it take?

Programmable Logic Array (PLA)

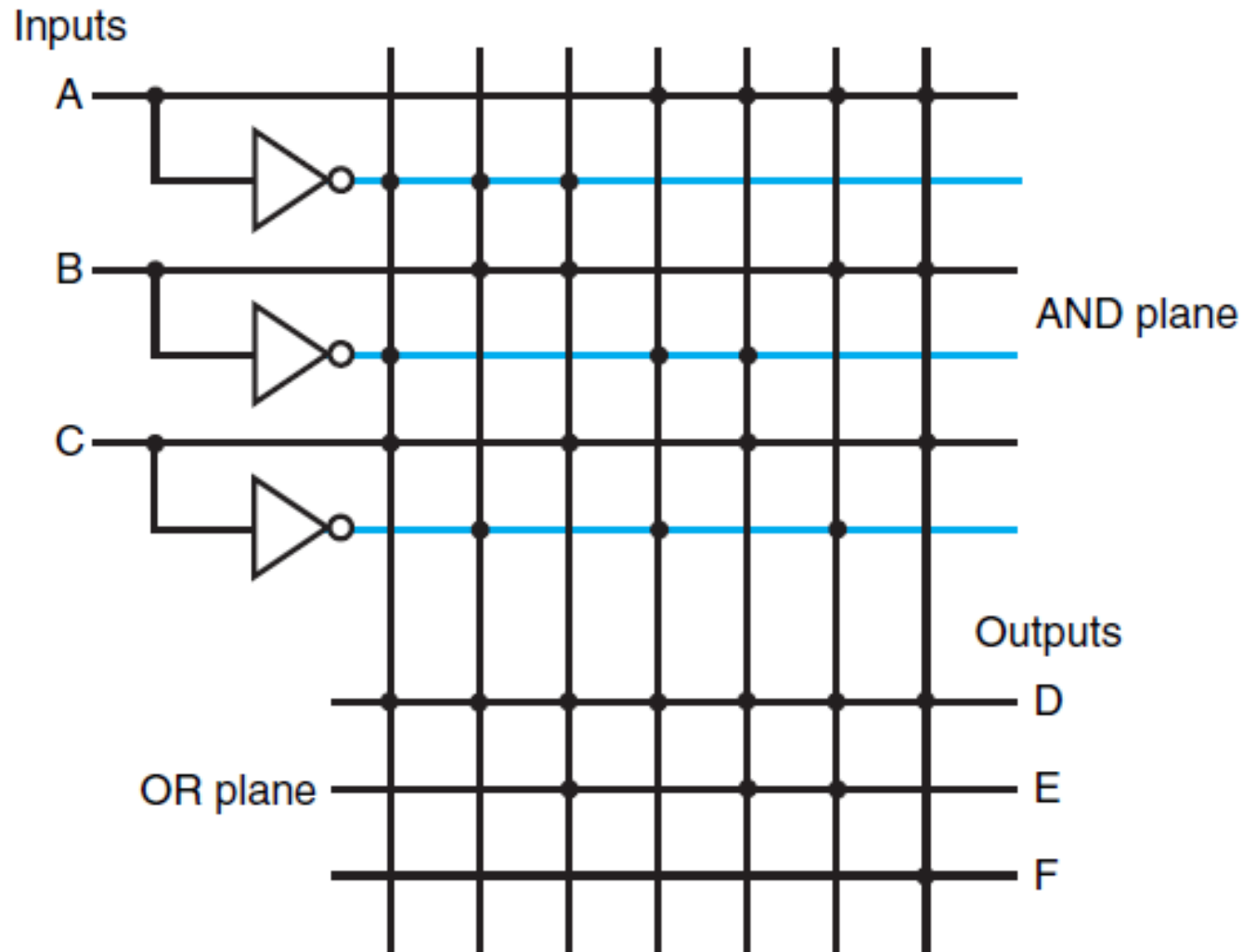

how many logic gates?
how long does it take?

worst case:

how many logic gates?

how long does it take?

I : #inputs

O : #outputs

$$\# \text{ GATES} = I + O$$

(OR, AND)

$$\text{DELAY} = L \cdot E \quad (E \text{ is single GATE DELAY/LATENCY})$$

want parallel

Binary representation/encoding of Unsigned Integers

n-bit string “ $x_{n-1}x_{n-2} \dots x_1x_0$ ” has/encodes **value** x

$$x = x_{n-1}2^{n-1} + x_{n-2}2^{n-2} + \dots + x_12^1 + x_02^0$$

x_0 Least Significant Bit (**LSB**)

x_{n-1} Most Significant Bit (**MSB**)


binair - decimaal (tutorial opzoeken)

- Range: 0 to $+2^n - 1$

- Example

- $0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 1011_2$
 $= 0 + \dots + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0$
 $= 0 + \dots + 8 + 0 + 2 + 1 = 11_{10}$

Decoder (n bits to 2^n outputs)

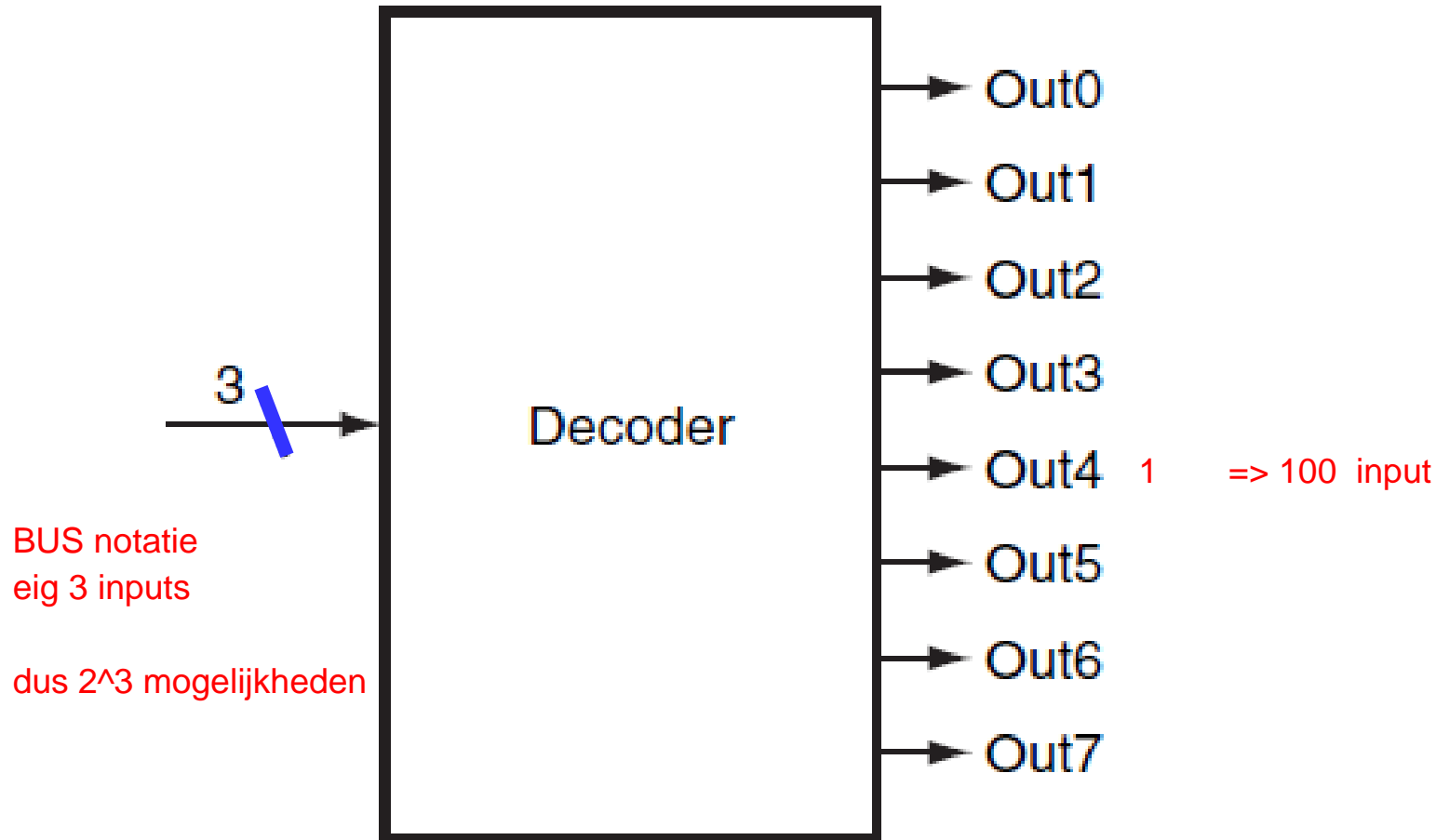

Note: (3 bit wide) signal “bus”

how many logic gates?
how long does it take?

vraag: hoe krijg je 1 bij out 4, welke inputs? (antw: 1 0 0) || hoe lang duurt het om alle 8 de outputs te krijgen (antw: 2 epsi



Decoder (truth table)

Inputs			Outputs							
12	11	10	Out7	Out6	Out5	Out4	Out3	Out2	Out1	Out0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Use “Sum of Products” or “Product of Sums”

split vs. decoder

"Bus"

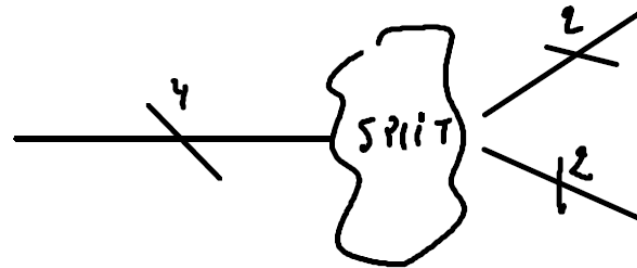
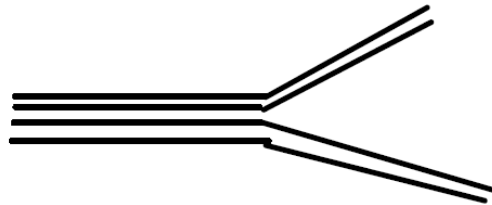


= 0
= 1




= 14
= 15

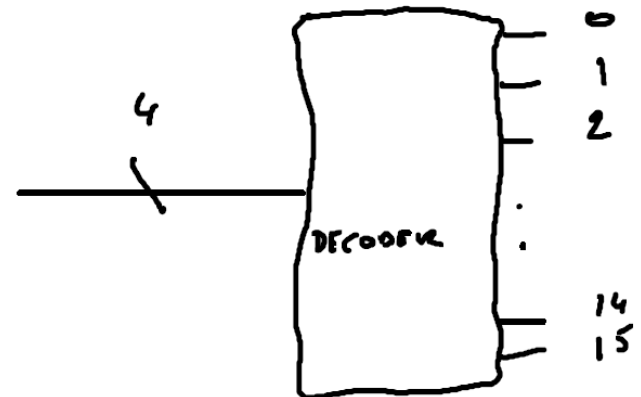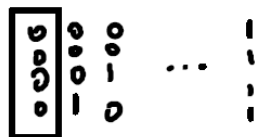4 bit $\rightarrow 2^4 = 16$ mogelijke bit combinaties



Multiplexor (1 bit)

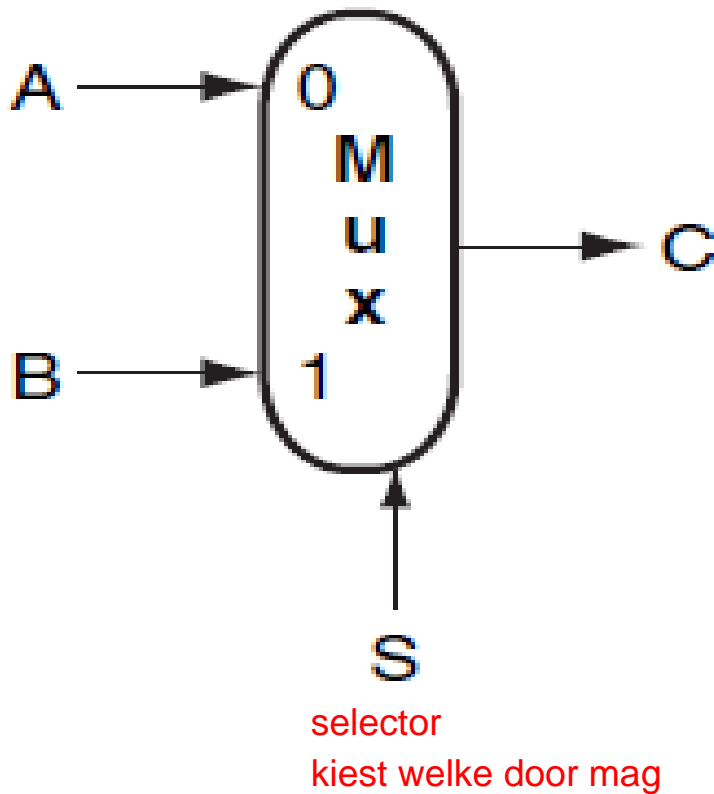selector: bij 0 --> A MAG DOOR
bij 1 --> B MAG DOOR




- Selection
- From **parallel** to **serial**
- Operates on digital **signals**!

A	B	S	C
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	1
0	0	1	0
0	1	1	1
1	0	1	0
1	1	1	1

how many logic gates?
how long does it take?

Multiplexor (1 bit) implementation

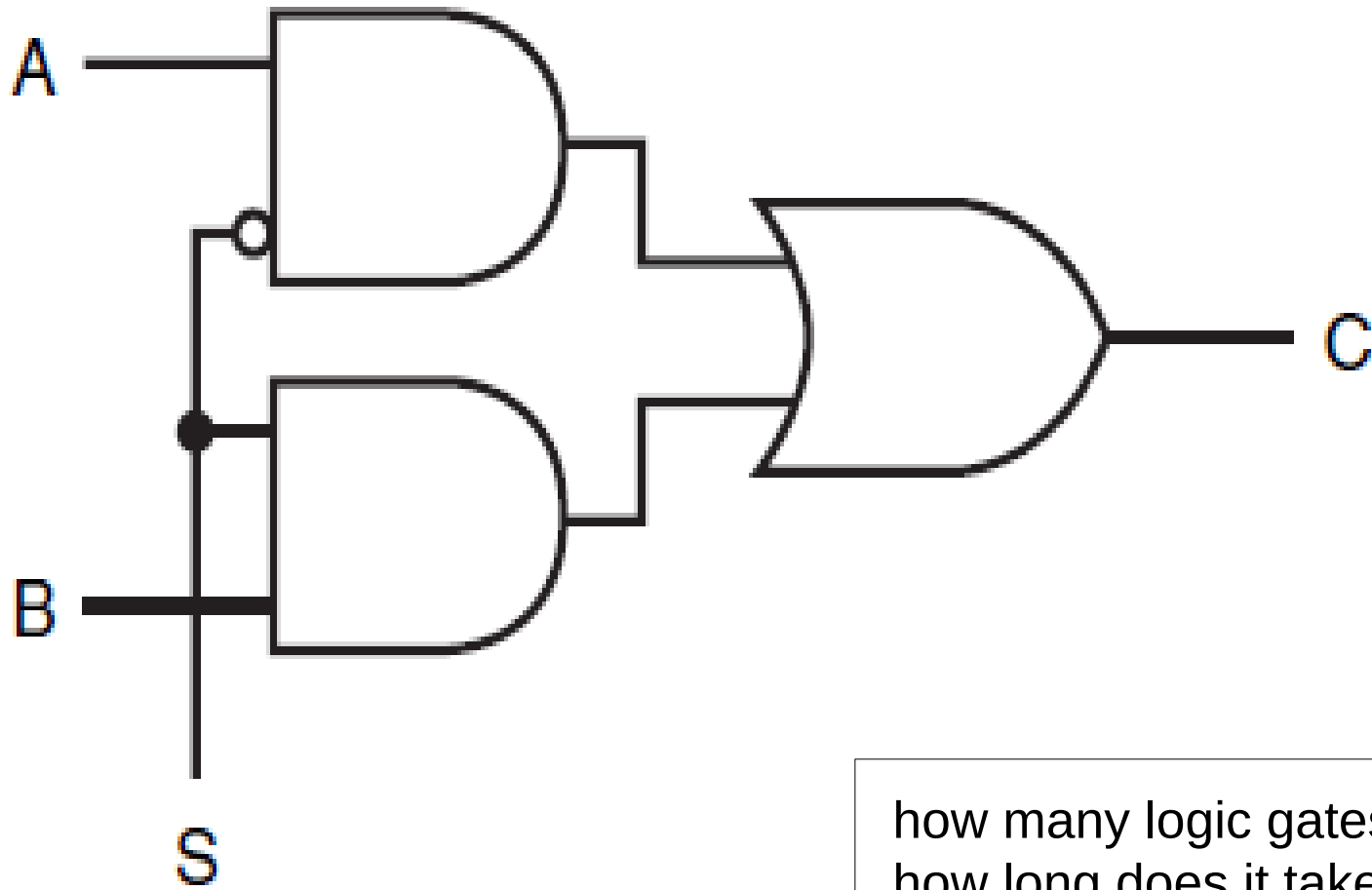

Multiplexor (32 bit), “bus”


#i = 65

o = 32

#GATES = 3

DELAY = 2 epsilon

3*32 gates

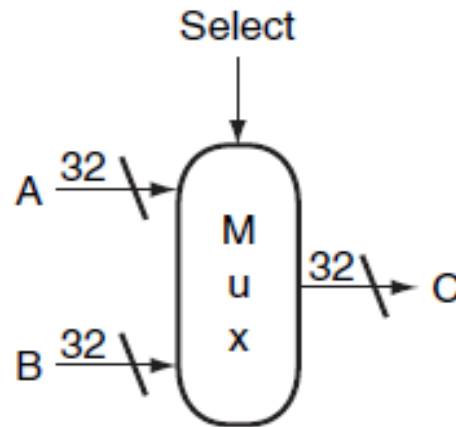


32 1 bit multiplexors, 1 selector

thus 64 + 1 bits

how many logic gates?
how long does it take?

Multiplexor (32 bit) implementation

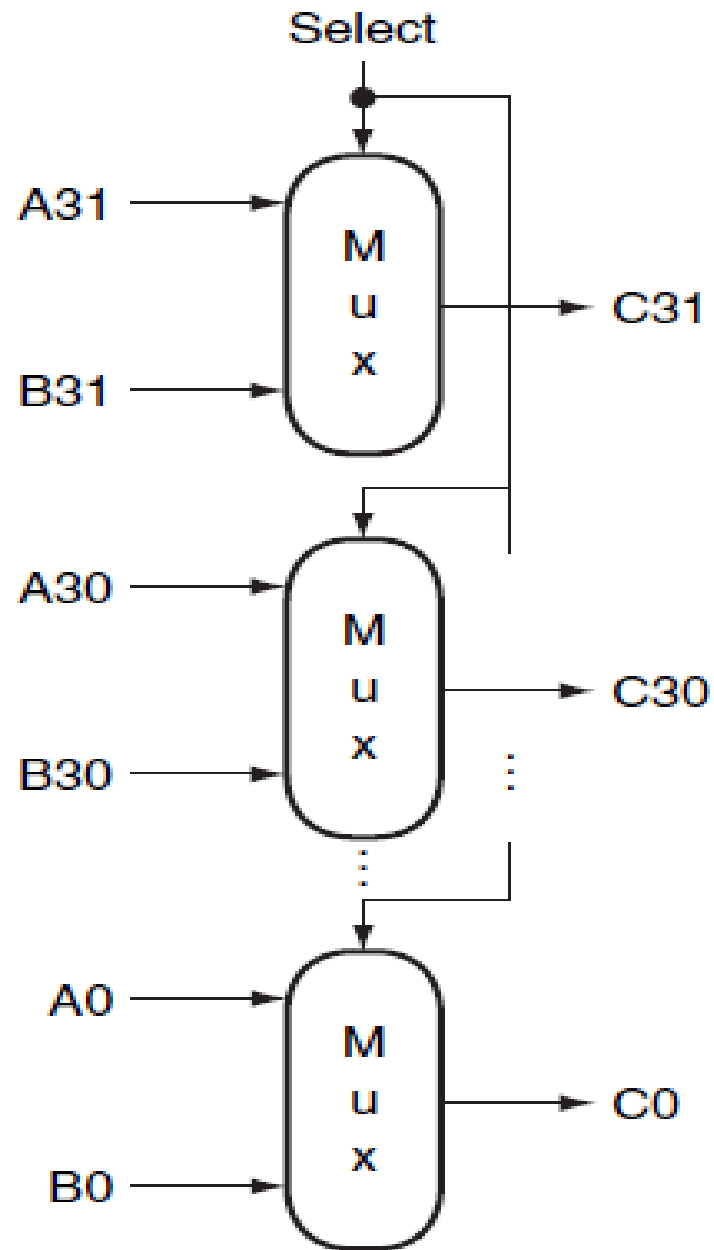

how many logic gates?
how long does it take?

#waarden met 2 bits

00
01
10
11


#waarden n bits
 2^n

K verschillende waarden (in dit geval 3)
bits nodig = k
 $\Rightarrow \log_2(K)$

$\log_2(2^N) = N$

ALTIJD NAAR BOVEN AFRONDEN!
want 1 bit voor 1,001 is niet genoeg

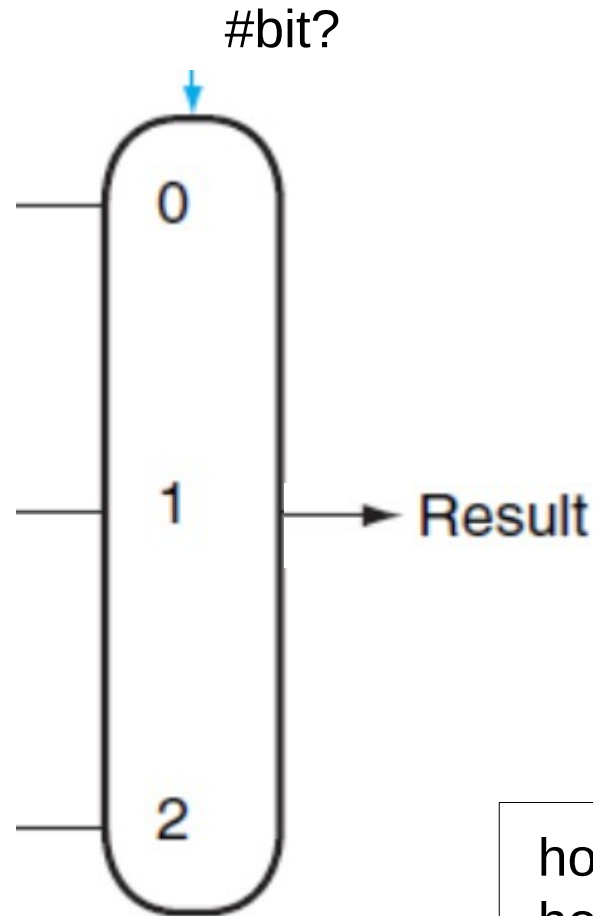$\Rightarrow \text{CEIL}(\log_2(K))$
(omgekeerde is FLOOR)




5 input
1 output

$(5^3 + 1)$ GATES

how many logic gates?
how long does it take?

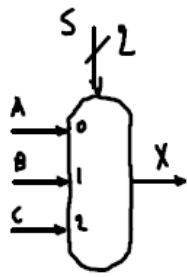sum of products ... "clever"
(I, II, III, see scribbles)




S_1, S_2		
0 0	A	
0 1	B	
1 0	C	
1 1		

$$\Delta t = ?$$


$$\#G = ?$$

I

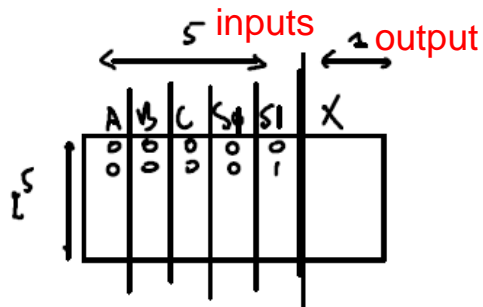

SUM OF PRODUCT 7


II

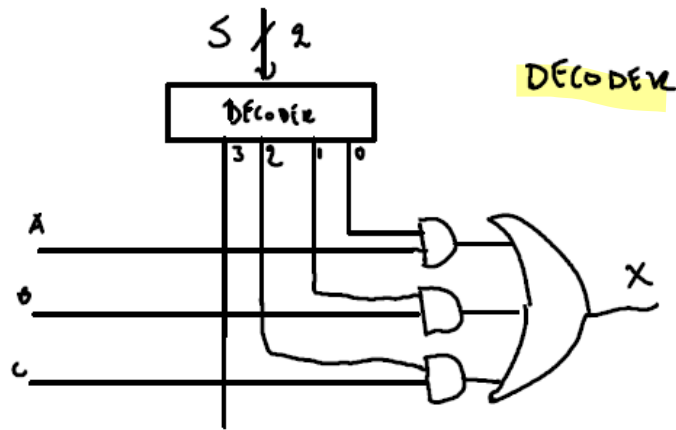

DECODE

III


selector

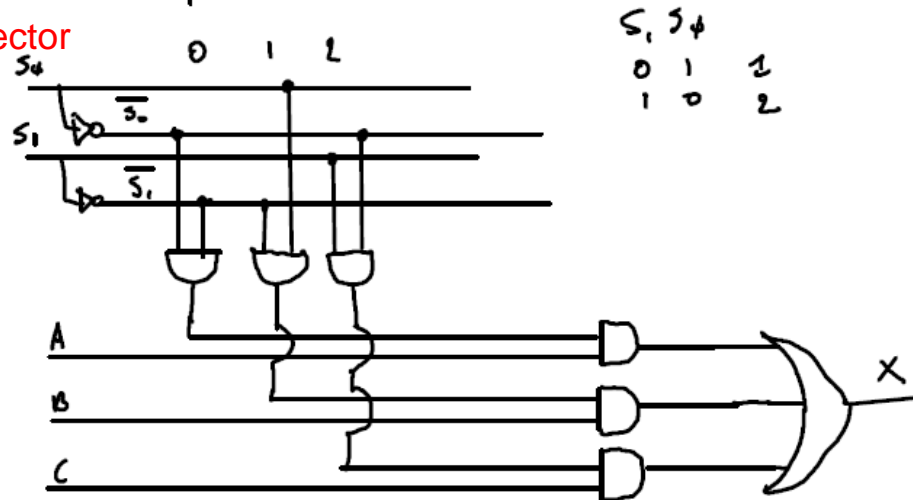

S_1, S_2		
0 1	2	
1 0	2	

7 gates

==> 3 epsilon

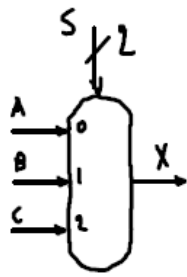


S_1, S_0		A
0 0		B
0 1		C
1 0		
1 1		

$$\Delta t = ?$$

$$\#G = ?$$

I

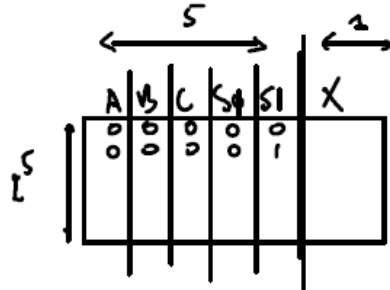


SUM OF PRODUCTS

$$\Delta t = 2\epsilon$$

$$\#G =$$

$$2^5 + 1 = 33$$

II

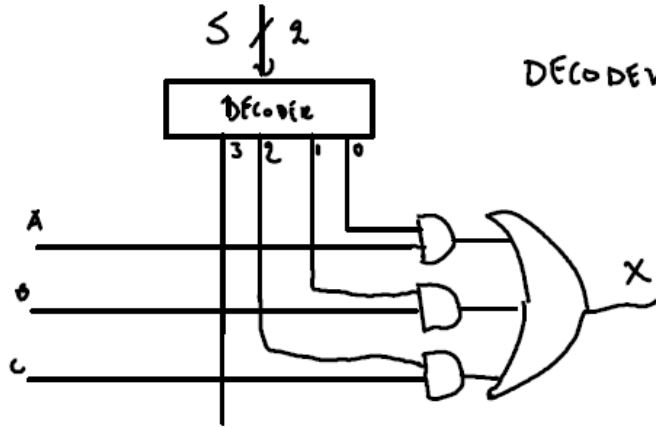

DECODE

NAIVE: SUM OF PRODUCTS

$$\Delta t = \Delta t_{\text{DECODE}} + 2\epsilon$$

$$\#G =$$


$$= 2\epsilon + 2\epsilon$$

$$\#G_{\text{DECODE}} + 4 =$$

$$= 4\epsilon$$

$$(2^2 + 4) + 4 = 12$$

III

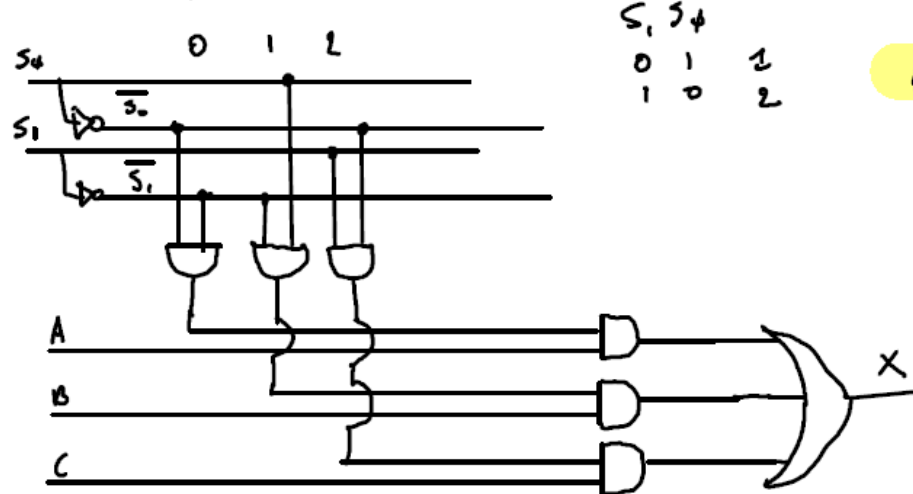

S_1, S_0		0	1	2
0 1				
1 0				

$$\Delta t = 3\epsilon$$

$$\#G = 7$$

Arithmetic and Logic Unit (ALU)

R-Type Instructions

funct	meaning
0	or: $\$rd = \$rd \mid \$rx$
1	xor: $\$rd = \$rd \wedge \$rx$
2	and: $\$rd = \$rd \& \$rx$
3	add: $\$rd = \$rd + \$rx$
4	srl: $\$rd = \$rx \gg 1$
5	sra: $\$rd = \$rx / 2$
6	not: $\$rd = \sim \rx
7	neg: $\$rd = -1 * \rx

1 0 1 1 ==> _ 1 0 1

--> SHIFT RIGHT:

- logical: meest rechste verdwijnt, meest linke wordt 0
- arithmmetic: meest linkse copied 2de

unsigned

DECODE(1011) = $1+2+0+8 = 11$ (basis 2 -> 10)

ENCODE(11) = 1011 (basis 10 -> 2)

1 vooraan zorgt voor negatief getal, als er al een 1 stond, dan willen we het getal ook negatief houden

signed

DECODE(1011) =

ENCODE(1011) =

dus 1111 kan je interpreteren als unsigned (15) en signed (-1) (geheel getal)

PS: 4 bits ==> 2^4 values

shift right logical

shift right arithmetic

bij shift left arithmetic ==> $*2$

$$G = 2 * D + R$$

$$D = G \text{ DIV } 2$$


$$K = G \text{ MOD } 2$$

Note: instruction (e.g., not vs. neg) determines data type (e.g., Boolean vs. Int)


$$5 \text{ DIV } 2 = 2 \text{ (hoeveel keer 2 in 5)}$$

$$5 \text{ MOD } 2 = 1 \text{ (hoeveel rest bij optimale 5/2)}$$

Arithmetic and Logic Unit (ALU)

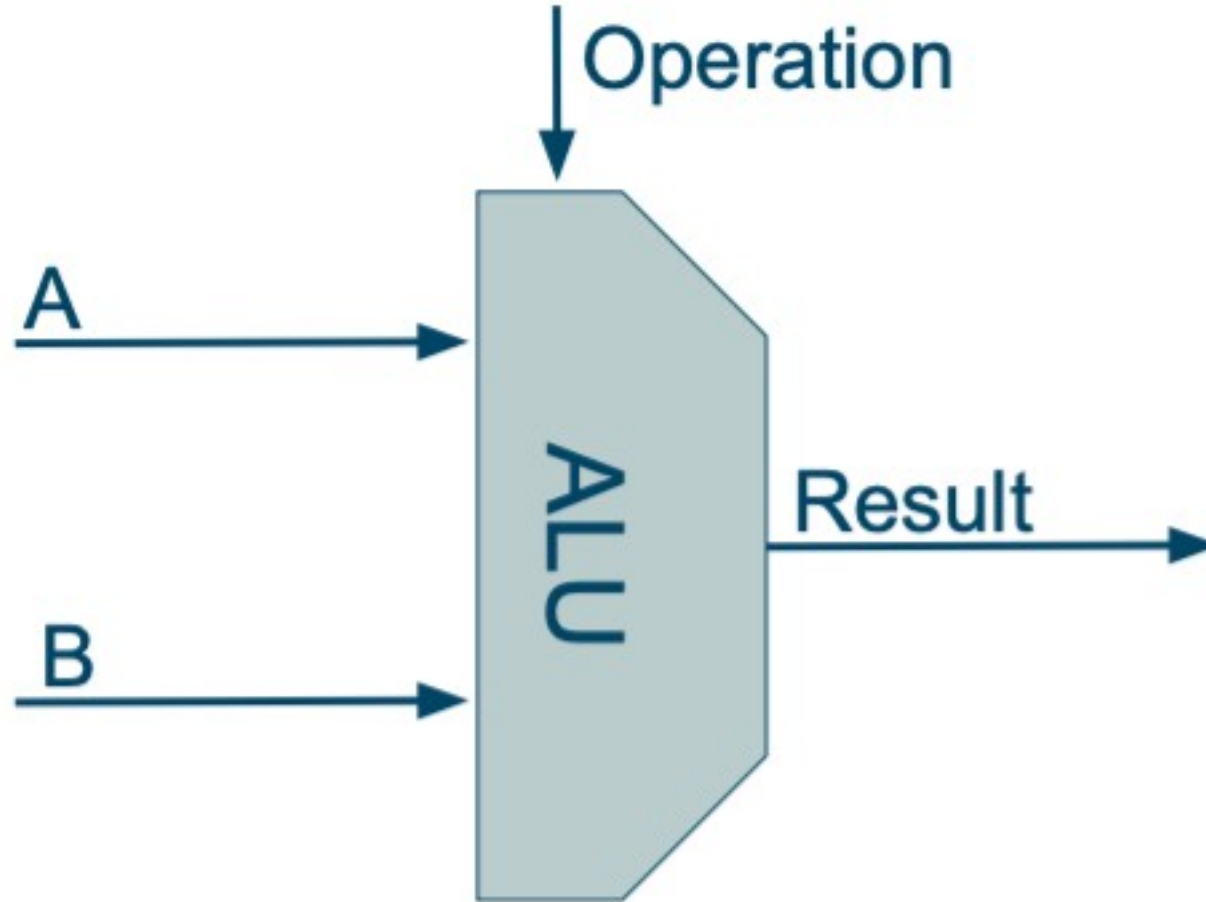

1-bit AND, OR

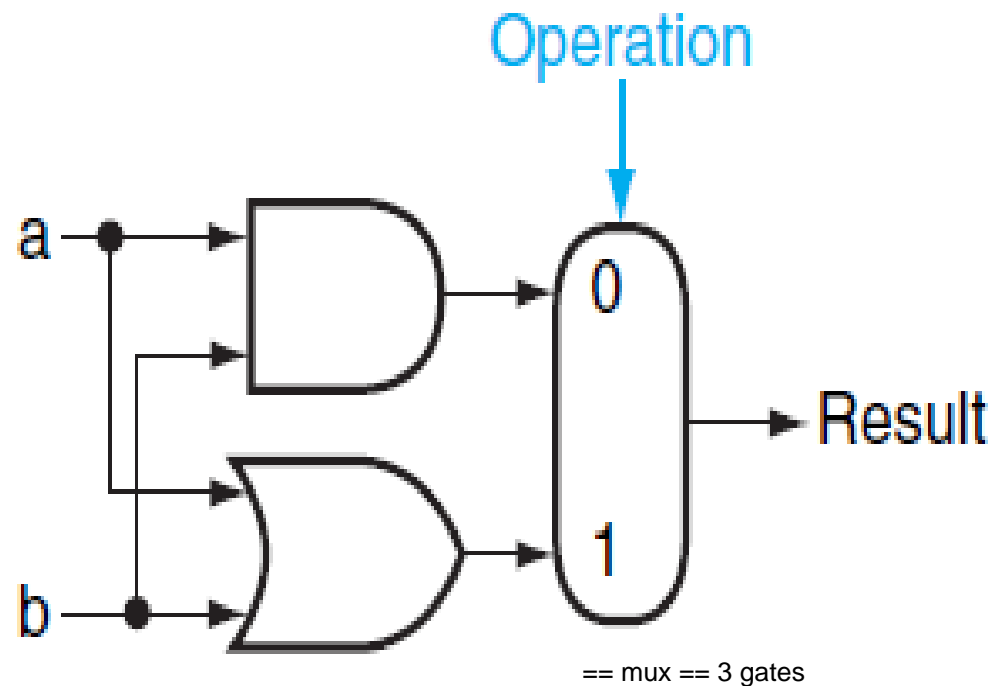

how many logic gates? 5 gates

how long does it take? 3 epsilon

want 3 keer gate
doorgang

Binary representation of information

- in computing and telecommunications
- a **bit** is a basic *unit of information storage*
- “**binary digit**”
- the maximum amount of information
- that can be stored in only two distinct states

0 or 1

Bit sequences (bit) “string” (vs. char string)

0	1 bit	bit
0111	4 bits	nibble
01100001	8 bits	byte
0101010110110111	16 bits	half-word
...	32 bits	word
...	64 bits	word

A **word** is a natural unit of data used by a particular processor design (8, 16, 24, 32, or 64 bits)

Byte = Octet (in French)



Disque Dur Externe WD My Book New 8 To Noir

Disques durs externes - Western Digital ★★★★★ (19)



PRIX ADHERENT

[Voir le produit](#)

Type de disque dur	Disque Dur Externe	✓ En stock en ligne Livraison gratuite
Technologie de disque dur	Disque Dur (HDD)	
Capacité de stockage (Go)	8000 Go	📍 En magasin Choisir

Origin of the term “byte”

The term byte was coined by Werner Buchholz in June 1956, during the early design phase for the IBM Stretch computer, which had addressing to the bit and variable field length (VFL) instructions with a byte size encoded in the instruction. It is a deliberate respelling of **bite** to avoid accidental mutation to bit.

Binary representation ++

1 Bit	2 Bits	3 Bits	4 Bits	5 Bits
0	00	000	0000	00000
1	01	001	0001	00001
	10	010	0010	00010
	11	011	0011	00011
		100	0100	00100
		101	0101	00101
		110	0110	00110
		111	0111	00111
			1000	01000
			1001	01001
			1010	01010
			1011	01011
			1100	01100
			1101	01101
			1110	01110
			1111	01111
				10000
				10001
				10010
				10011
				10100
				10101
				10110
				10111
				11000
				11001
				11010
				11011
				11100
				11101
				11110
				11111

With 1 bit, can **represent/encode**
2 distinct entities


With 2 bits, can represent/encode
4 distinct entities

...

With **N** bits, can represent/encode
 2^N distinct entities

Example: {Red, Green, Blue}
encoded as {00, 01, 10}
code 11 not used

Arithmetic and Logic Unit (ALU)

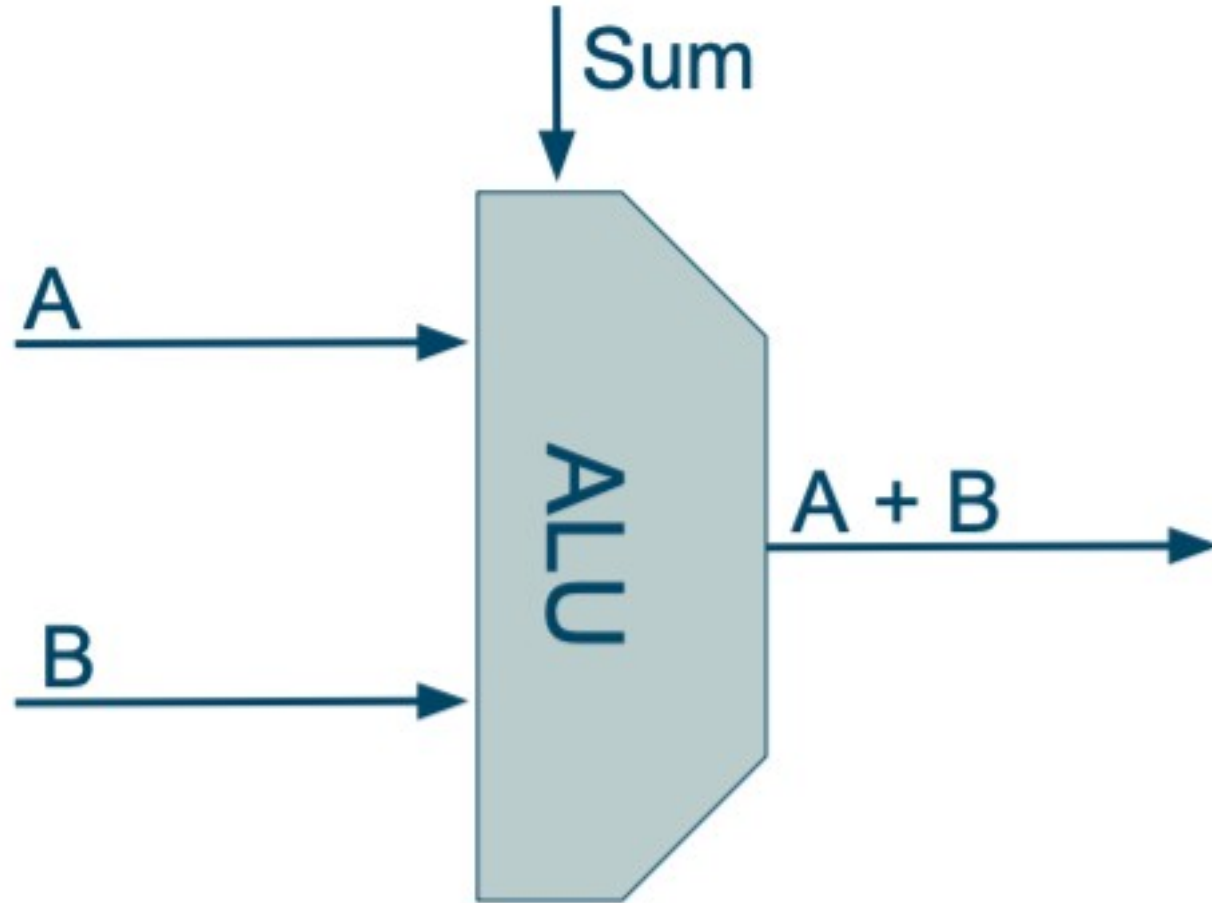

Addition (decimal)

$$\begin{array}{r} 81730 \\ + 19223 \\ \hline \end{array}$$

Addition (decimal)

“carry”

$$\begin{array}{r} 0 \\ 81730 \\ + 19223 \\ \hline 3 \end{array}$$

Addition (decimal)

$$\begin{array}{r} \text{"carry"} \quad 00 \\ 81730 \\ + 19223 \\ \hline 3 \end{array}$$

Addition (decimal)

$$\begin{array}{r} \text{"carry"} \quad 000 \\ 81730 \\ + 19223 \\ \hline 53 \end{array}$$

Addition (decimal)

$$\begin{array}{r} \text{"carry"} \quad 0000 \\ 81730 \\ + 19223 \\ \hline 953 \end{array}$$

Addition (decimal)

$$\begin{array}{r} \text{"carry"} \quad 10000 \\ 81730 \\ + 19223 \\ \hline 0953 \end{array}$$

Addition (decimal)

$$\begin{array}{r} \text{"carry"} \quad 110000 \\ \quad 81730 \\ + \quad 19223 \\ \hline \quad 00953 \end{array}$$


Addition (decimal)

$$\begin{array}{r} \text{"carry"} \quad 110000 \\ \quad 81730 \\ + \quad 19223 \\ \hline 100953 \end{array}$$

Binary Addition

$$\begin{array}{r} 00101110 \\ + 00100111 \\ \hline \end{array}$$


Binary Addition (8 bit)


$$\begin{array}{r} 01011100 \\ 00101110 \\ + 00100111 \\ \hline 01010101 \end{array}$$


how many inputs?
how many outputs?

how many logic gates?
how long does it take?

Binary Addition (1 bit at a time)
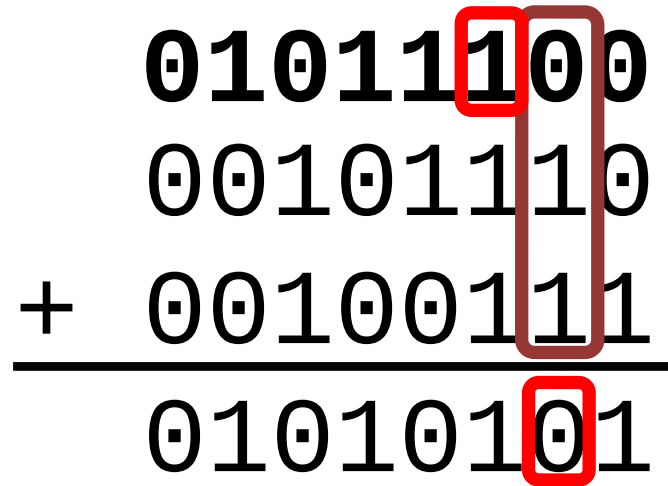
$$\begin{array}{r} 01011100 \\ 00101110 \\ + 00100111 \\ \hline 01010101 \end{array}$$

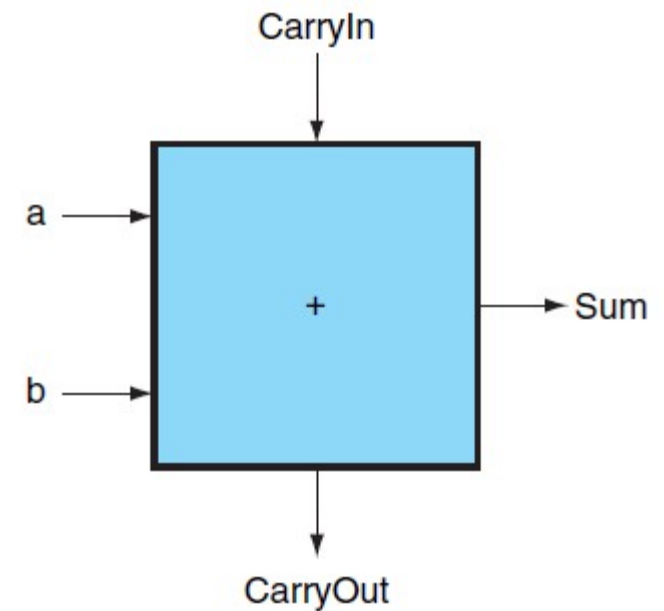
(zoek tutorial, nog niet volledig gesnapt)



1-bit adder

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

$$\begin{array}{r}
 01011100 \\
 00101110 \\
 + 00100111 \\
 \hline
 01010101
 \end{array}$$

1-bit adder

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

$$\begin{array}{r}
 01011100 \\
 00101110 \\
 + 00100111 \\
 \hline
 01010101
 \end{array}$$

1-bit adder

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

$$\begin{array}{r}
 01011100 \\
 00101110 \\
 + 00100111 \\
 \hline
 01010101
 \end{array}$$

1-bit adder

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

$$\begin{array}{r}
 01011\boxed{1}\boxed{0}0 \\
 00101110 \\
 + 00100111 \\
 \hline
 010101\boxed{0}1
 \end{array}$$

1-bit adder

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

Sum

Is 1 when *exactly one input is one* or when *all inputs are one*

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

Sum

Is 1 when *exactly one input is one* or when *all inputs are one*

$$\text{Sum} = (a \cdot \bar{b} \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot b \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot \bar{b} \cdot \text{CarryIn}) + (a \cdot b \cdot \text{CarryIn})$$

how many logic gates? 5
 how long does it take? 2 epsilon

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

CarryOut

Is 1 when *at least two inputs are one*


Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

CarryOut

Is 1 when *at least two inputs are one*

$$\text{CarryOut} = (b \cdot \text{CarryIn}) + (a \cdot \text{CarryIn}) + (a \cdot b) + \dots ?$$

1-bit Adder: Carry Out

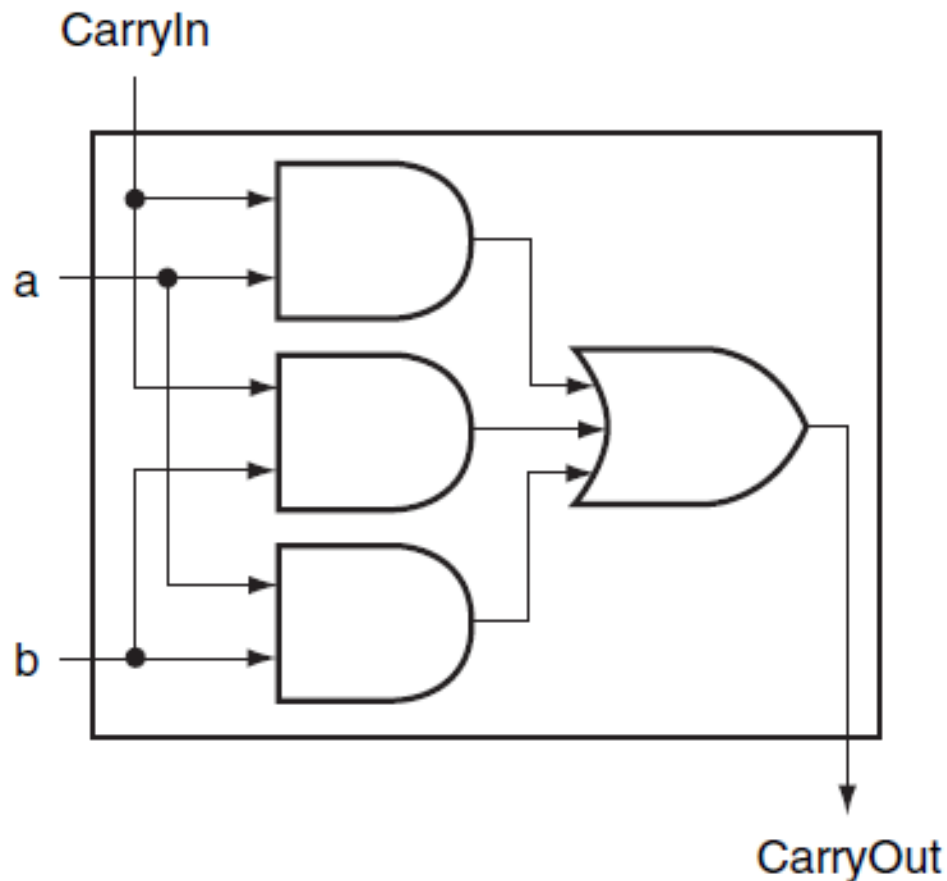

CarryOut is 1 when


Inputs		
a	b	CarryIn
0	1	1
1	0	1
1	1	0
1	1	1

how many logic gates? ⁴
how long does it take? ^{2 epsilon}


voor heel de doos, 9 gates (sum + carryin); 2 epsilon delay

32 bit adder ==> 1 bit adders aan elkaar hangen dus #GATES = 32 * 9 & DELAY = 32 * 2 epsilon

Arithmetic and Logic Unit (ALU)

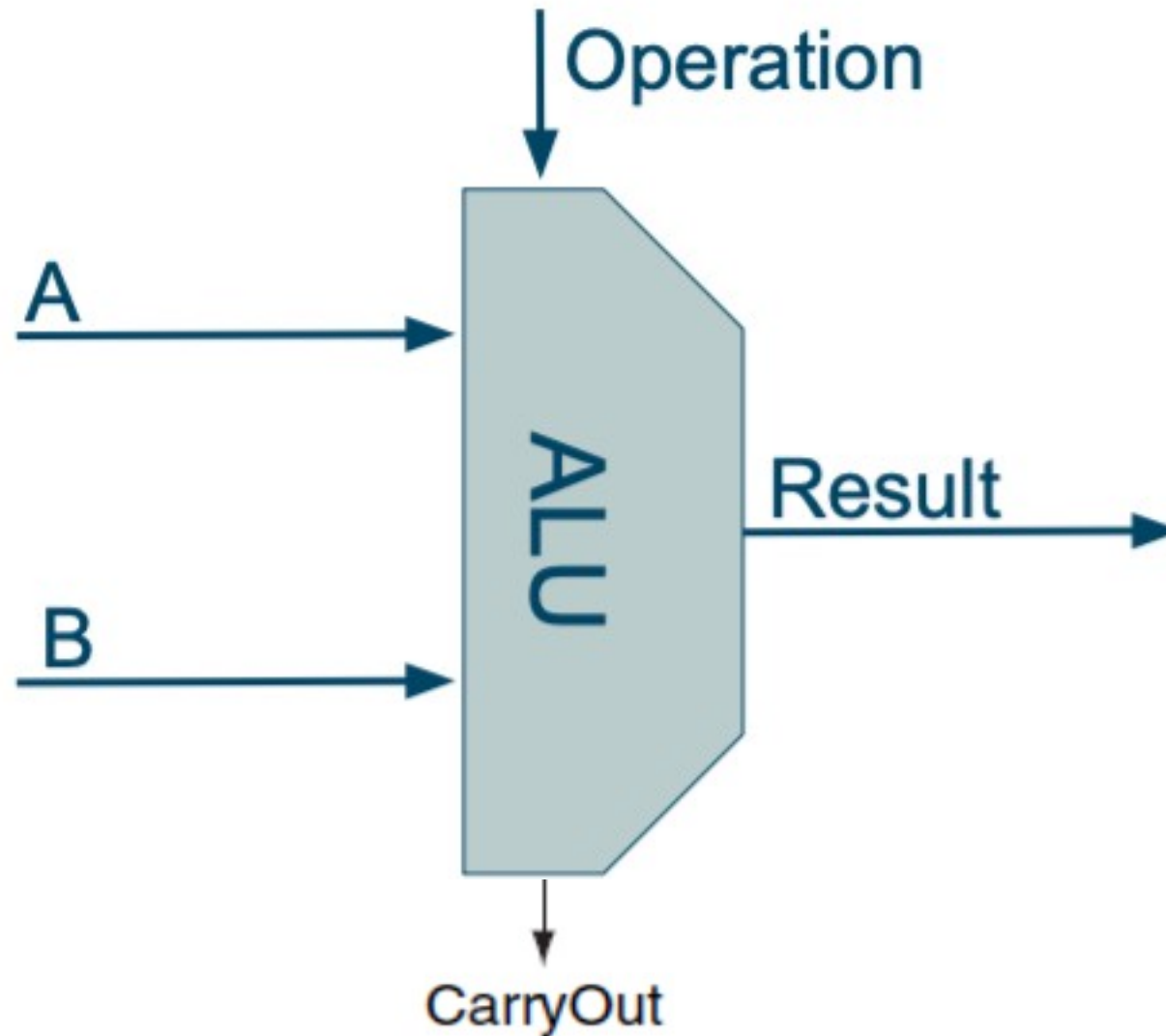

1-bit ALU (AND, OR, +)

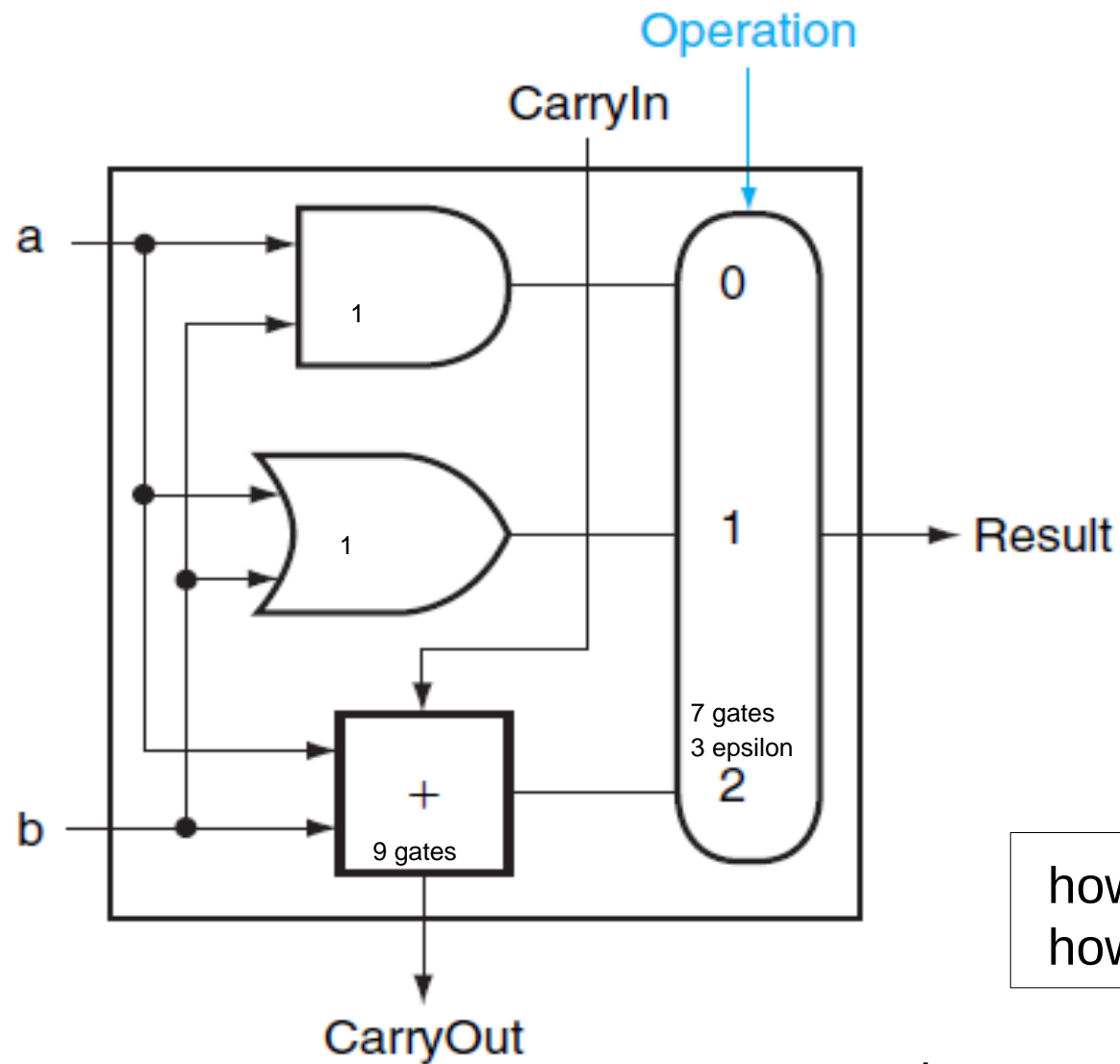


how many logic gates? ¹⁸
how long does it take? _{4 epsilon}

beware: multiplexor has 3 choices!

Ripple Carry Adder

Series of 1-bit full adders

Carry ripples through addition = Slow!

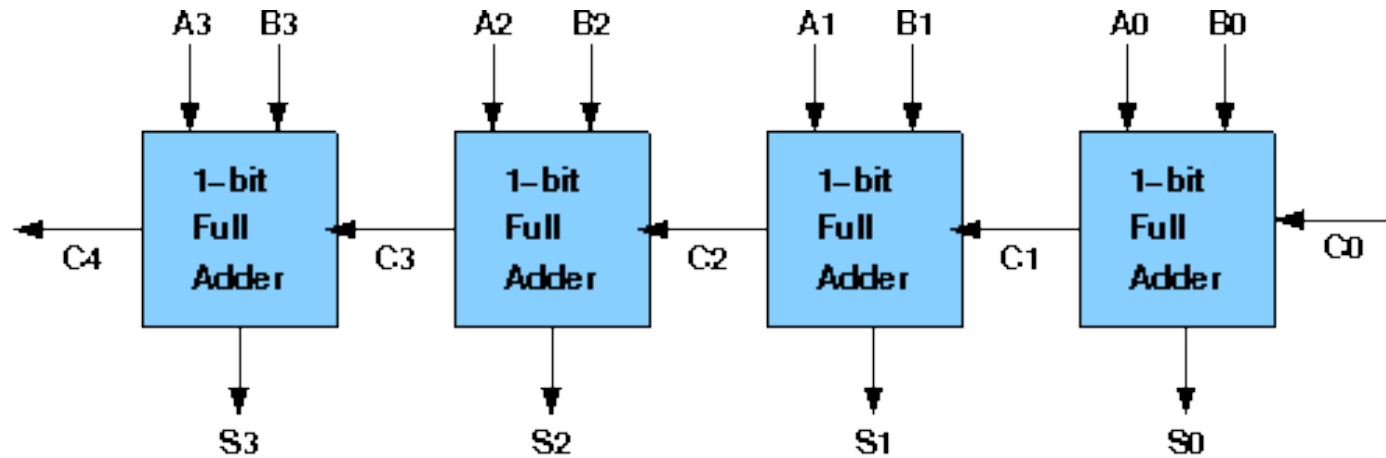


Ripple Carry Adder

Series of 1-bit full adders

Carry ripples through addition = Slow!
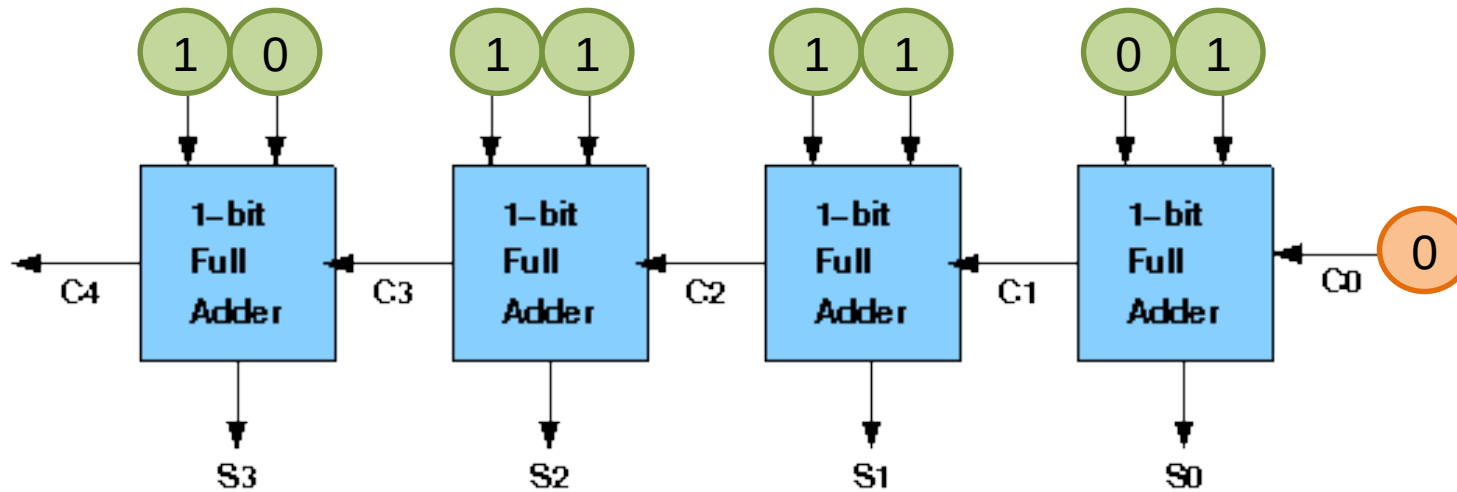
$$\begin{array}{r} 0 \\ 1110 \\ + 0111 \\ \hline \end{array}$$




Ripple Carry Adder

Series of 1-bit full adders

Carry ripples through addition = Slow!
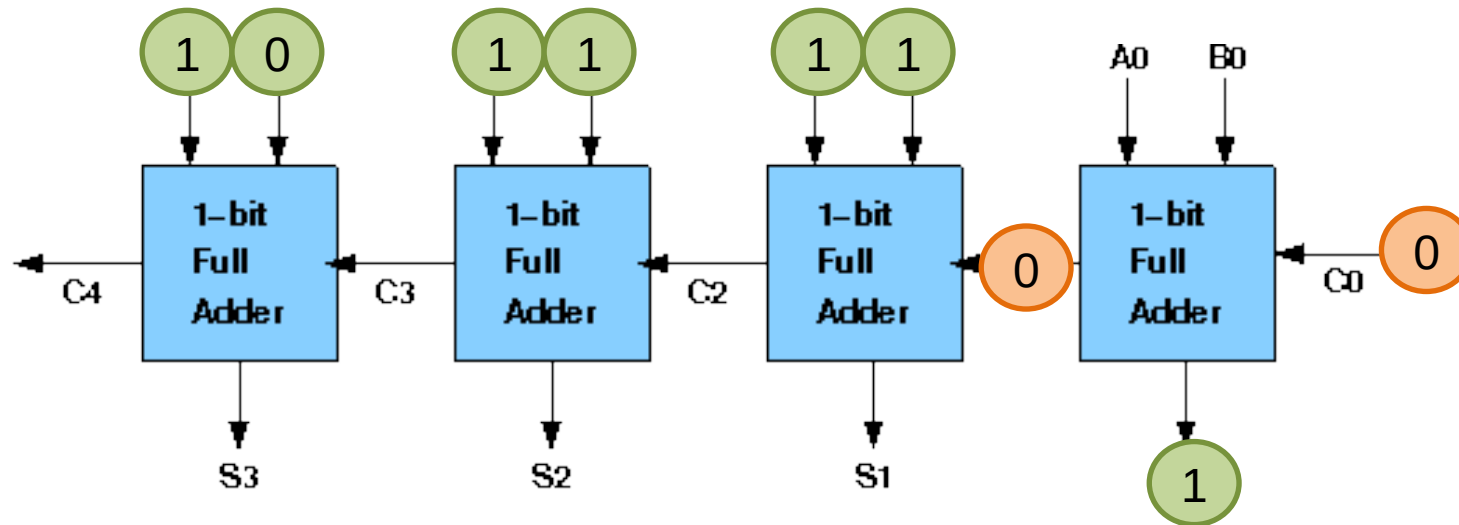
$$\begin{array}{r} 00 \\ 1110 \\ + 0111 \\ \hline 1 \end{array}$$




Ripple Carry Adder

Series of 1-bit full adders

Carry ripples through addition = Slow!
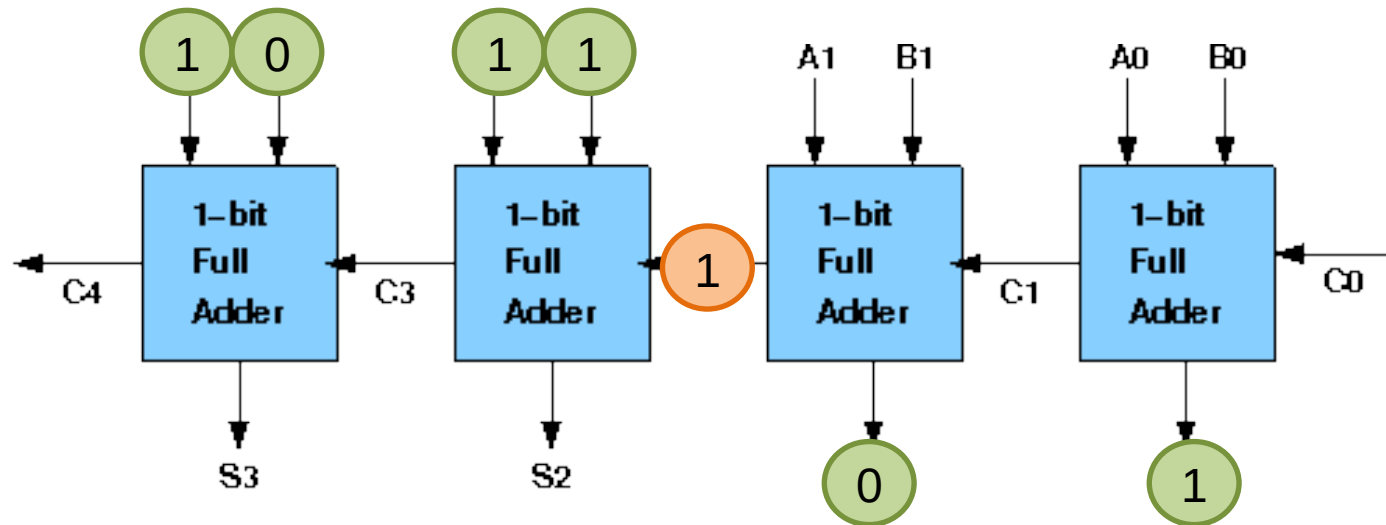
$$\begin{array}{r} 100 \\ 1110 \\ + 0111 \\ \hline 01 \end{array}$$




Ripple Carry Adder

Series of 1-bit full adders

Carry ripples through addition = Slow!
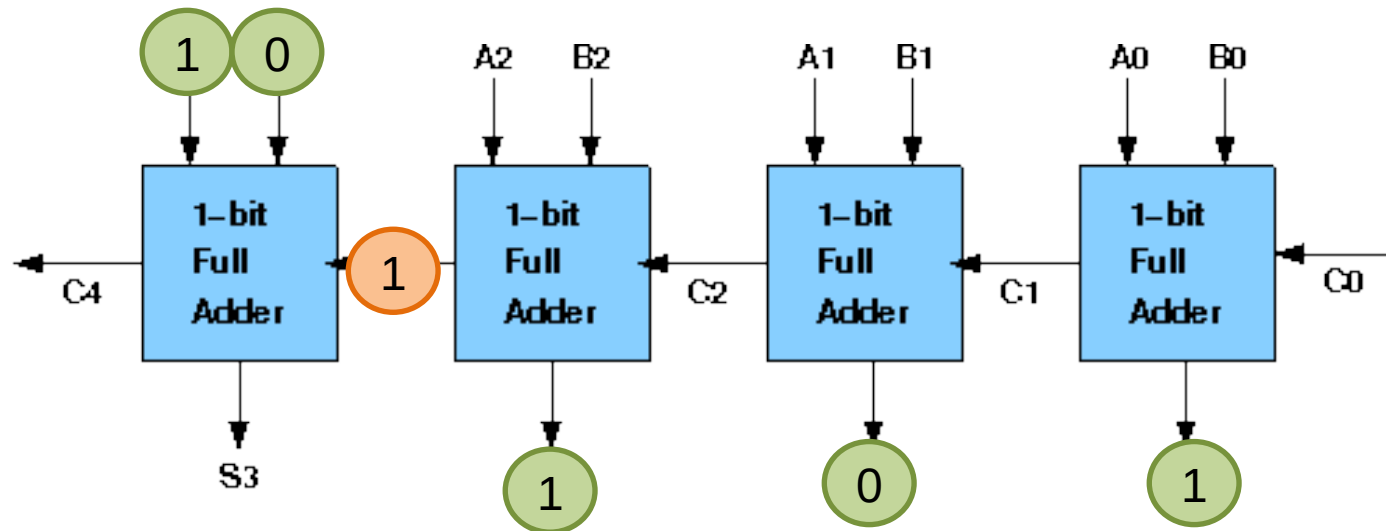
$$\begin{array}{r} 1100 \\ 1110 \\ + 0111 \\ \hline 1011 \end{array}$$




Ripple Carry Adder

Series of 1-bit full adders

Carry ripples through addition = Slow!
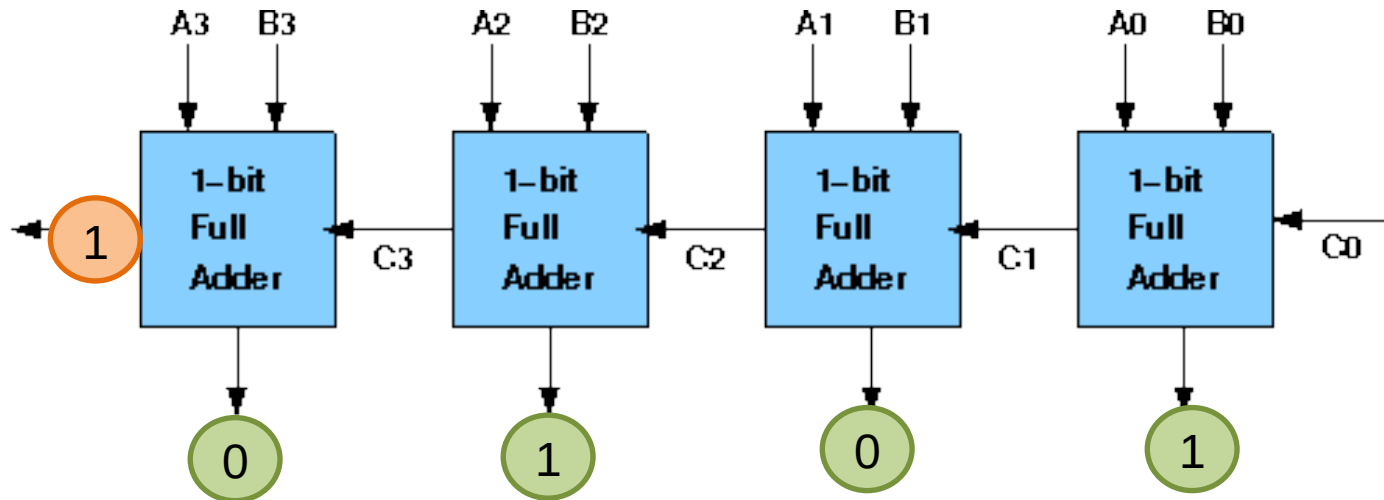
$$\begin{array}{r} 11100 \\ 1110 \\ + 0111 \\ \hline 0101 \end{array}$$



Ripple Carry Adder


Series of 1-bit full adders

Carry ripples through addition = Slow!

Incorrect intermediate result!

(assume result of previous calculation all 0s)
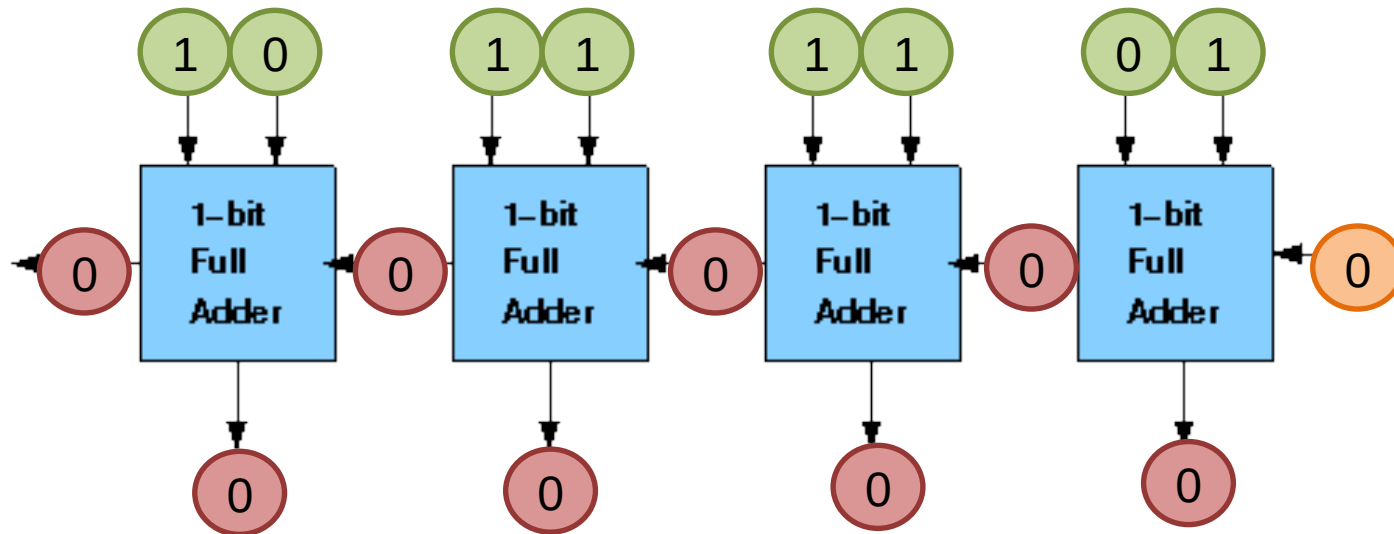
$$\begin{array}{r} 00000 \\ 1110 \\ + 0111 \\ \hline 0000 \end{array}$$




Ripple Carry Adder

Series of 1-bit full adders

Carry ripples through addition = Slow!

Incorrect intermediate result!
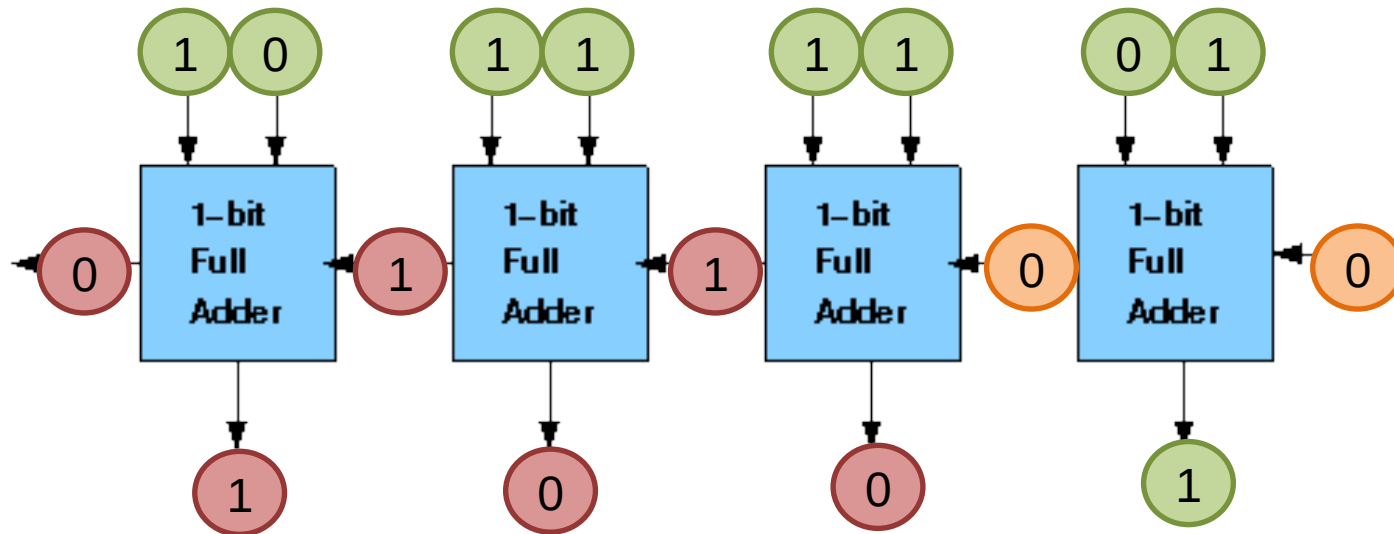
$$\begin{array}{r} 01100 \\ 1110 \\ + 0111 \\ \hline 0001 \end{array}$$




Ripple Carry Adder

Series of 1-bit full adders

Carry ripples through addition = Slow!

Incorrect intermediate result!
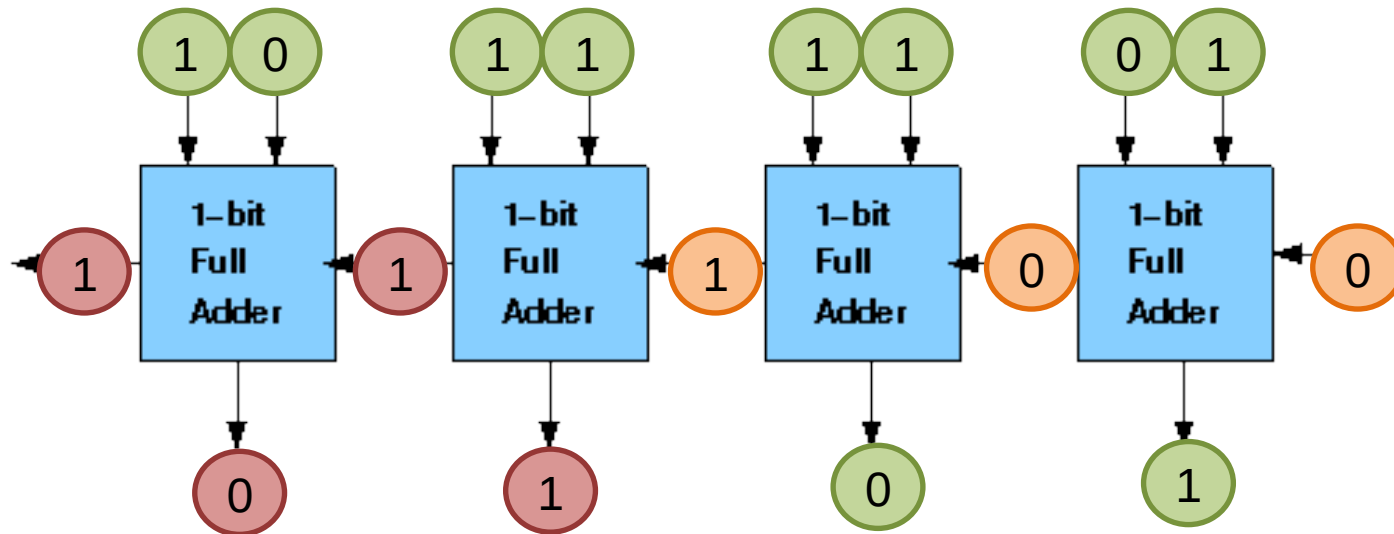
$$\begin{array}{r} 11100 \\ 1110 \\ + 0111 \\ \hline 0101 \end{array}$$




Ripple Carry Adder


Series of 1-bit full adders

Carry ripples through addition = Slow to get to final correct result!
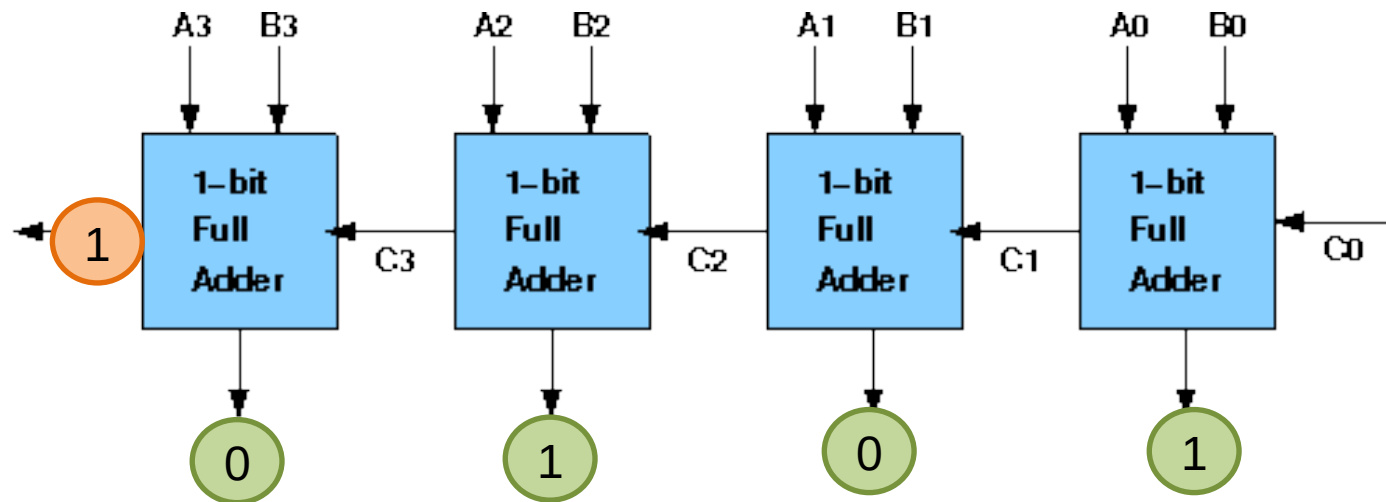
$$\begin{array}{r} 11100 \\ 1110 \\ + 0111 \\ \hline 0101 \end{array}$$



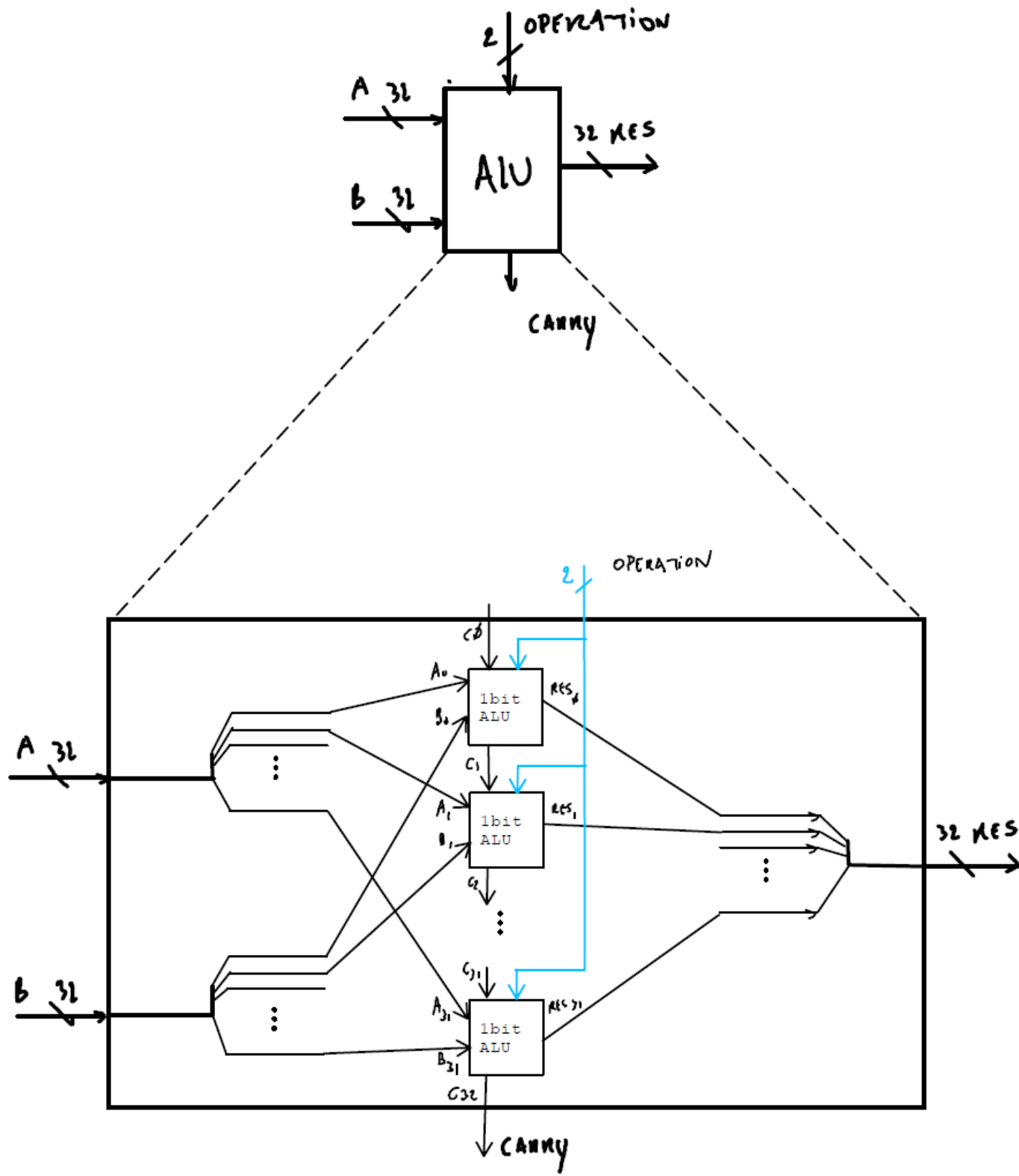how many logic gates?
how long does it take?




32-bit ALU

**Adder:
Ripple Carry**

Inefficient!

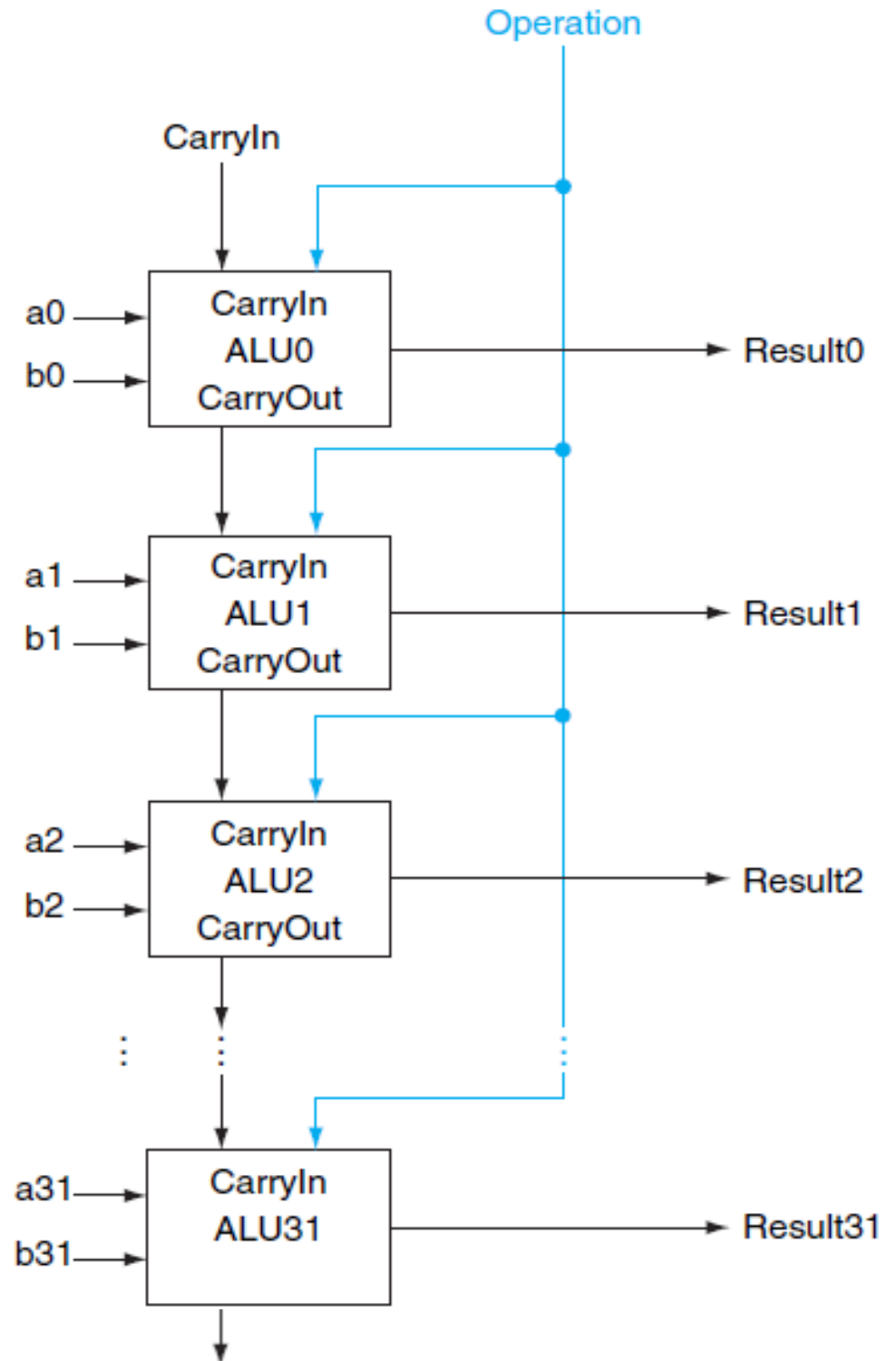how many logic gates?
how long does it take?



32-bit ALU


Adder:
Ripple Carry

Inefficient!

how many logic gates? $(2+33) \cdot 32 + 32 + 1 = 65$
how long does it take? $2 \cdot \epsilon$

can we make this faster?
→ number of gates?

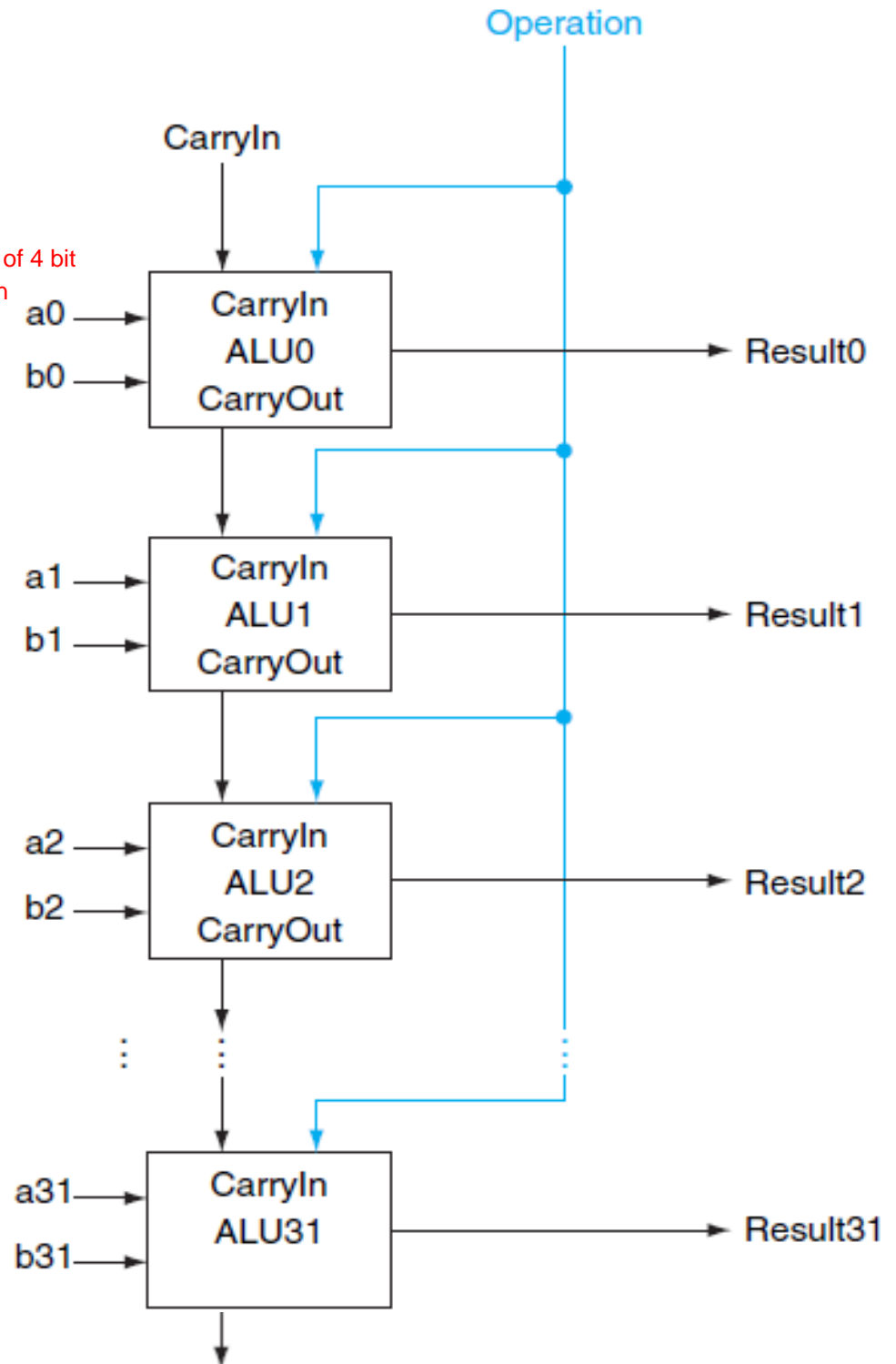groeperen en 2 bit of 4 bit
adder ervan maken



Solution: Calculate Carry Faster

$$\begin{array}{r} \text{???????0} \text{ carry in} \\ 00101110 \text{ A} \\ + 00100111 \text{ B} \\ \hline 01010101 \end{array}$$

Adder: Fast Carry using “infinite hardware”

CarryIn1 = CarryOut0

op voorhand berekenen

$$\begin{array}{cccc} & c3 & c2 & c1 & c0 \\ & a3 & a2 & a1 & a0 \\ + & b3 & b2 & b1 & b0 \\ \hline & s3 & s2 & s1 & s0 \end{array}$$

Adder: Fast Carry using “infinite hardware”

$$\text{CarryIn1} = (\text{b0.CarryIn0}) + (\text{a0.CarryIn0}) + (\text{a0.b0})$$

$$\begin{array}{cccc} & c3 & c2 & c1 & c0 \\ & a3 & a2 & a1 & a0 \\ + & b3 & b2 & b1 & b0 \\ \hline & s3 & s2 & s1 & s0 \end{array}$$

Adder: Fast Carry using “infinite hardware”

$$\text{CarryIn1} = (b0.\text{CarryIn0}) + (a0.\text{CarryIn0}) + (a0.b0)$$

$$c1 = (a0.c0) + (b0.c0) + (a0.b0)$$

$$\begin{array}{cccc} & c3 & c2 & c1 & c0 \\ & a3 & a2 & a1 & a0 \\ + & b3 & b2 & b1 & b0 \\ \hline & s3 & s2 & s1 & s0 \end{array}$$

Adder: Fast Carry using “infinite hardware”

$$\text{CarryIn1} = (b0.\text{CarryIn0}) + (a0.\text{CarryIn0}) + (a0.b0)$$

$$c1 = (a0.c0) + (b0.c0) + (a0.b0)$$

$$c2 = (a1.c1) + (b1.c1) + (a1.b1)$$

$$\begin{array}{cccc} & c3 & c2 & c1 & c0 \\ & a3 & a2 & a1 & a0 \\ + & b3 & b2 & b1 & b0 \\ \hline & s3 & s2 & s1 & s0 \end{array}$$

Adder: Fast Carry using “infinite hardware”

$$\text{CarryIn1} = (b0.\text{CarryIn0}) + (a0.\text{CarryIn0}) + (a0.b0)$$

$$c1 = (a0.c0) + (b0.c0) + (a0.b0)$$

$$\begin{array}{cccc}
 & c3 & c2 & c1 & c0 \\
 & a3 & a2 & a1 & a0 \\
 + & b3 & b2 & b1 & b0 \\
 \hline
 & s3 & s2 & s1 & s0
 \end{array}$$

$$c2 = (a1.c1) + (b1.c1) + (a1.b1)$$

$$= (a1. ((a0.c0) + (b0.c0) + (a0.b0))) + (b1.((a0.c0) + (b0.c0) + (a0.b0))) + (a1.b1)$$

Adder: Fast Carry using “infinite hardware”

$$\text{CarryIn1} = (b0.\text{CarryIn0}) + (a0.\text{CarryIn0}) + (a0.b0)$$

$$c1 = (a0.c0) + (b0.c0) + (a0.b0)$$

$$\begin{array}{r}
 c3 \ c2 \ c1 \ c0 \\
 a3 \ a2 \ a1 \ a0 \\
 b3 \ b2 \ b1 \ b0 \\
 + \hline
 s3 \ s2 \ s1 \ s0
 \end{array}$$

$$c2 = (a1.c1) + (b1.c1) + (a1.b1)$$

$$= (a1. ((a0.c0) + (b0.c0) + (a0.b0))) + (b1.((a0.c0) + (b0.c0) + (a0.b0))) + (a1.b1)$$

$$= (a1 . a0 . c0) + (a1 . b0 . c0) + (a1 . a0 . b0)$$

$$+ (b1 . a0 . c0) + (b1 . b0 . c0) + (b1 . a0 . b0) + (a1 . b1)$$

Adder: Fast Carry using “infinite hardware”

$$\text{CarryIn1} = (b0.\text{CarryIn0}) + (a0.\text{CarryIn0}) + (a0.b0)$$

$$c1 = (a0.c0) + (b0.c0) + (a0.b0)$$

$$\begin{array}{cccc} & c3 & c2 & c1 & c0 \\ & a3 & a2 & a1 & a0 \\ + & b3 & b2 & b1 & b0 \\ \hline & s3 & s2 & s1 & s0 \end{array}$$

$$\begin{aligned} c2 &= (a1.c1) + (b1.c1) + (a1.b1) \\ &= (a1.(a0.c0) + (b0.c0) + (a0.b0)) + (b1.(a0.c0) + (b0.c0) + (a0.b0)) + (a1.b1) \\ &= (a1 . a0 . b0) + (a1 . a0 . c0) + (a1 . b0 . c0) \\ &\quad + (b1 . a0 . b0) + (b1 . a0 . c0) + (b1 . b0 . c0) + (a1 . b1) \end{aligned}$$

“direct” computation of carry (**sum of products**) ... fast, but complex

$$c3 = \dots$$

$$c4 = \dots$$

how many logic gates?
how long does it take?

Size of circuit grows **exponentially** (cfr. naive sum of products)

Adder: Fast Carry using “infinite hardware”

$$\text{CarryIn1} = (b0.\text{CarryIn0}) + (a0.\text{CarryIn0}) + (a0.b0)$$

$$c1 = (a0.c0) + (b0.c0) + (a0.b0)$$

$$\begin{array}{cccc} & c3 & c2 & c1 & c0 \\ & a3 & a2 & a1 & a0 \\ + & b3 & b2 & b1 & b0 \\ \hline & s3 & s2 & s1 & s0 \end{array}$$

$$c2 = (a1.c1) + (b1.c1) + (a1.b1)$$

$$= (a1.(a0.c0) + (b0.c0) + (a0.b0)) + (b1.(a0.c0) + (b0.c0) + (a0.b0)) + (a1.b1)$$

$$= (a1 . a0 . b0) + (a1 . a0 . c0) + (a1 . b0 . c0)$$

$$+ (b1 . a0 . b0) + (b1 . a0 . c0) + (b1 . b0 . c0) + (a1 . b1)$$

“direct” computation of carry (**sum of products**) ... fast, but complex

$$c3 = \dots$$

$$c4 = \dots$$

Size of circuit grows **exponentially**

how many logic gates?
how long does it take?

can we reduce #gates?
→ how long does it take?

Abstraction:

Propagate and Generate

$$c1 = (a0.c0) + (b0.c0) + (a0.b0) = (a0 + b0).c0 + (a0.b0)$$

propagate generate

Generate: “When do a_i en b_i generate a carry-out?”

	c3	c2	c1	c0
	a3	a2	a1	a0
	b3	b2	b1	b0
+	<hr/>			
	s3	s2	s1	s0

Abstraction:

Propagate and Generate

$$c1 = (a0.c0) + (b0.c0) + (a0.b0) = (a0 + b0).c0 + (a0.b0)$$

Generate: “When do a_i en b_i generate a carry-out?”

$$g_i = a_i \cdot b_i$$

	c3	c2	c1	c0
	a3	a2	a1	a0
	b3	b2	b1	b0
+	s3	s2	s1	s0

Abstraction:

Propagate and Generate

$$c1 = (a0.c0) + (b0.c0) + (a0.b0) = (a0 + b0).c0 + (a0.b0)$$

Generate: “When do a_i en b_i generate a carry-out?”

$$g_i = a_i \cdot b_i$$

Propagate: “When do a_i en b_i propagate a carry?”

$$\begin{array}{cccc} c3 & c2 & c1 & c0 \\ a3 & a2 & a1 & a0 \\ b3 & b2 & b1 & b0 \\ + \hline s3 & s2 & s1 & s0 \end{array}$$

Abstraction:

Propagate and Generate

$$c1 = (a0.c0) + (b0.c0) + (a0.b0) = (a0 + b0).c0 + (a0.b0)$$

Generate: “When do a_i en b_i generate a carry-out?”

$$g_i = a_i \cdot b_i$$

Propagate: “When do a_i en b_i propagate a carry?”

$$p_i = a_i + b_i$$

$$\begin{array}{cccc} c3 & c2 & c1 & c0 \\ a3 & a2 & a1 & a0 \\ b3 & b2 & b1 & b0 \\ + \hline s3 & s2 & s1 & s0 \end{array}$$

Abstraction:

Propagate and Generate

$$c1 = (a0.c0) + (b0.c0) + (a0.b0) = (a0 + b0).c0 + (a0.b0)$$

Generate: “When do a_i en b_i generate a carry-out?”

$$g_i = a_i \cdot b_i$$

Propagate: “When do a_i en b_i propagate a carry?”

$$p_i = a_i + b_i$$

$$\begin{array}{rcccc} & c3 & c2 & c1 & c0 \\ & a3 & a2 & a1 & a0 \\ + & b3 & b2 & b1 & b0 \\ \hline & s3 & s2 & s1 & s0 \end{array}$$

generate + propagate * carryin

$$\text{carry-out}_i = g_i + p_i \cdot c_i$$

note that g_i and p_i do not depend on c_i

$$\text{carry-in}_{i+1} = \text{carry-out}_i = g_i + p_i \cdot c_i$$

g_i en p_i hangen puur af van $a0$ en $b0$

“generate”

$$g_i = a_i \cdot b_i$$

“propagate”

$$p_i = a_i + b_i$$

$$c_{i+1} = g_i + p_i \cdot c_i$$

When $g_i = 1$:



$$c_{i+1} = g_i + p_i \cdot c_i = 1 + p_i \cdot c_i = 1 \quad \text{independent of } c_i : \text{“generate”}$$

When $g_i = 0$ and $p_i = 1$:

$$c_{i+1} = 0 + 1 \cdot c_i = c_i$$

independent of a_i and b_i
: “propagate” c_i

Adder: Fast Carry

“Carry-Lookahead” (16-bit adder)

Level of abstraction 1 (4-bit adder)

$$\begin{aligned}c_1 &= (a_0.b_0) + (a_0 + b_0).c_0 \\c_2 &= (a_1.b_1) + (a_1 + b_1).c_1 \\&= (a_1.b_1) + (a_1 + b_1).((a_0.b_0) + (a_0 + b_0).c_0)\end{aligned}$$

$$\begin{array}{rcccccc} & c_4 & c_3 & c_2 & c_1 & c_0 \\ & & a_3 & a_2 & a_1 & a_0 \\ & & b_3 & b_2 & b_1 & b_0 \\ + & \hline s_4 & s_3 & s_2 & s_1 & s_0\end{array}$$

“generate” $g_i = a_i.b_i$
“propagate” $p_i = a_i + b_i$

$$C_{i+1} = g_i + p_i.C_i$$


$$\begin{aligned}c_1 &= g_0 + p_0.c_0 \\c_2 &= g_1 + (p_1.g_0) + (p_1.p_0.c_0) \\c_3 &= g_2 + (p_2.g_1) + (p_2.p_1.g_0) + (p_2.p_1.p_0.c_0) \\c_4 &= g_3 + (p_3.g_2) + (p_3.p_2.g_1) + (p_3.p_2.p_1.g_0) + (p_3.p_2.p_1.p_0.c_0)\end{aligned}$$

how many logic gates?
how long does it take? ^{3 epsilon}

1 grote OR gate per 'c', maar parallel ==> 1 epsilon

OR | AND | OR/AND ==> 3 epsilon

Plumbing Analogy

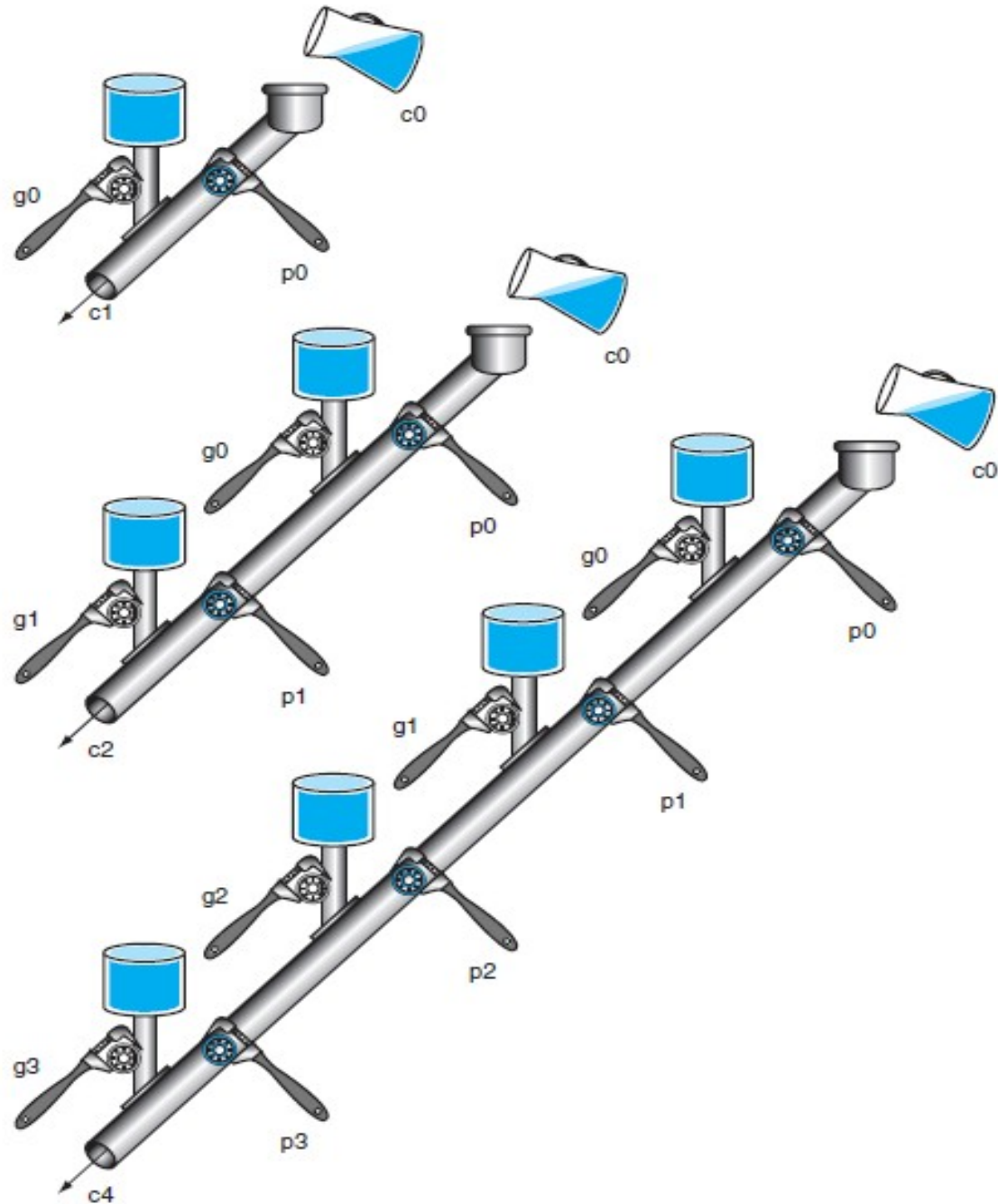

Calculate Carry

$$\begin{array}{rccccccccc} & & c4 & c3 & c2 & c1 & c0 & & & \\ & & & a3 & a2 & a1 & a0 & & & \\ + & & & b3 & b2 & b1 & b0 & & & \\ \hline & s4 & s3 & s2 & s1 & s0 & & & & \end{array}$$

$$\begin{aligned} c1 &= g0 + p0 \cdot c0 \\ c2 &= g1 + (p1 \cdot g0) + (p1 \cdot p0 \cdot c0) \\ c3 &= g2 + (p2 \cdot g1) + (p2 \cdot p1 \cdot g0) + (p2 \cdot p1 \cdot p0 \cdot c0) \end{aligned}$$

Calculate Carry

$$\begin{array}{rcccccc} & c4 & c3 & c2 & c1 & c0 \\ & & a3 & a2 & a1 & a0 \\ + & & b3 & b2 & b1 & b0 \\ \hline & s4 & s3 & s2 & s1 & s0 \end{array}$$

$$c4 = g3 + (p3.g2) + (p3.p2.g1) + (p3.p2.p1.g0) + (p3.p2.p1.p0.c0)$$

note: **only** depends on c0 and a0,b0 a1,b1 a2,b2 a3, b3


Carry-Lookahead

Level of abstraction 2

hoe alles aan elkaar hangen

16-bit adder using
4 x 4-bit efficient adders

4 bit adder
niet ripple 1
bits

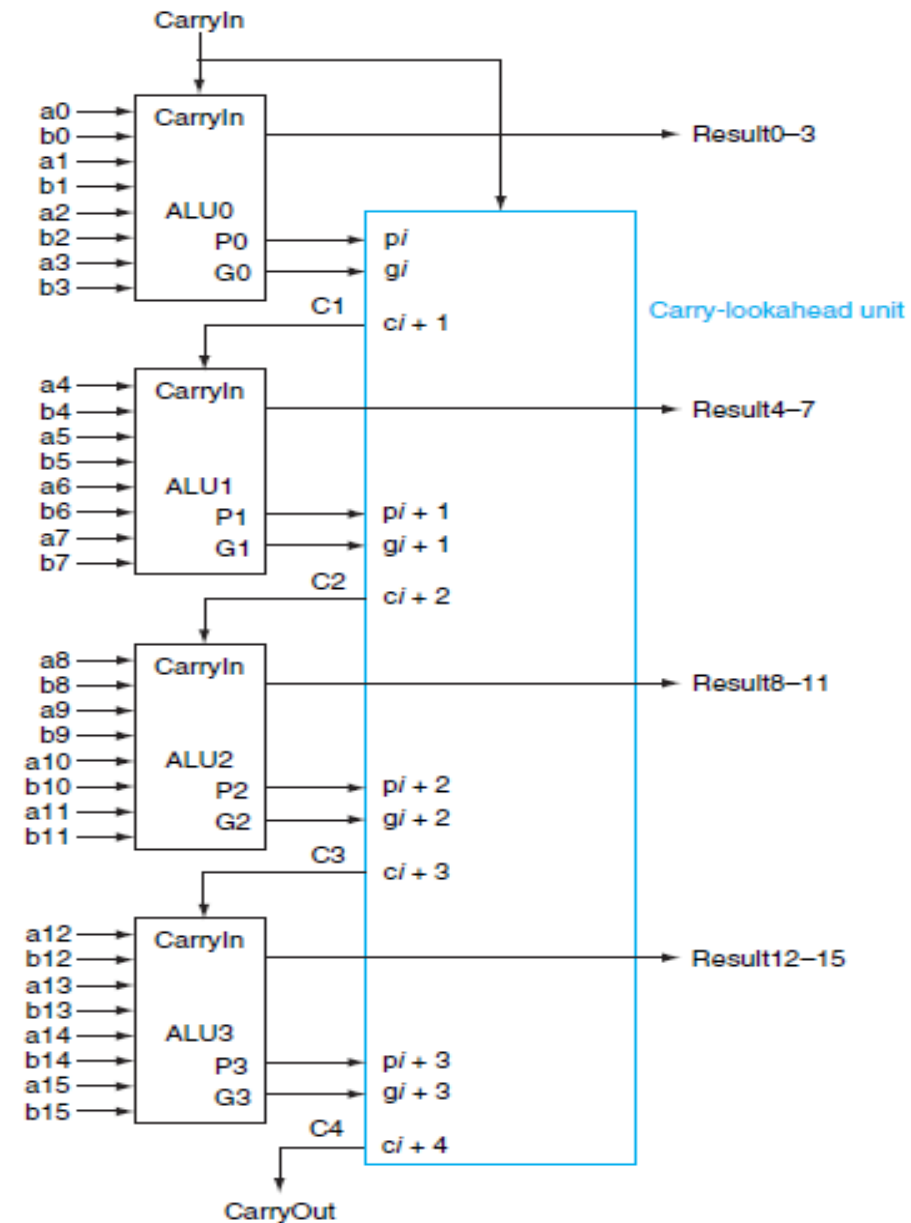

Level of abstraction 2

Super-Propagate and Super-Generate

$$c4 = g3 + (p3.g2) + (p3.p2.g1) + (p3.p2.p1.g0) + (p3.p2.p1.p0.c0)$$

Super-Propagate: “When do $A_{0,4}$ en $B_{0,4}$ propagate a carry?”

Level of abstraction 2

Super-Propagate and Super-Generate

$$c4 = g3 + (p3.g2) + (p3.p2.g1) + (p3.p2.p1.g0) + (p3.p2.p1.p0.c0)$$

Super-Propagate: “When do $A_{0,4}$ en $B_{0,4}$ propagate a carry?”

$$P0 = p3.p2.p1.p0$$

Level of abstraction 2

Super-Propagate and Super-Generate

$$c4 = g3 + (p3.g2) + (p3.p2.g1) + (p3.p2.p1.g0) + (p3.p2.p1.p0.c0)$$

Super-Propagate: “When do $A_{0,4}$ en $B_{0,4}$ propagate a carry?”

$$P0 = p3.p2.p1.p0$$

Super-Generate: “When do $A_{0,4}$ en $B_{0,4}$ generate a carry-out?”

Level of abstraction 2

Super-Propagate and Super-Generate

$$c4 = g3 + (p3.g2) + (p3.p2.g1) + (p3.p2.p1.g0) + (p3.p2.p1.p0.c0)$$


Super-Propagate: “When do $A_{0,4}$ en $B_{0,4}$ propagate a carry?”

$$P0 = p3.p2.p1.p0$$

Super-Generate: “When do $A_{0,4}$ en $B_{0,4}$ generate a carry-out?”

$$G0 = g3 + (p3.g2) + (p3.p2.g1) + (p3.p2.p1.g0)$$

Plumbing Analogy

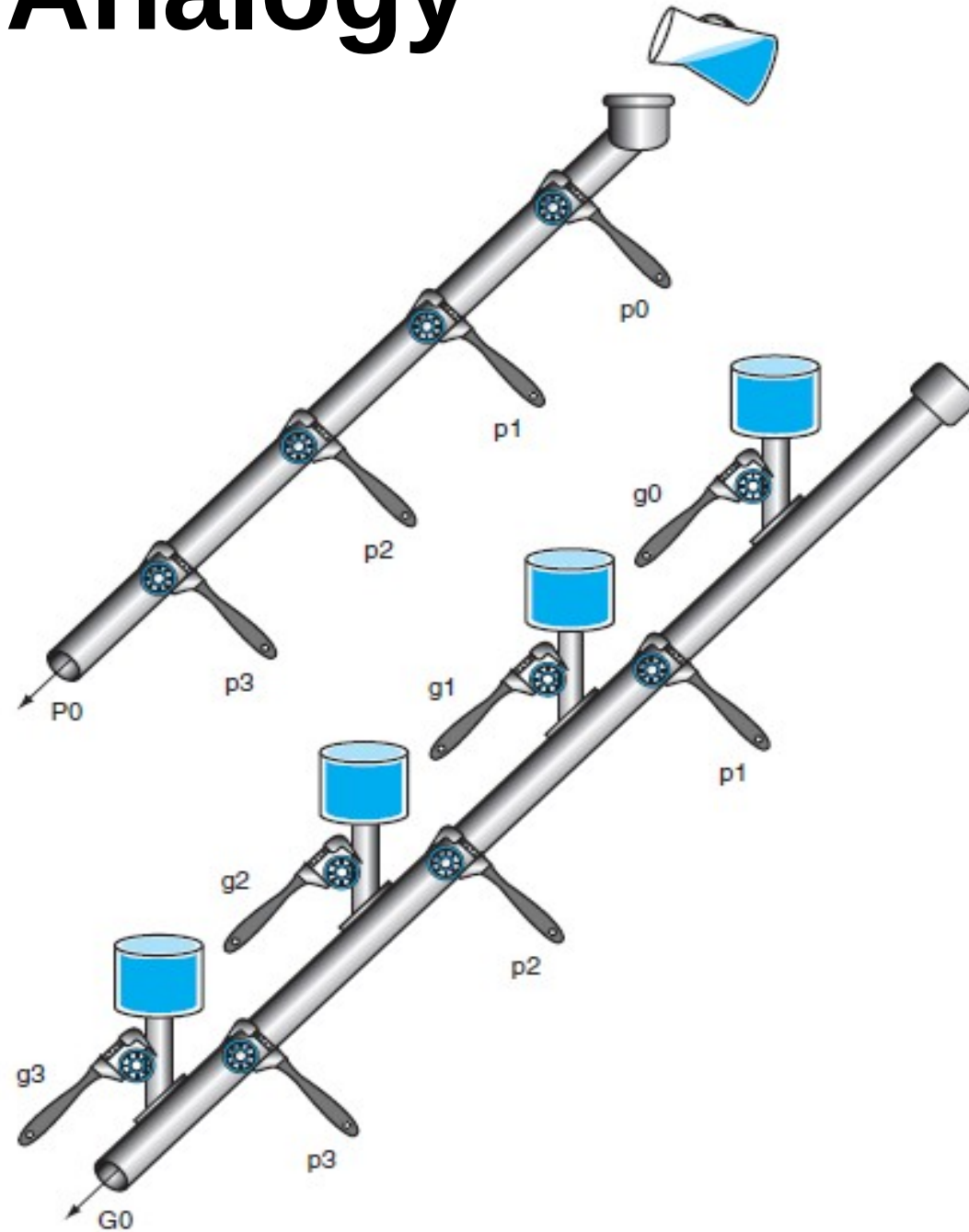

Level of abstraction 2

Super-Propagate and Super-Generate

$$c4 = g3 + (p3.g2) + (p3.p2.g1) + (p3.p2.p1.g0) + (p3.p2.p1.p0.c0)$$

Super-Propagate: “When do $A_{0,4}$ en $B_{0,4}$ propagate a carry?”

$$P0 = p3.p2.p1.p0$$

Super-Generate: “When do $A_{0,4}$ en $B_{0,4}$ generate a carry-out?”

$$G0 = g3 + (p3.g2) + (p3.p2.g1) + (p3.p2.p1.g0)$$


$$\underline{C1} = G0 + (P0.c0)$$

weer hetzelfde als ervoor

Carry-Lookahead

Level of abstraction 2

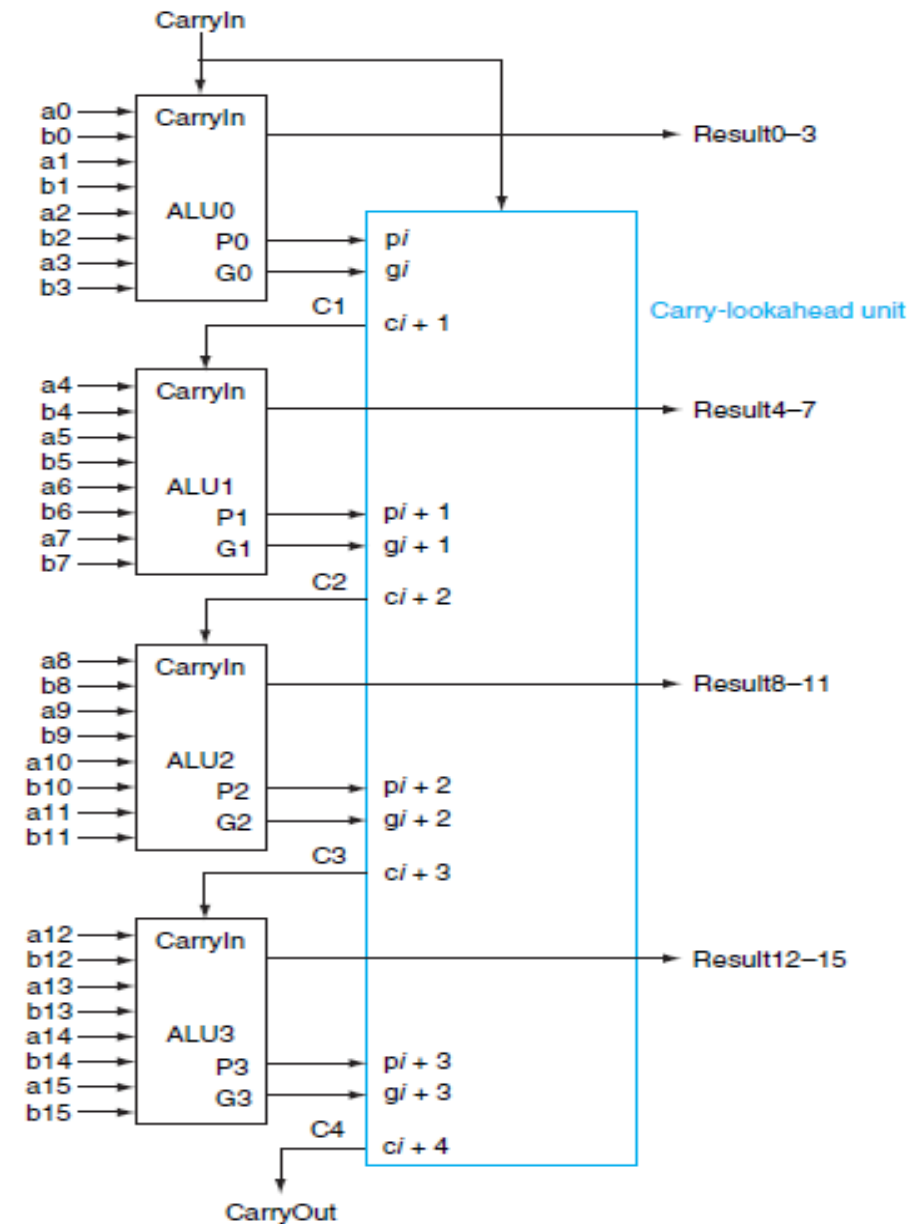16-bit adder using
4 x 4-bit efficient adders



Carry-Lookahead

Level of abstraction 2 (16-bit adder)

<https://www.youtube.com/watch?v=SQKdnxysXnw&pp=ygUpY2FycnkGbG9vayBhaGVhZCBhZGRlciBhYnN0cmFjdGlubiBsZXZlbHM%3D>

$$P0 = p3.p2.p1.p0$$

$$P1 = p7.p6.p5.p4$$

$$P2 = p11.p10.p9.p8$$

$$P3 = p15.p14.p13.p12$$

$$G0 = g3 + (p3.g2) + (p3.p2.g1) + (p3.p2.p1.g0)$$

$$G1 = g7 + (p7.g6) + (p7.p6.g5) + (p7.p6.p5.g4)$$

$$G2 = g11 + (p11.g10) + (p11.p10.g9) + (p11.p10.p9.g8)$$

$$G3 = g15 + (p15.g14) + (p15.p14.g13) + (p15.p14.p13.g12)$$

$$\underline{C1} = G0 + (P0.c0)$$

$$C2 = G1 + (P1.G0) + (P1.P0.c0)$$

$$C3 = G2 + (P2.G1) + (P2.P1.G0) + (P2.P1.P0.c0)$$

$$C4 = G3 + (P3.G2) + (P3.P2.G1) + (P3.P2.P1.G0) + (P3.P2.P1.P0.c0)$$

Carry-Lookahead

Level of abstraction 2 (16-bit adder)

$$P0 = p3.p2.p1.p0$$

$$P1 = p7.p6.p5.p4$$

$$P2 = p11.p10.p9.p8$$

$$P3 = p15.p14.p13.p12$$

$$G0 = g3 + (p3.g2) + (p3.p2.g1) + (p3.p2.p1.g0)$$

$$G1 = g7 + (p7.g6) + (p7.p6.g5) + (p7.p6.p5.g4)$$

$$G2 = g11 + (p11.g10) + (p11.p10.g9) + (p11.p10.p9.g8)$$

$$G3 = g15 + (p15.g14) + (p15.p14.g13) + (p15.p14.p13.g12)$$

$$\underline{C1} = G0 + (P0.c0)$$

$$C2 = G1 + (P1.G0) + (P1.P0.c0)$$

$$C3 = G2 + (P2.G1) + (P2.P1.G0) + (P2.P1.P0.c0)$$

$$C4 = G3 + (P3.G2) + (P3.P2.G1) + (P3.P2.P1.G0) + (P3.P2.P1.P0.c0)$$

how many logic gates?
how long does it take?

Binary representation/encoding of Unsigned Integers

n-bit string “ $x_{n-1}x_{n-2} \dots x_1x_0$ ” has/encodes **value** x

$$x = x_{n-1}2^{n-1} + x_{n-2}2^{n-2} + \dots + x_12^1 + x_02^0$$

x_0 Least Significant Bit (**LSB**)

x_{n-1} Most Significant Bit (**MSB**)

- Range: 0 to $+2^n - 1$

- Example

- $0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 1011_2$
 $= 0 + \dots + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0$
 $= 0 + \dots + 8 + 0 + 2 + 1 = 11_{10}$

Addition of Unsigned Integers in binary representation/encoding

0	Carry	0
1110	A	14
+ 0111	B	+ 7
<hr/>		<hr/>
	Result	

Addition of Unsigned Integers in binary representation/encoding

11100	Carry	10
1110	A	14
+ 0111	B	+ 7
<hr/>		<hr/>
10101	Result	21

2's complement binary representation/encoding of Signed Integers

met n bits kan ik 2^n dingen voorstellen

==> 1 vooraan = -

n-bit string ' $x_{n-1}x_{n-2} \dots x_1x_0$ ' has **value** x

$$x = -x_{n-1}2^{n-1} + x_{n-2}2^{n-2} + \dots + x_12^1 + x_02^0$$

101: $-4 + 0 + 1 = -3$

100	-4
101	-3
110	-2
111	-1
000	0
001	1
010	2
011	3

VB:
x 011 =3

!x 100
+1 001

101 = -3

negatieve versie van getal vinden

	unsigned	signed
000	0	0
001	1	1
010	2	2
011	3	3
100	4	-4
101	5	-3
110	6	-2
111	7	-1

!! nog eens herbekijken, ik snap het niet !!

Negation for 2's complement

Complement and add 1

complement means $1 \rightarrow 0, 0 \rightarrow 1$

$$x + \bar{x} = 1111 \dots 111_2 = -1$$

$$\bar{x} + 1 = -x$$

Example: negate +2

$$\blacksquare +2 = 0000 \ 0000 \ \dots \ 0010_2$$


$$\blacksquare -2 = 1111 \ 1111 \ \dots \ 1101_2$$

$$+ 1_2$$

$$= 1111 \ 1111 \ \dots \ 1110_2$$

Note: works for positive and negative numbers

1-bit ALU with subtraction

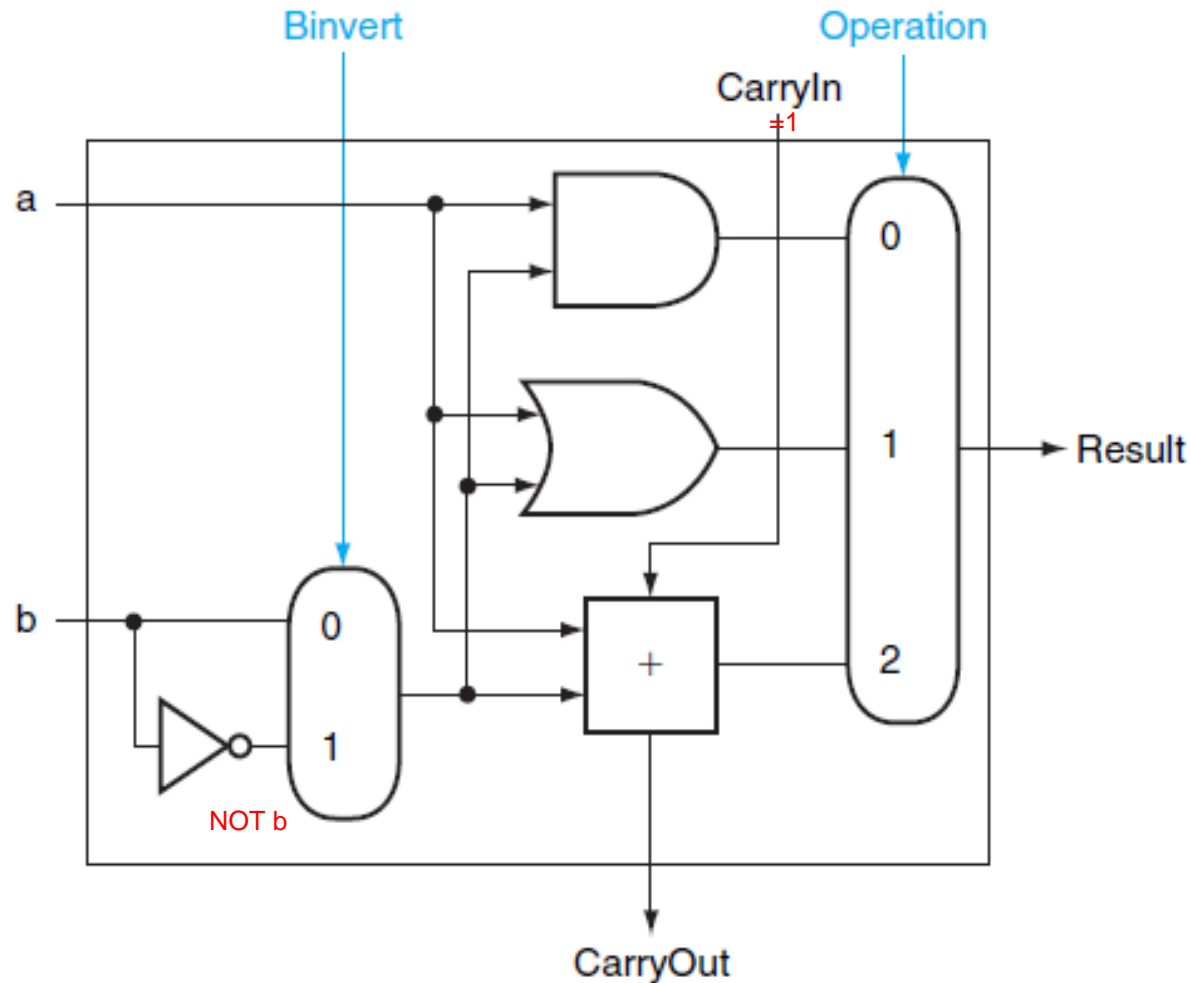


$$\begin{aligned} a - b &= a + (-b) \\ &= a + (\bar{b} + \overset{\text{carryin}}{1}) \end{aligned}$$

($\bar{}$ = 1's complement)

Binvert **and** *CarryIn*: 1

1-bit ALU with NOR
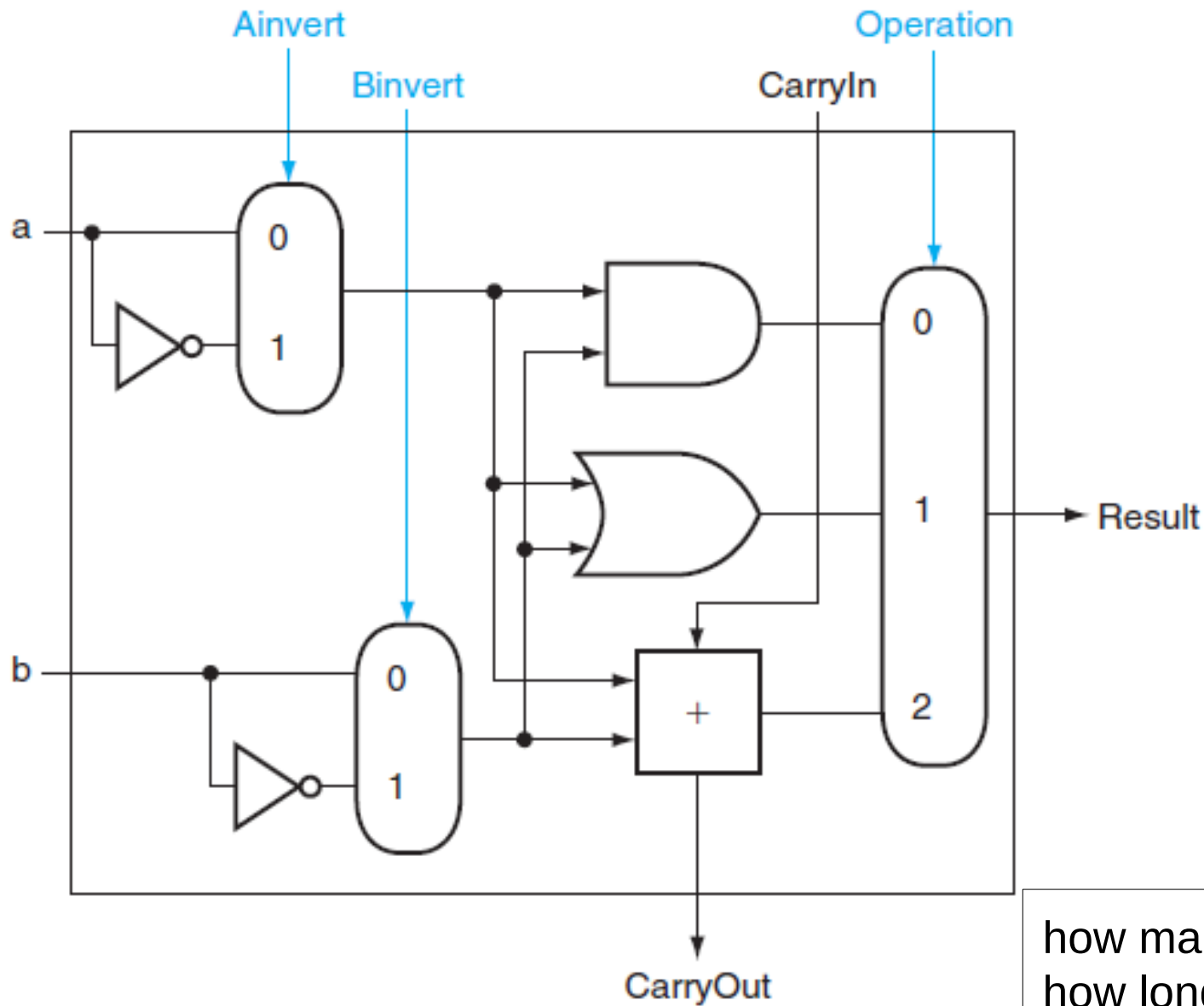
$$a \text{ NOR } b = \text{not}(a \text{ OR } b) = (\text{not } a) \text{ AND } (\text{not } b)$$



how many logic gates?
how long does it take?

Overflow Conditions

(for 2's complement signed binary integers)

Operation	Operand A	Operand B	Result indicating overflow
$A + B$	≥ 0	≥ 0	< 0
$A + B$	< 0	< 0	≥ 0
$A - B$	≥ 0	< 0	< 0
$A - B$	< 0	≥ 0	≥ 0

SIGNED INTEGERS (gehele getallen)

oef:

```

1
010 ==2
+ 011 ==3
-----
101 == -3
  
```

OVERFLOW

MSB (eerste) najken

```

0
0
1
  
```

SIGNED INTEGERS (natuurlijke getallen)

oef:

```

1
010 ==2
+ 011 ==3
-----
101 ==> 5
  
```

oef:

carryin = 1 & valt weg

```

111
101 ==5
+ 011 ==3
-----
  
```

```

000 ==> 0
  
```

(3 bit unsigned optelling)

MOD(8) optellen

dus 8 = 0, 12 = 4 ... VAN 0 - 7

Unsigned Binary Addition


“modulo” calculation, no overflow!

$$\begin{aligned} \text{N bits: } (2^N) \text{ MOD } 2^N &= 0 = [[2^N]] \\ (2^N) \text{ DIV } 2^N &= 1 \end{aligned}$$


$$[[2^N + k]] = (2^N + k) \text{ MOD } 2^N = k$$

used in for example memory address calculation (Program Counter)

1-bit ALU (AND, OR, +, -, slt)

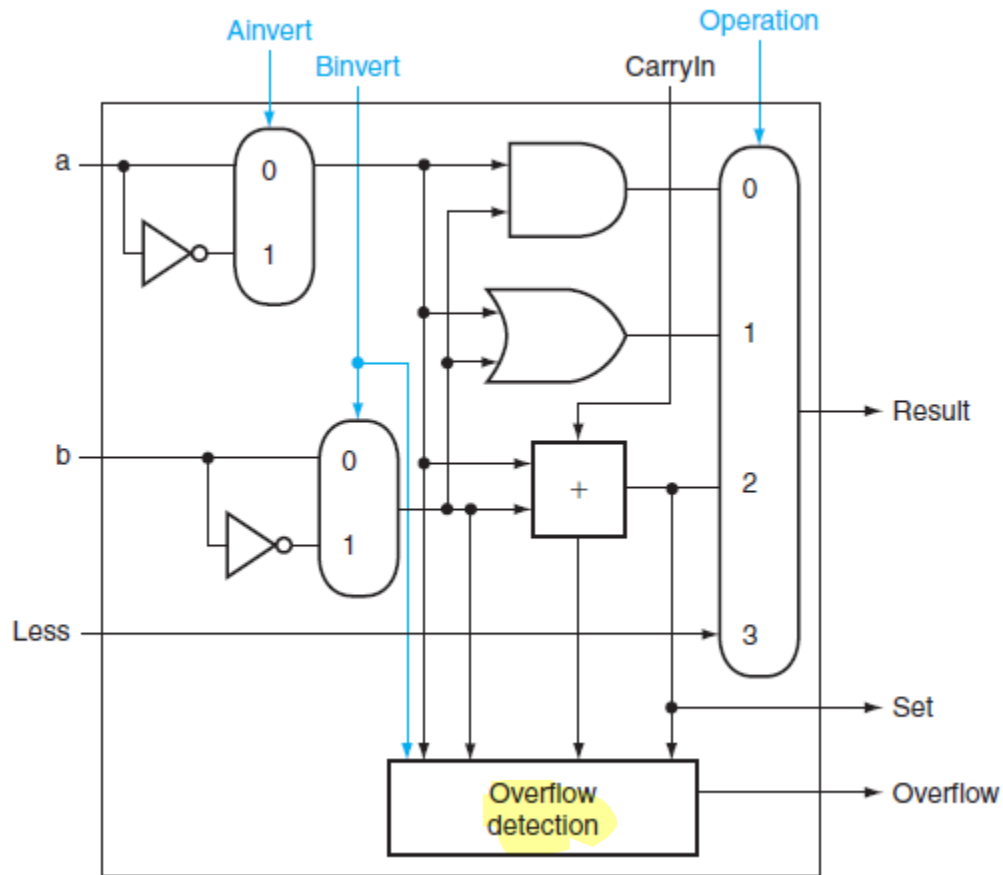

MSb

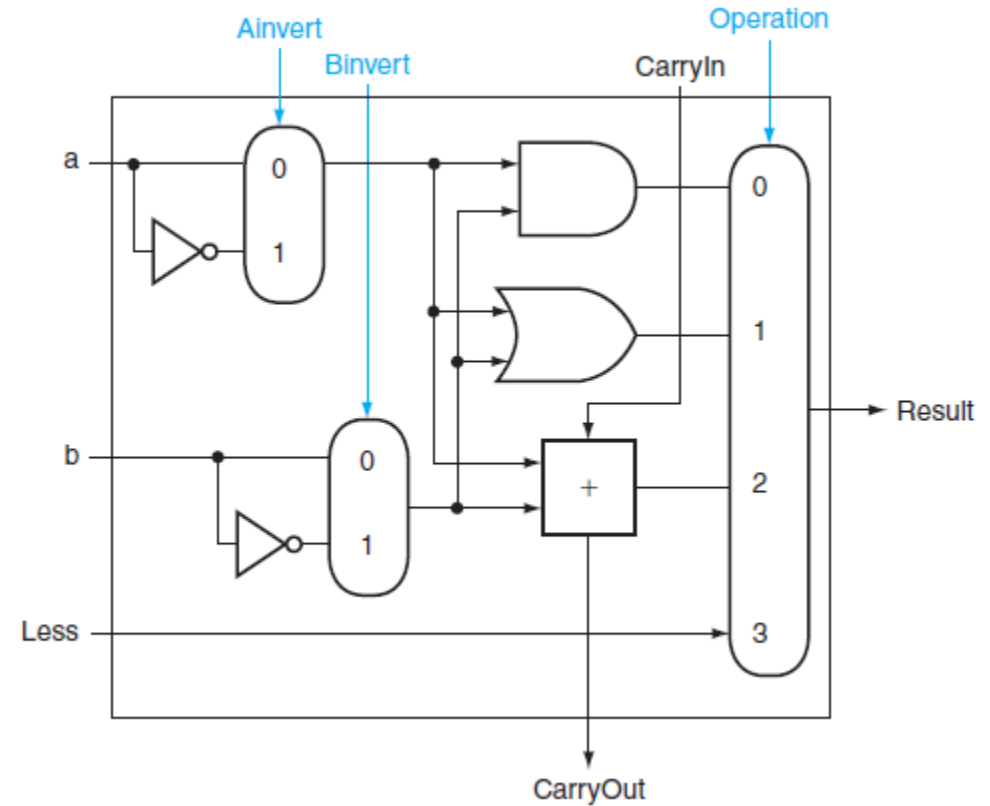


non-MSb

32-bit ALU: only connect

```
getal a = 32 bits
getal b = 32 bits
set less than
```

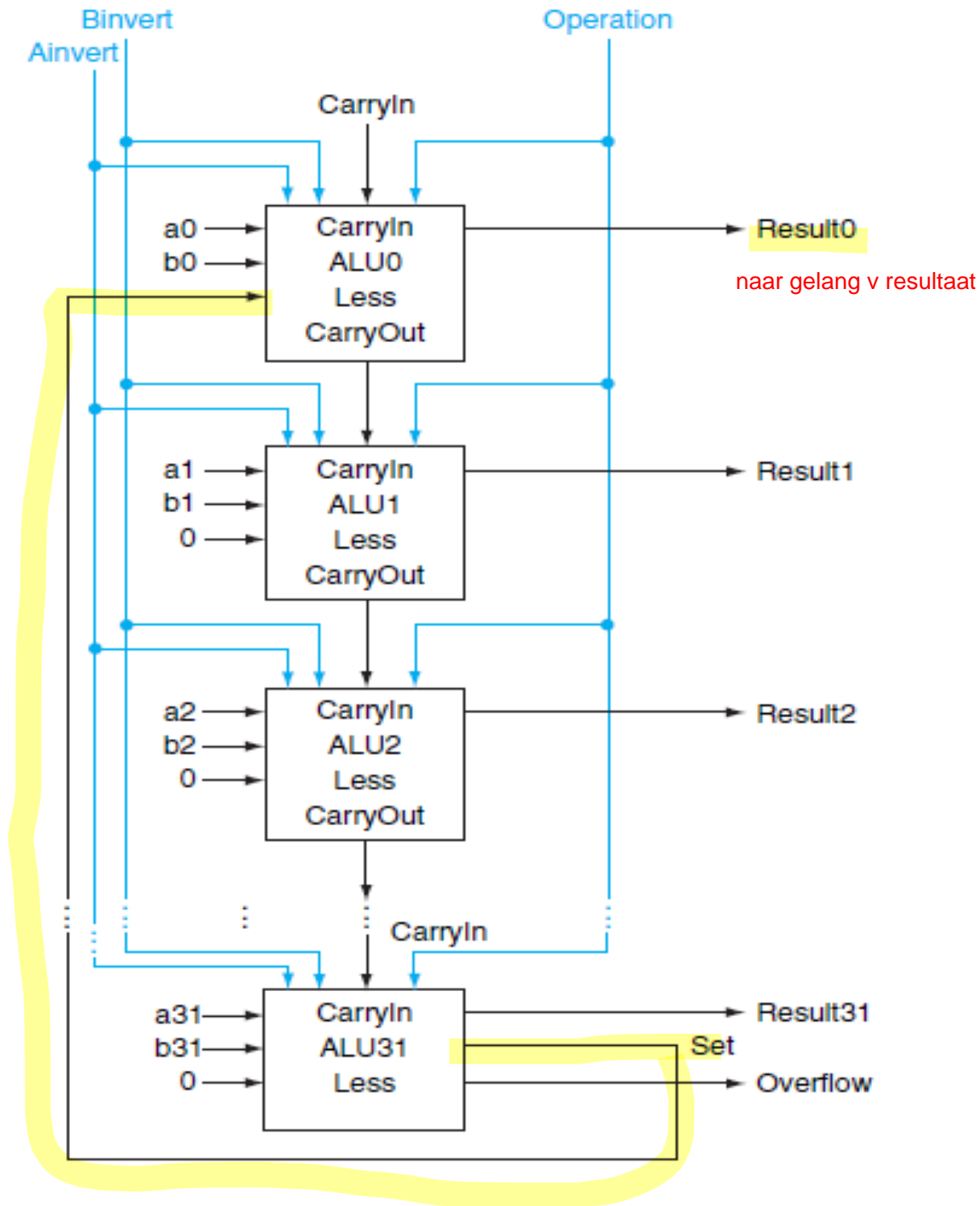hoogste bit bekijken
==> zien ofdat we die op 1 of 0 zetten



How to efficiently compare **non-negative** numbers?

(useful for fast comparison of Floating Point number exponents)

Is $A > B$?

e.g., is $00101000 > 00111010$

Solution:

NOT: check whether $A - B$ is negative (as for `slt`)
this works for unsigned numbers, but is slow ...

maar ter informatie
niet belangrijk

How to efficiently compare **non-negative** numbers?

Is $A > B$?

Solution:

from MSB to LSB (left to right): **compare bit per bit**

```
00101000
00111010
```

Assuming that the two bit strings
(representing non-negative integers) both have N bits

```
for i = N-1 downto 0:
    if bit  $A_i > B_i$  then
        A is larger than B
        break
    elif bit  $A_i < B_i$  then
        A is smaller than B
        break
    else // bit  $A_i == B_i$ 
        if i == 0 then
            A is equal to B
// else
//     continue loop with next i
```


How to efficiently compare **non-negative** numbers?

Is $A > B$?

Solution:

but we want a **hardware** solution ...

check whether i^{th} bits are equal $(A_i == B_i) = A_i \cdot B_i + \bar{A}_i \cdot \bar{B}_i = e_i$

check whether i^{th} bits $<$ $(A_i < B_i) = \bar{A}_i \cdot B_i$

check whether i^{th} bits $>$ $(A_i > B_i) = A_i \cdot \bar{B}_i$


4 bits example, check $A > B$:

$$A_3 \cdot \bar{B}_3 + e_3 \cdot A_2 \cdot \bar{B}_2 + e_3 \cdot e_2 \cdot A_1 \cdot \bar{B}_1 + e_3 \cdot e_2 \cdot e_1 \cdot A_0 \cdot \bar{B}_0$$

Number of gates?
Delay?

maar ter informatie
niet belangrijk

32-bit ALU with zero detect

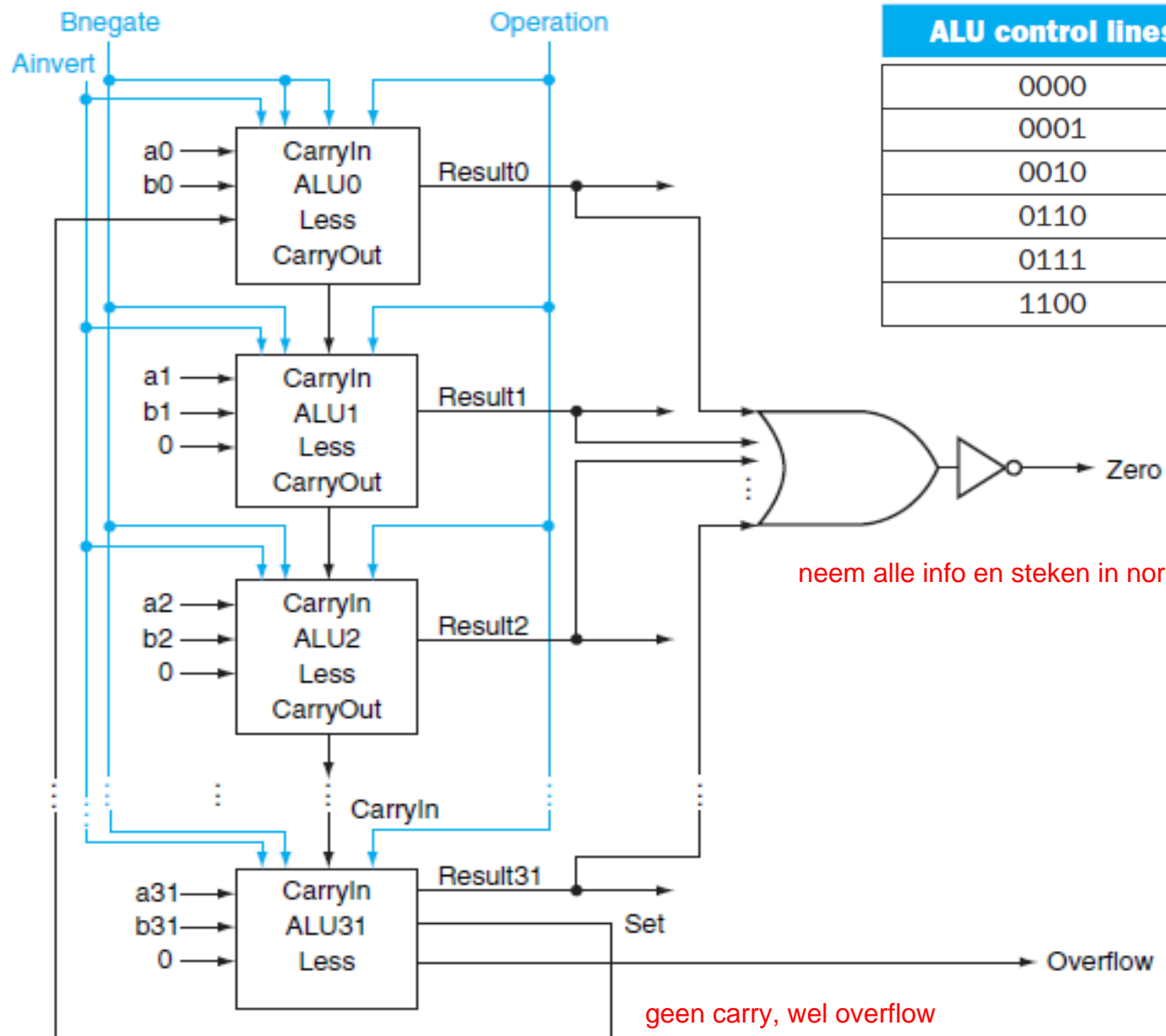

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR

Higher-level: ALU

